



**UTM**  
UNIVERSITI TEKNOLOGI MALAYSIA



innovative • entrepreneurial • global

ONLINE

LEARNING

# Digital Electronics (SKEE1223)

## Boolean Algebra

Muhammad Arif Abd Rahim

Muhammad Mun'im Ahmad Zabidi

Ab Hadi Abd Rahman

Faculty of Electrical Engineering

# Introduction

- Boolean algebra consists of:
  - Boolean Theorems
  - DeMorgan's Theorem


# Boolean Theorems

<b>Theorem 1</b>	$A + 0 = A$	$A \cdot 1 = A$
<b>Theorem 2</b>	$A + \bar{A} = 1$	$A \cdot \bar{A} = 0$
<b>Theorem 3</b>	$A + A = A$	$A \cdot A = A$
<b>Theorem 4</b>	$A + 1 = 1$	$A \cdot 0 = 0$
<b>Theorem 5</b>		$\bar{\bar{A}} = A$
<b>Theorem 6</b>	$A + B = B + A$	$A \cdot B = B \cdot A$
<b>Theorem 7</b>	$A + (B + C) = (A + B) + C$	$A \cdot (B \cdot C) = (A \cdot B) \cdot C$
<b>Theorem 8</b>	$A \cdot (B + C) = A \cdot B + A \cdot C$	$A + B \cdot C = (A + B)(A + C)$
<b>Theorem 9</b>	$A + A \cdot B = A$	$A \cdot (A + B) = A$
<b>Theorem 10</b>	$A + \bar{A} \cdot B = A + B$	$A \cdot (\bar{A} + B) = A \cdot B$

# DeMorgan's Theorem

$$\overline{A \cdot B} = \bar{A} + \bar{B}$$

$$\overline{A + B} = \bar{A}\bar{B}$$

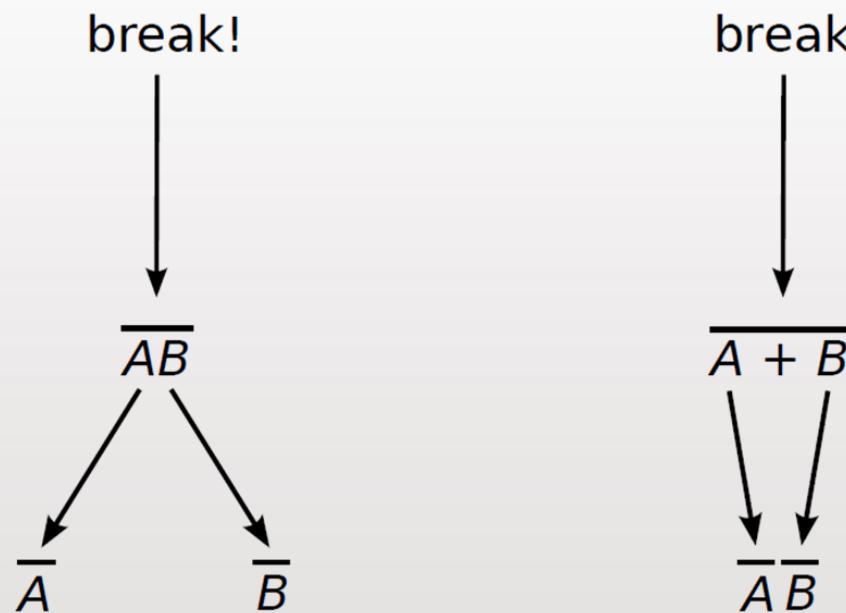

# Example of Boolean Proof

$$\begin{aligned} A + \bar{A}B &= A + B \\ &= A(\bar{B} + B) + \bar{A} \cdot B & \bar{B} + B = 1 \\ &= A\bar{B} + AB + \bar{A} \cdot B \\ &= A\bar{B} + AB + AB + \bar{A} \cdot B & AB + AB = AB \\ &= A(\bar{B} + B) + B(\bar{A} + A) \\ &= A + B \end{aligned}$$

# Boolean Expressions

SOP

POS

Sum-of-  
Products

Product-of-  
Sums

# Canonical SOP

- Each AND term must have all the input variables (or their complements).

Simplified or Minimized SOP

$$F(A, B, C) = A \cdot B + \bar{B} \cdot C$$

Canonical SOP

$$F(A, B, C) = \bar{A} \cdot \bar{B} \cdot C + A \cdot \bar{B} \cdot C + A \cdot B \cdot \bar{C} + A \cdot B \cdot C$$

# Canonical POS

- Each OR term must have all the input variables (or their complements).

Simplified or Minimized SOP

$$F(A, B, C) = (A + \bar{B})(B + C)$$

Canonical SOP

$$F(A, B, C) = (\bar{A} + B + C) \cdot (A + \bar{B} + \bar{C}) \cdot (A + \bar{B} + C) \cdot (A + B + C)$$



# Minterms & Maxterms

Decimal Equivalent		Minterm		Maxterm	
	ABC	Expression	Symbol	Expression	Symbol
0	000	$\bar{A} \cdot \bar{B} \cdot \bar{C}$	$m_0$	$A + B + C$	$M_0$
1	001	$\bar{A} \cdot \bar{B} \cdot C$	$m_1$	$A + B + \bar{C}$	$M_1$
2	010	$\bar{A} \cdot B \cdot \bar{C}$	$m_2$	$A + \bar{B} + C$	$M_2$
3	011	$\bar{A} \cdot B \cdot C$	$m_3$	$A + \bar{B} + \bar{C}$	$M_3$
4	100	$A \cdot \bar{B} \cdot \bar{C}$	$m_4$	$\bar{A} + B + C$	$M_4$
5	101	$A \cdot \bar{B} \cdot C$	$m_5$	$\bar{A} + B + \bar{C}$	$M_5$
6	110	$A \cdot B \cdot \bar{C}$	$m_6$	$\bar{A} + \bar{B} + C$	$M_6$
7	111	$A \cdot B \cdot C$	$m_7$	$\bar{A} + \bar{B} + \bar{C}$	$M_7$

# Deriving SOP Canonical Expressions

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Minterm

$\bar{A} \cdot \bar{B} \cdot C$

$$\begin{aligned}F &= \bar{A} \cdot \bar{B} \cdot C + A \cdot \bar{B} \cdot C + A \cdot B \cdot \bar{C} + A \cdot B \cdot C \\&= \Sigma(m_1 + m_5 + m_6 + m_7) \\&= \Sigma m(1, 5, 6, 7)\end{aligned}$$

$A \cdot \bar{B} \cdot C$

$A \cdot B \cdot \bar{C}$

$A \cdot \bar{B} \cdot \bar{C}$

# Deriving POS Canonical Expressions

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

**Maxterm**

$$A + B + C$$

$$A + \bar{B} + C$$

$$A + \bar{B} + \bar{C}$$

$$\bar{A} + B + C$$


$$F = (A + B + C)(A + \bar{B} + C)(A + \bar{B} + \bar{C}) \\ (\bar{A} + B + C)$$

$$= \prod (M_0 + M_2 + M_3 + M_4)$$

$$= \prod M(0,2,3,4)$$

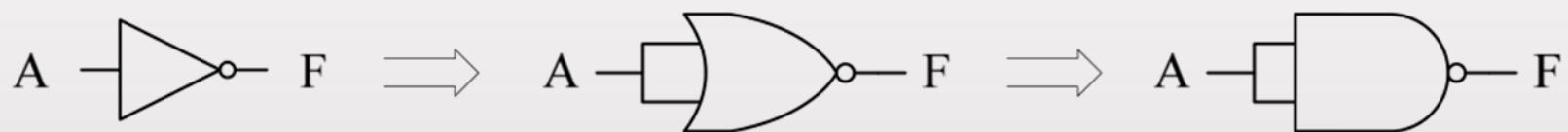
# Universal Gates

- NAND and NOR gates are universal
- Any Boolean function can be implemented using either of these gates only.





*NOT gate implemented using NOR or NAND gates*

# Implementing the NOT gate

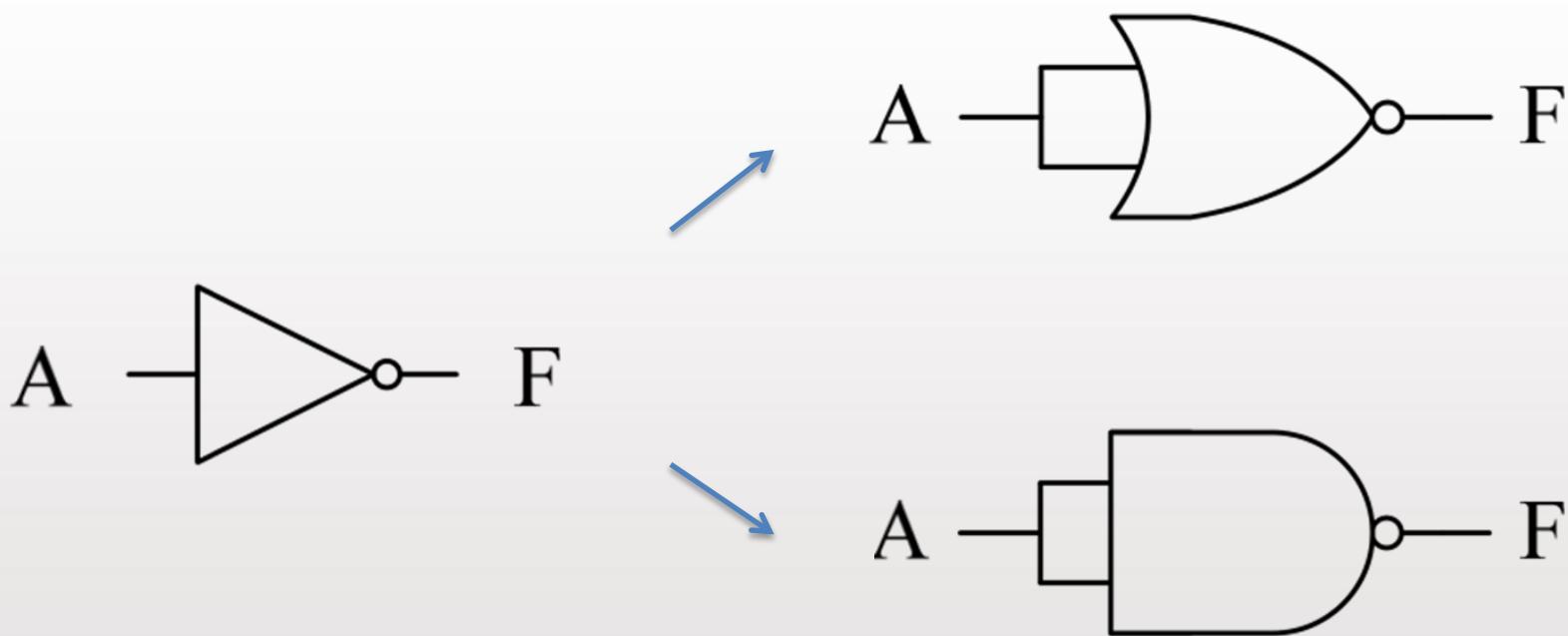


# Implementing the OR gate

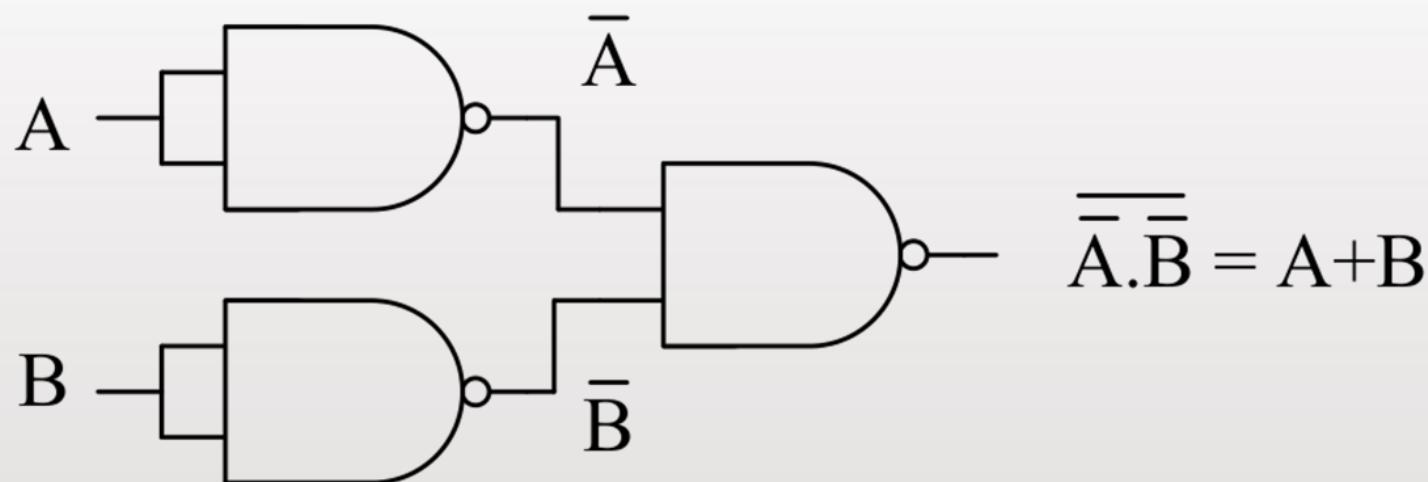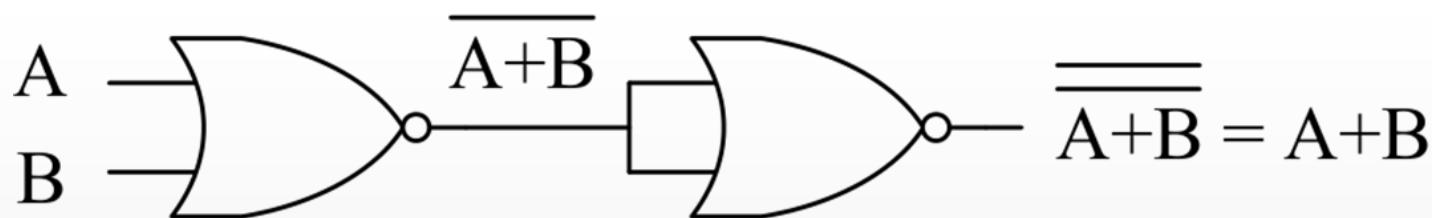

# Alternative Logic Symbols


- All basic gates (except XOR and XNOR) have alternative symbols which can be obtained as follows :
  1. Add bubbles to the inputs. Add a bubble at the output if there is no bubble in the standard symbol and remove it if there is one.
  2. Change the gate from AND to OR or vice-versa

# Alternative Symbol for NAND

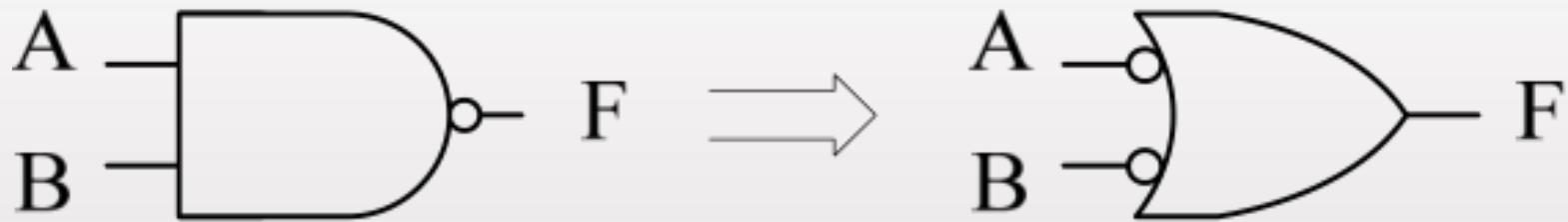

$$\overline{A \cdot B} = \bar{A} + \bar{B}$$

# Interpreting the Alternative Symbol

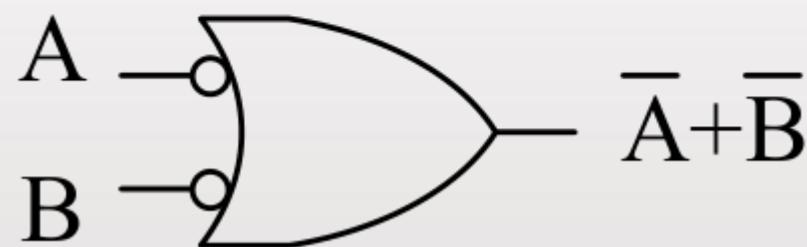

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

## Circuit Configurations


AND-OR

OR-AND


NAND-NAND

NOR-NOR


# AND-OR Configuration

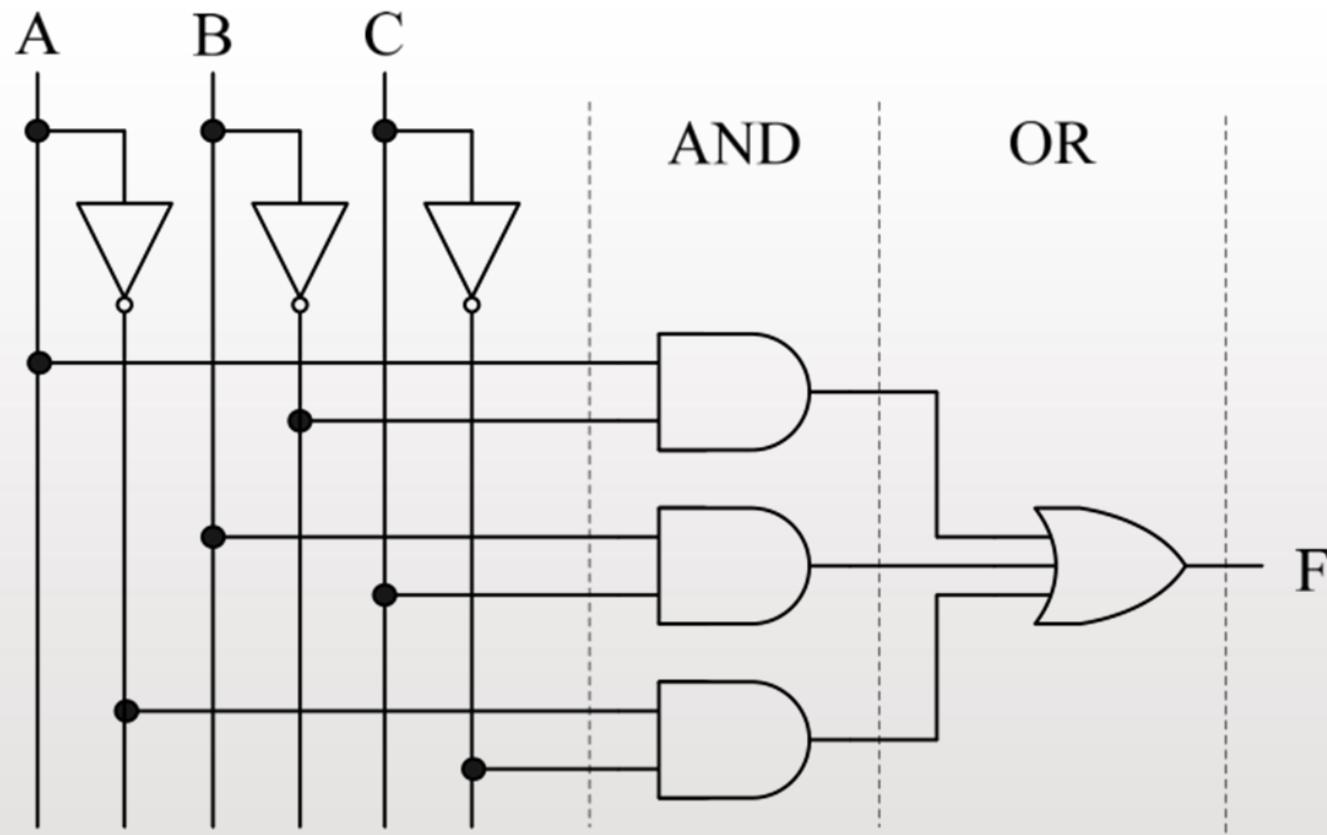

# NAND-NAND Configuration

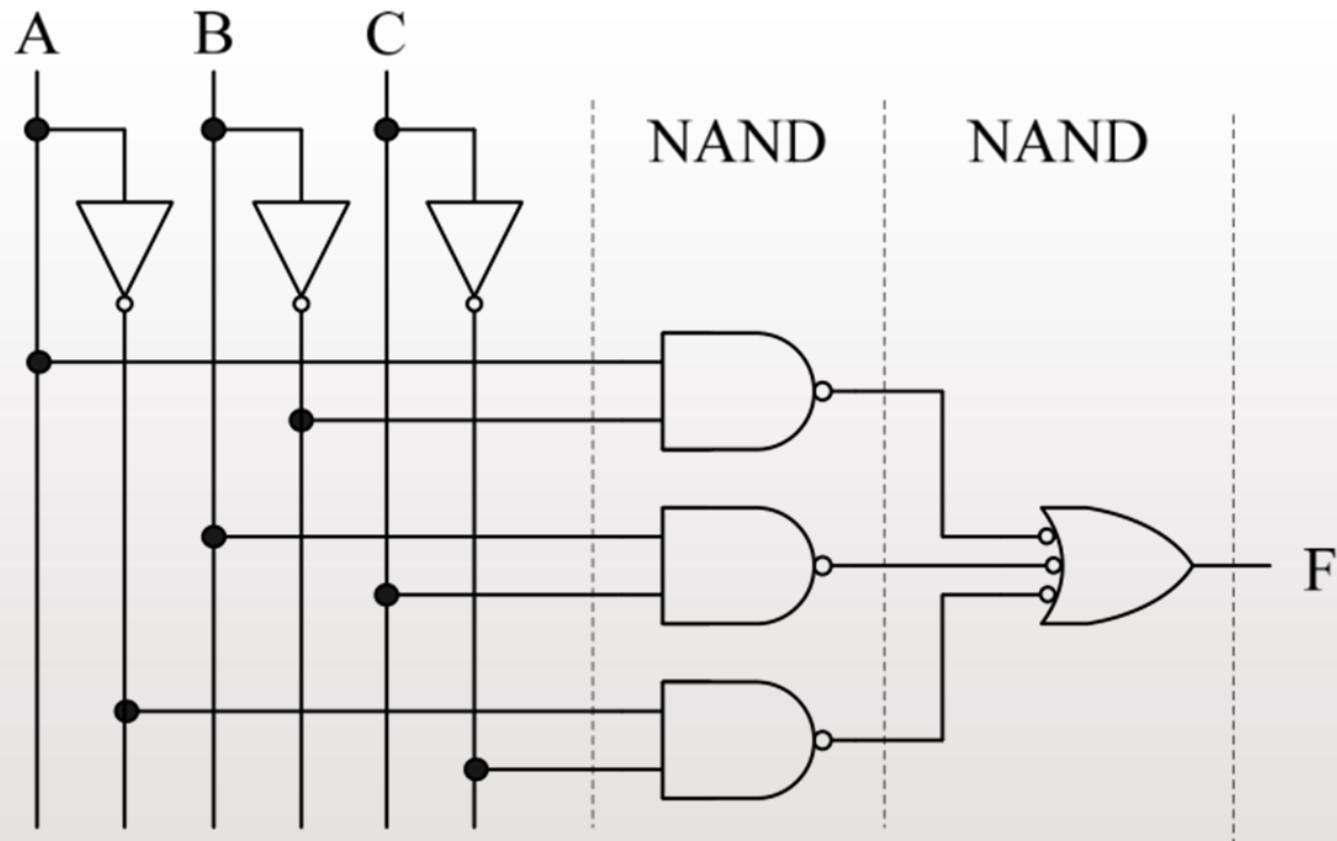

# OR-AND Configuration

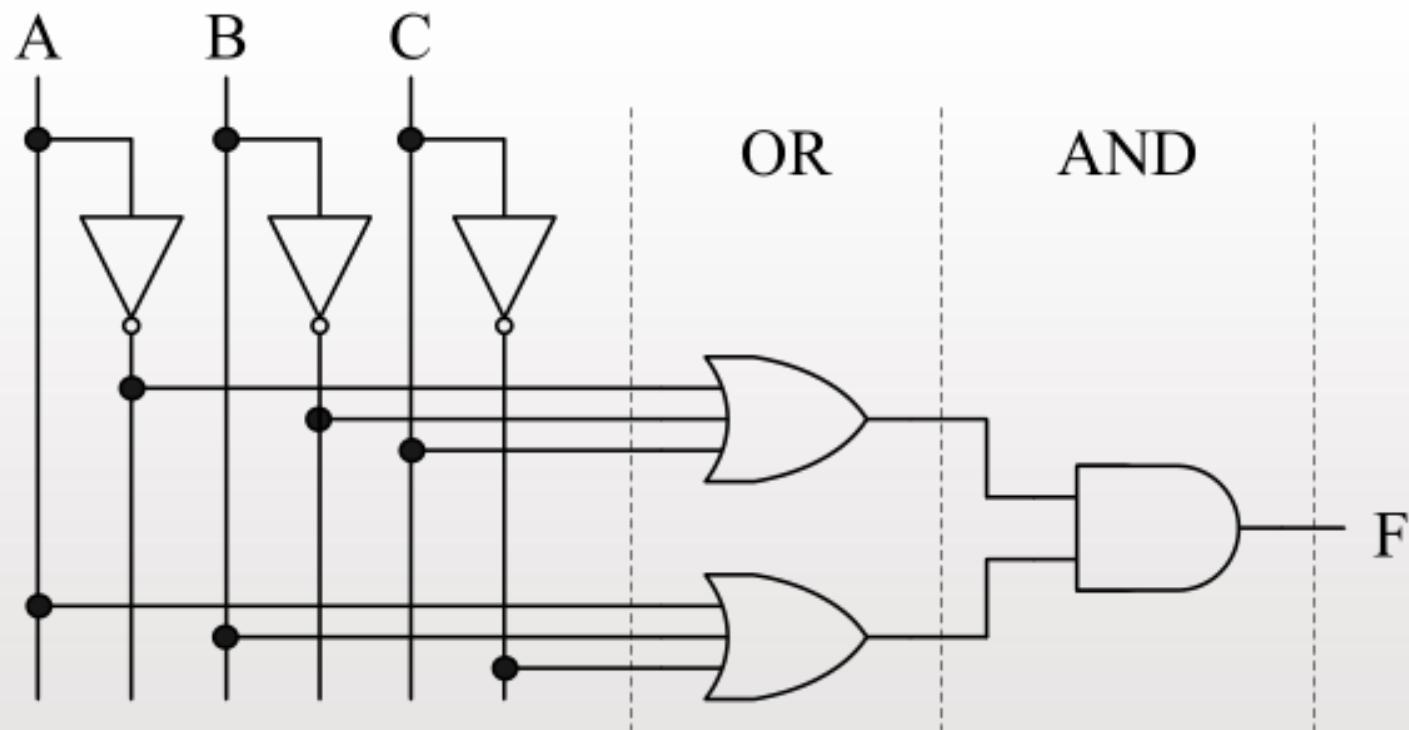

# NOR-NOR Configuration

