



**O N L I N E**

**L E A R N I N G**

# **Digital Electronics (SKEE1223)**

## **Combinational Logic Networks**


**Muhammad Arif Abd Rahim**

**Muhammad Mun'ím Ahmad Zabidi**

**Ab Hadi Abd Rahman**

**Faculty of Electrical Engineering**

# Adder Design using NANDs Only

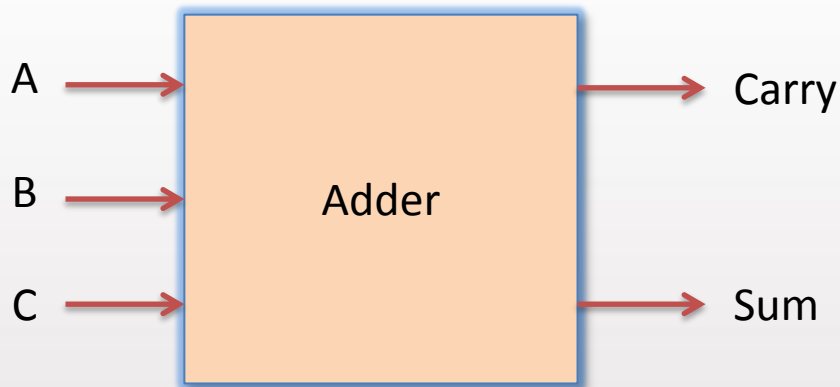

A	B	C	Carry	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1



# Adder Equations


		BC			
		00	01	11	10
A	0	0	0	1	0
	1	0	1	1	1

$$\text{Carry} = A.B + A.C + B.C$$


		BC			
		00	01	11	10
A	0	0	1	0	1
	1	1	0	1	0

$$\text{Sum} = \bar{A}.\bar{B}.C + \bar{A}.B.\bar{C} + A.\bar{B}.\bar{C} + A.B.C$$

# Adder Circuit

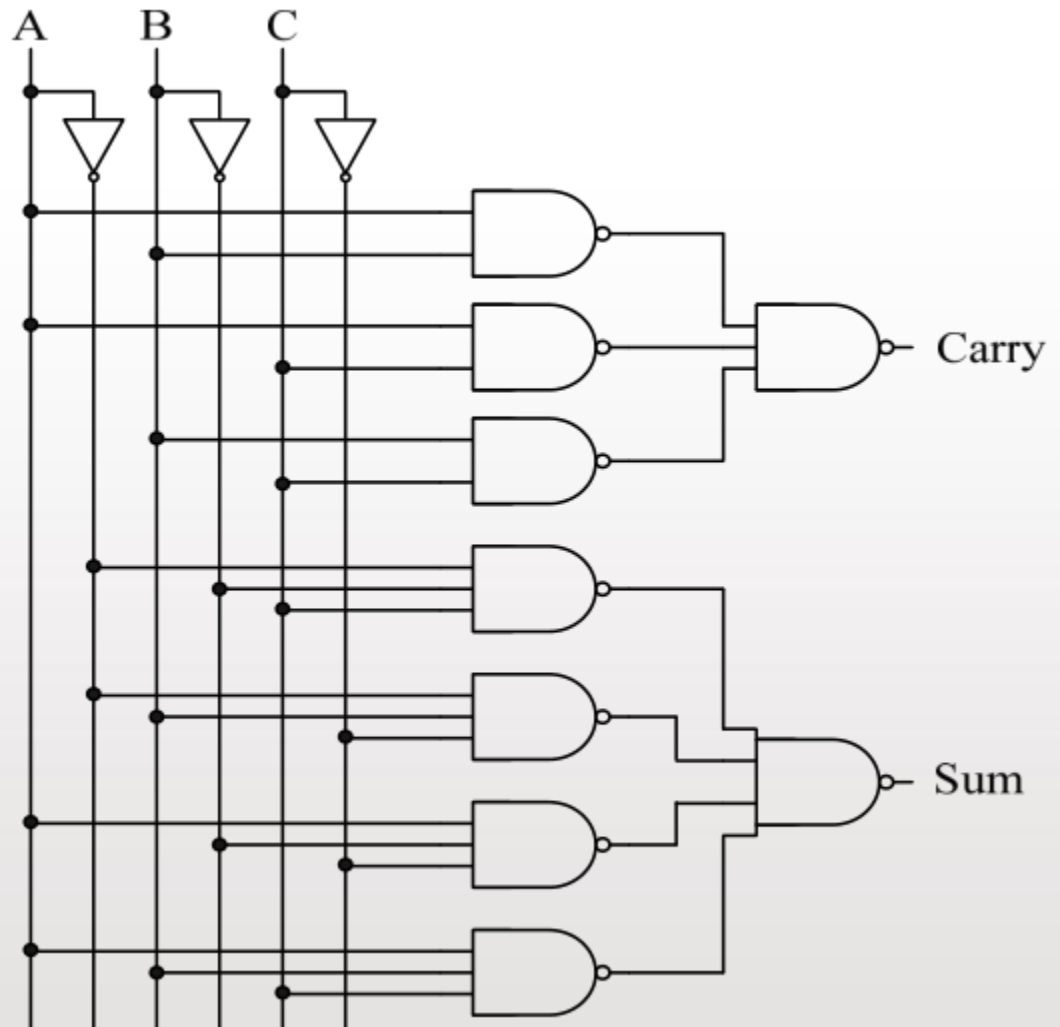

# Binary to Gray Code Converter

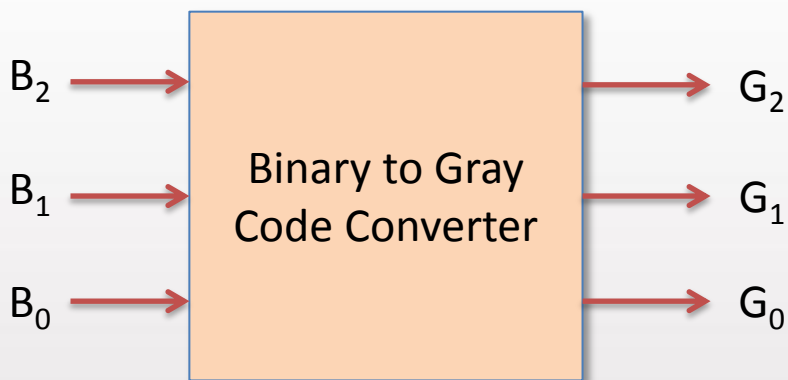

$B_2$	$B_1$	$B_0$	$G_2$	$G_1$	$G_0$
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	0	1	1
0	1	1	0	1	0
1	0	0	1	1	0
1	0	1	1	1	1
1	1	0	1	0	1
1	1	1	1	0	0

# Converter Equations

		$B_1B_0$			
		00	01	11	10
$B_2$	0	0	0	0	0
	1	1	1	1	1

$$G_2 = B_2$$

		$B_1B_0$			
		00	01	11	10
$B_2$	0	0	0	1	1
	1	1	1	0	0


$$G_1 = \overline{B_2} \cdot B_1 + B_2 \cdot \overline{B_1} = B_2 \oplus B_1$$

# Converter Equations

		$B_1B_0$			
		00	01	11	10
$B_2$	0	0	1	0	1
	1	0	1	0	1


$$G_0 = \overline{B_1} \cdot B_0 + B_1 \cdot \overline{B_0} = B_1 \oplus B_0$$

# Converter Circuit

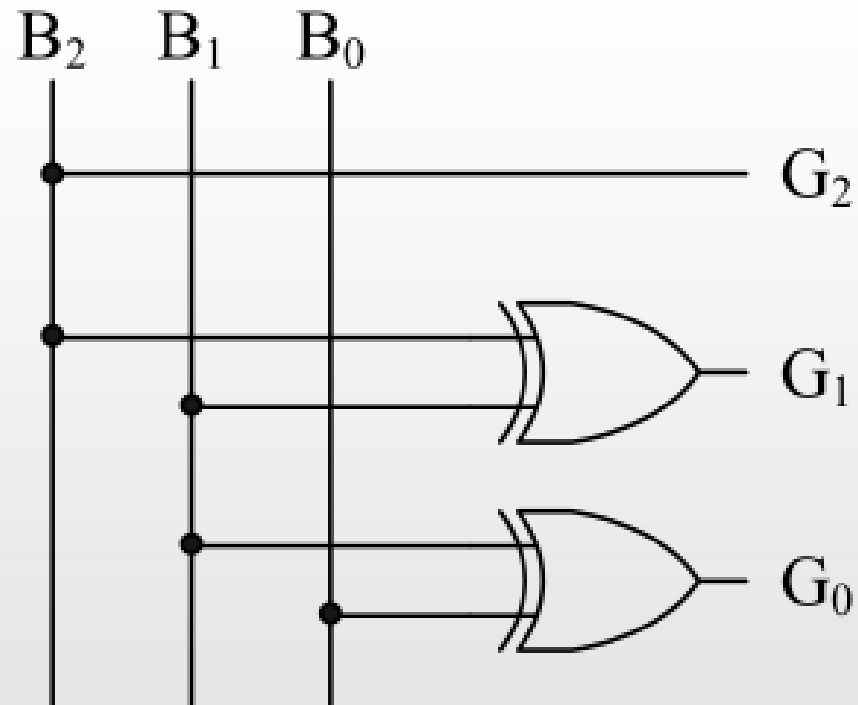



# Umbrella Controller

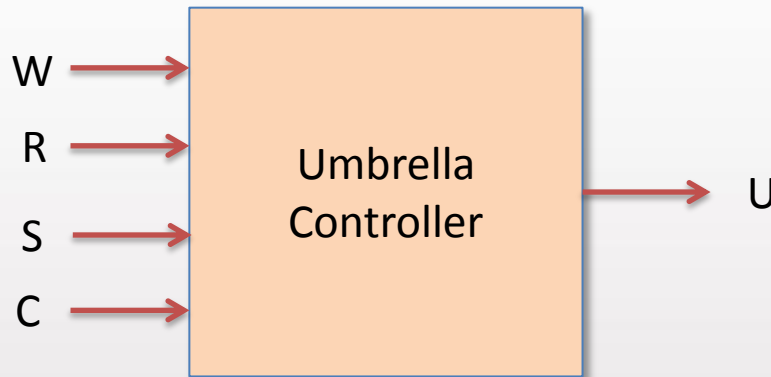

- A restaurant wants a smart umbrella system for its outdoor tables. It comprises of four sensors for
  - wind (W)
  - rain (R)
  - direct sunlight (S)
  - the presence of customers (C).



# Umbrella Sensor Specifications

---

Sensor	Conditions
W	0 if wind speed is less than 40 km/h 1 if wind speed is greater than 40 km/h
R	0 if no rain detected 1 if it is raining
S	0 if there is no direct sunlight 1 if there is a direct sunlight
C	0 if there is no customer 1 if one or more customers are present

---



# Umbrella Controller Specifications

---

## The umbrella is to open when:

- I If it is raining and the wind speed is less than 40 km/h, with or without any customers
- II If direct sunlight is detected when one or more customers are present at the table
- III If it is raining and the wind speed is greater than 40 km/h, with the presence of one or more customers



# Umbrella Controller SOP Equation

- Task: Design and implement the system in NOR-NOR configuration.
- Based on the given info, the equation for U is

$$U = \overline{W}.R + S.C + W.R.C$$

- To implement as NOR-NOR, U must be expressed in SOP form.

# Deriving the POS Equation

W	R	S	C	U
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1

W	R	S	C	U
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1

# Umbrella Controller POS Equation

		SC			
		00	01	11	10
WR	00	0 <sup>0</sup>	0 <sup>1</sup>	1 <sup>3</sup>	0 <sup>2</sup>
	01	1 <sup>4</sup>	1 <sup>5</sup>	1 <sup>7</sup>	1 <sup>6</sup>
	11	0 <sup>12</sup>	1 <sup>13</sup>	1 <sup>15</sup>	0 <sup>14</sup>
	10	0 <sup>8</sup>	0 <sup>9</sup>	1 <sup>11</sup>	0 <sup>10</sup>

$$U = (S + R)(\overline{W} + C)(R + C)$$

# Controller Circuit

