

# INDUSTRIAL ELECTRONICS

## DDPE 3103

### TOPIC 4



# FAMILY OF THYRISTOR

PROF MADYA DR MORINA ABDULLAH | ENCIK KAMARUDDIN TAWI

UTM KUALA LUMPUR CAMPUS
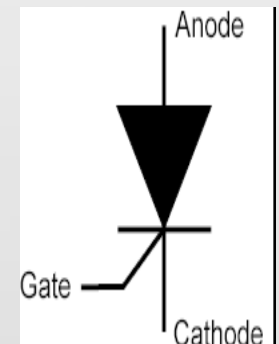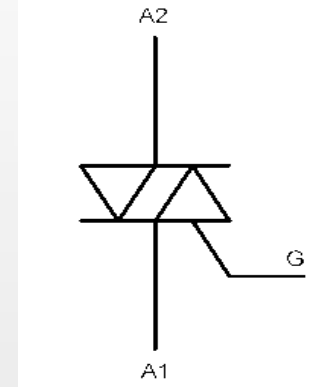
# FAMILY OF THYRISTOR



- ❑ A **thyristor** is a four layer three-terminal device.
- ❑ This device act as **an on – off** switch which is used to control output power of an electrical circuit.
- ❑ The main advantage of a thyristor over other electronics switches is that its can handle **large current** and can withstand **large voltage**.
- ❑ The three main thyristor will be discussed are the **Silicon Controlled Rectifier (SCR)**, **TRIAC** and **DIAC**.




# SILICON CONTROLLED RECTIFIER (SCR)

- SCR is a three **terminal four-layer pnpn device**.
- The three terminal are known as **anode (A), cathode (K), and gate (G)**.
- In **off** state, it has a very **high resistance**.
- In **on** state, there is a very **small resistance**.
- The SCR applications include : motor controls, time-delay circuits, heater controls and phase controls circuits.

# SYMBOL AND CONSTRUCTION OF THE SCR

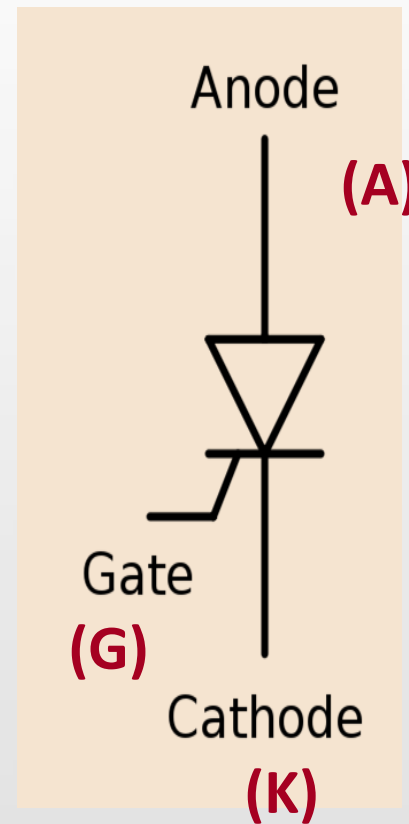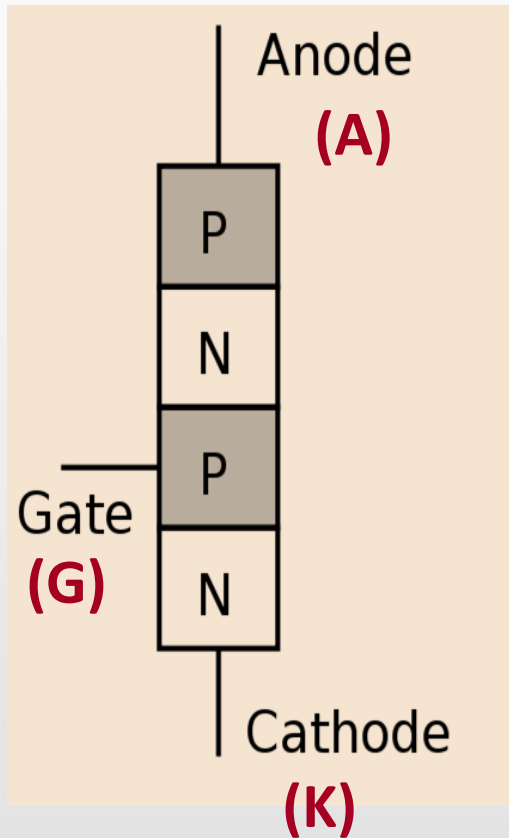


# SCR Equivalent Circuit

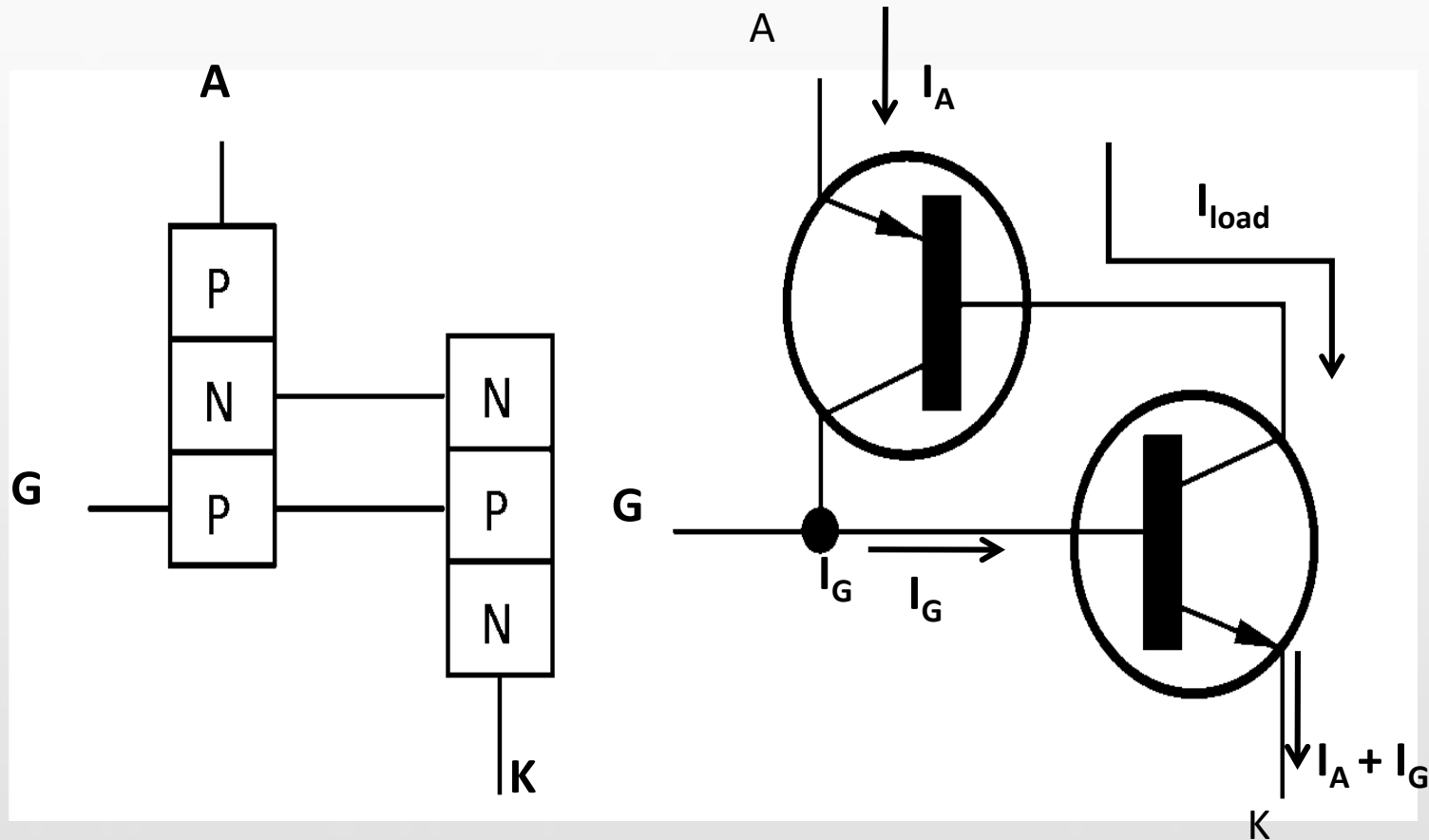


# V-I CHARACTERISTICS OF SCR



1	Breakover Voltage ( $V_{BO}$ )	Minimum forward voltage supply to SCR which makes it to start conducting.
2	Peak Reverse Voltage ( $V_{BR}$ )	The maximum reverse voltage apply to the SCR before breakdown.
3	Holding current ( $I_H$ )	The anode current at which SCR is turned OFF from ON condition. (if anode current less than the $I_H$ , the SCR will turn off)
4	Forward current ( $I_F$ )	It is the maximum anode current that an SCR is capable of passing without destruction.
5	Gate Trigger Current ( $I_{GT}$ )	Minimum gate current required to maintain the SCR in the on state
6	Gate Trigger Voltage ( $V_{GT}$ )	Gate voltage required to produce the gate trigger current

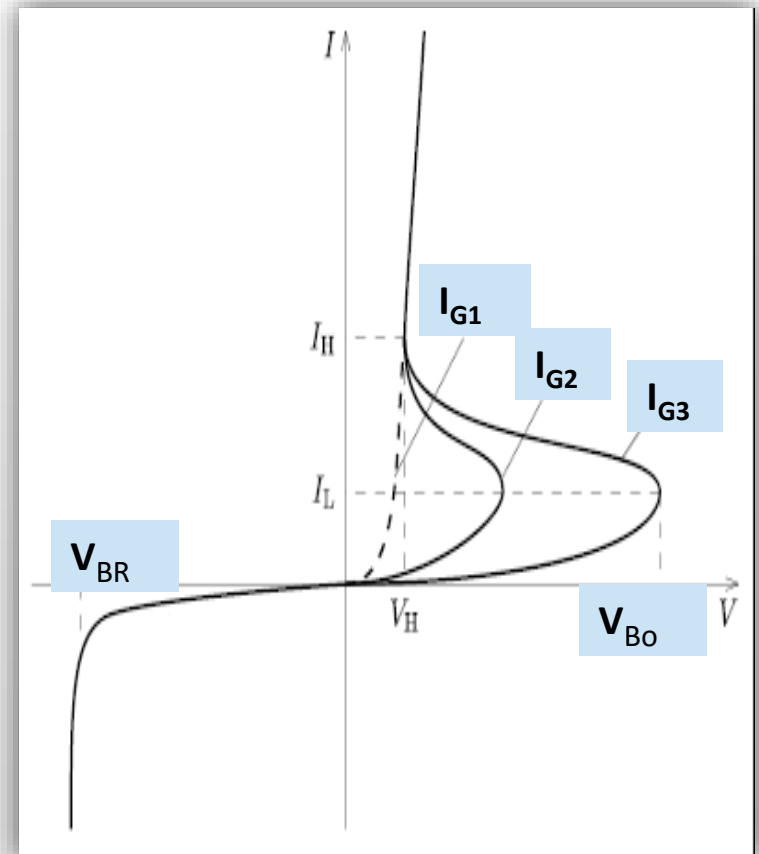



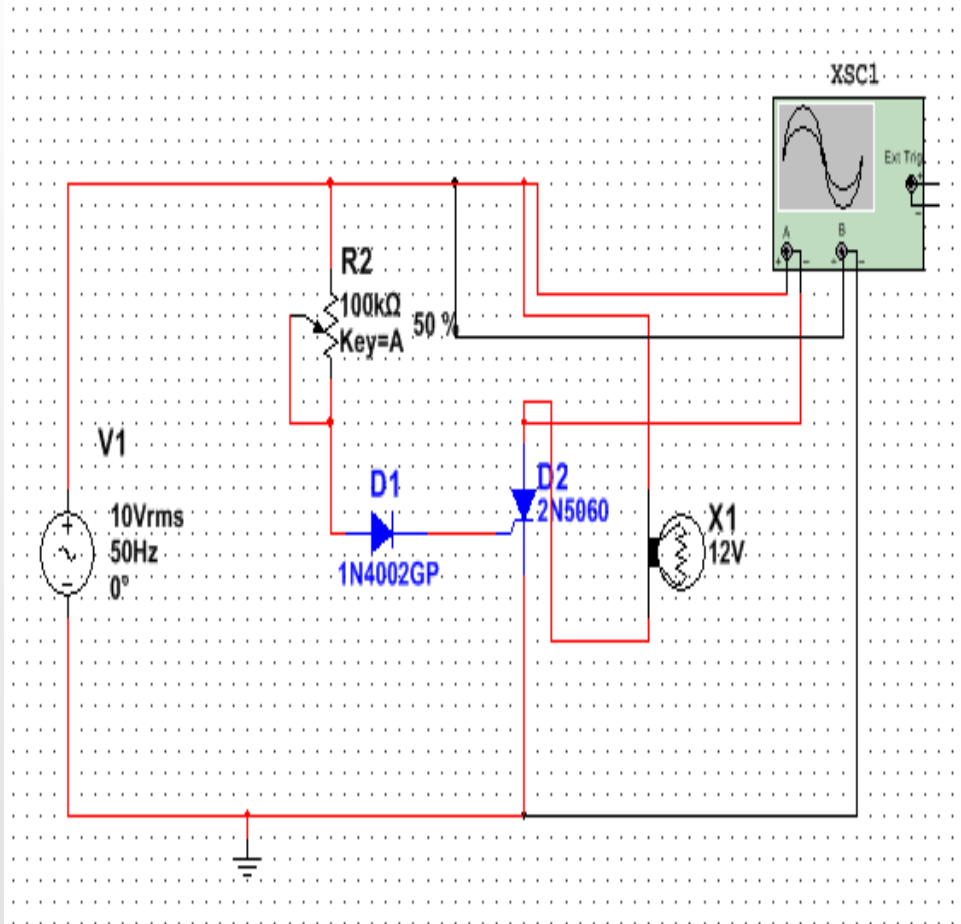
## Controlling the firing angle of the SCR by increasing and decreasing the variable resistor



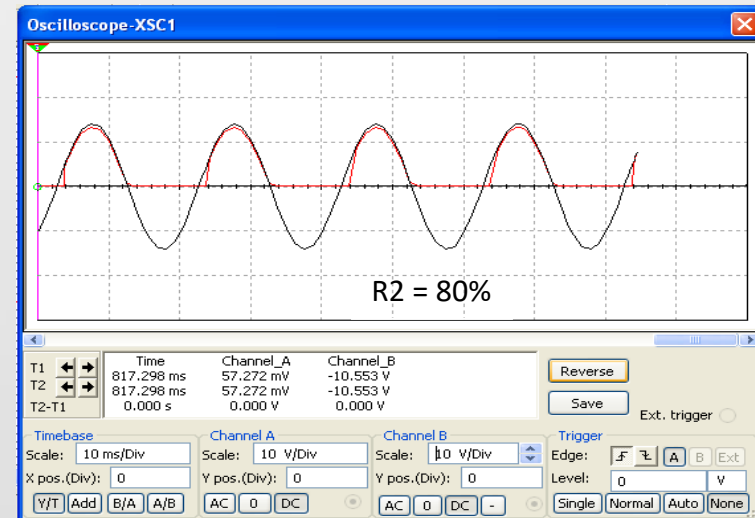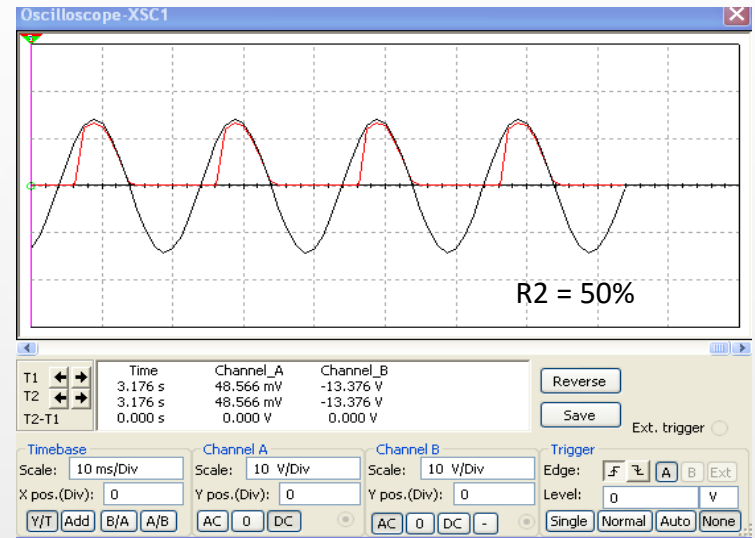The black waveform is the input voltage, while the red waveform is the voltage across the bulb.


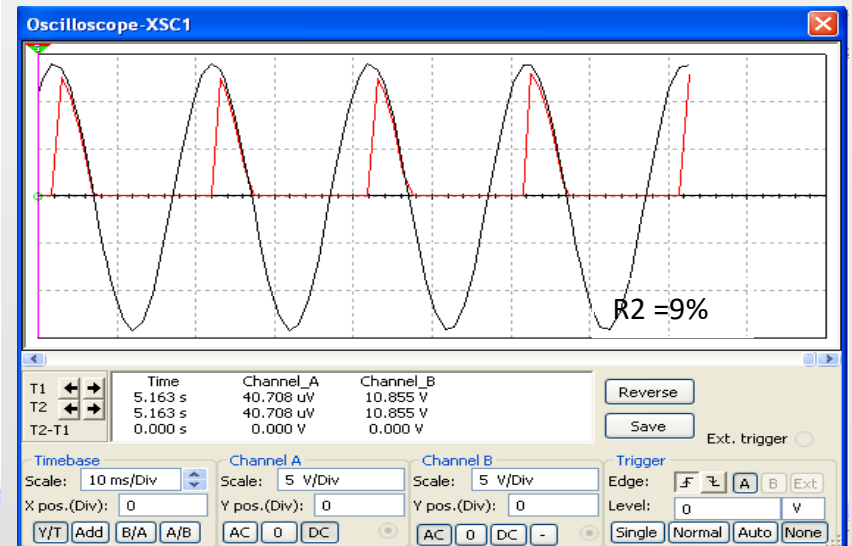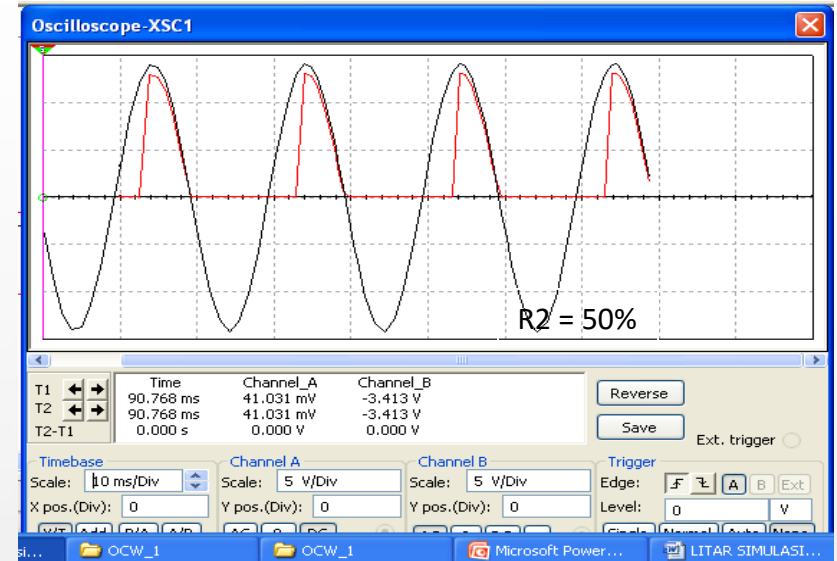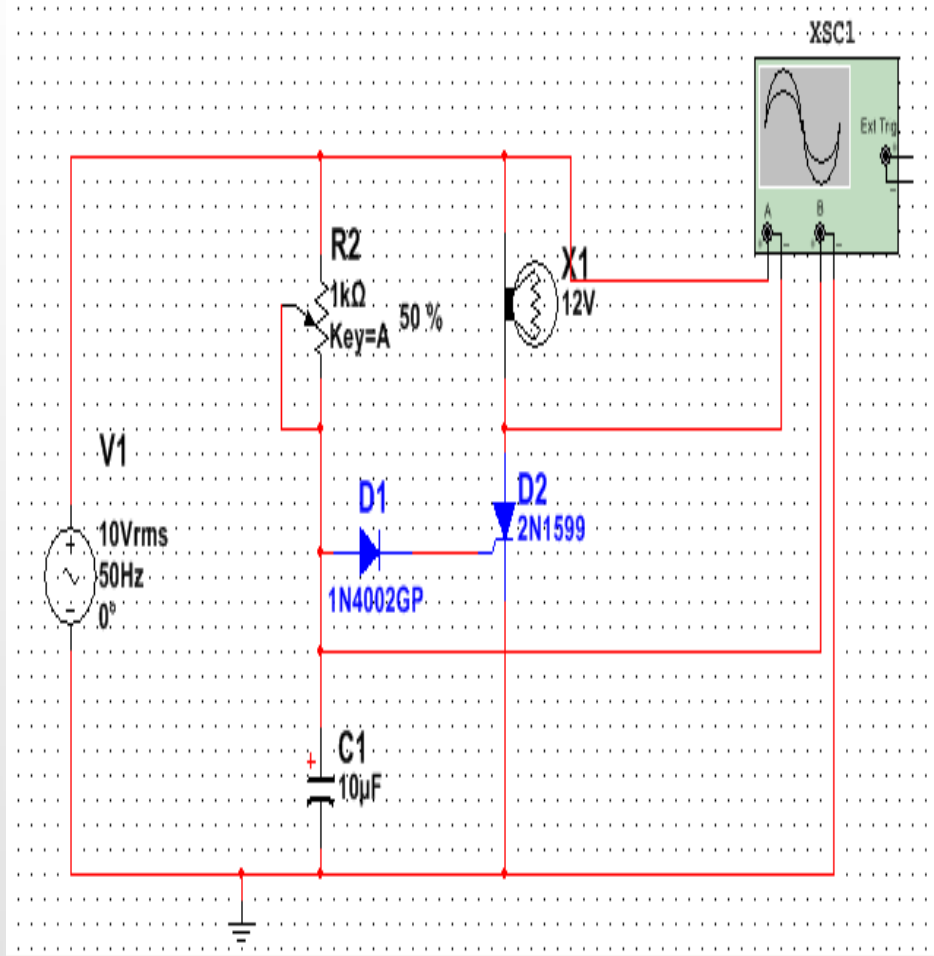
# Controlling the firing angle of the SCR with an RC circuit




The black waveform is the input voltage , while the **red waveform** is the voltage across the bulb.


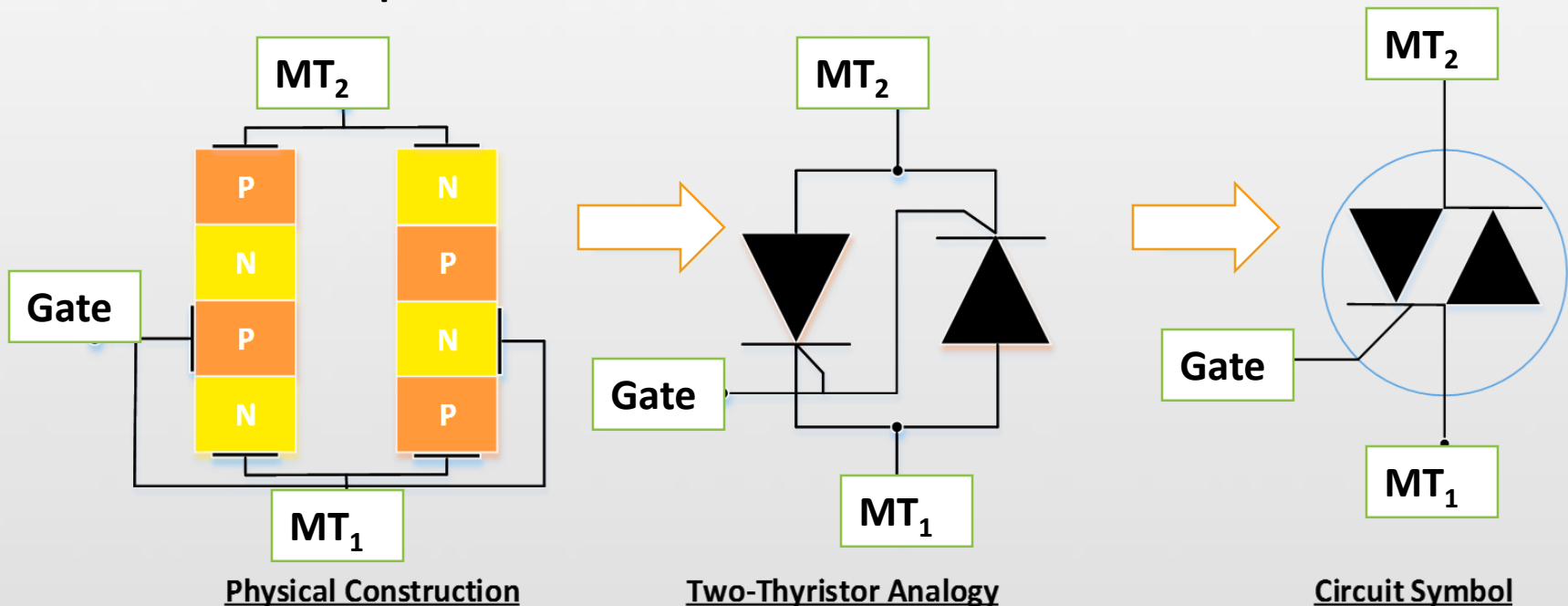
# TRIAC


- Triac is a three terminal semiconductor device for controlling current.
- Some applications of Triac are domestic light dimmers, electric fan speed control and small motor control


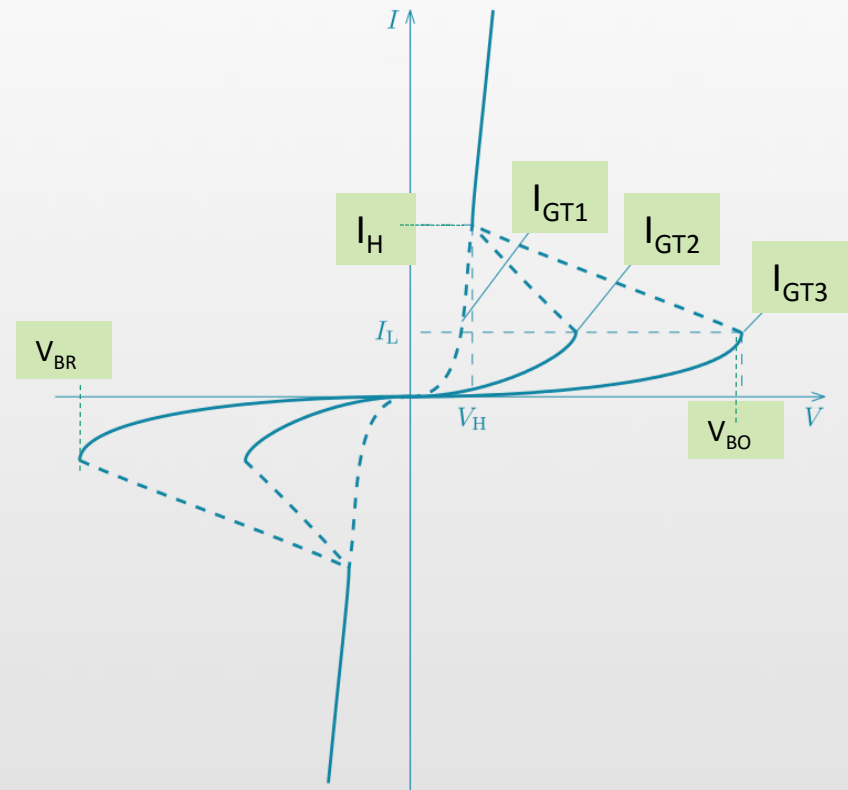
## Characteristic of a Triac


The voltage and current to be considered are:

- Forward breakover voltage
- Reverse breakover voltage.
- Holding current
- Gate voltage trigger
- Gate current trigger requirements.


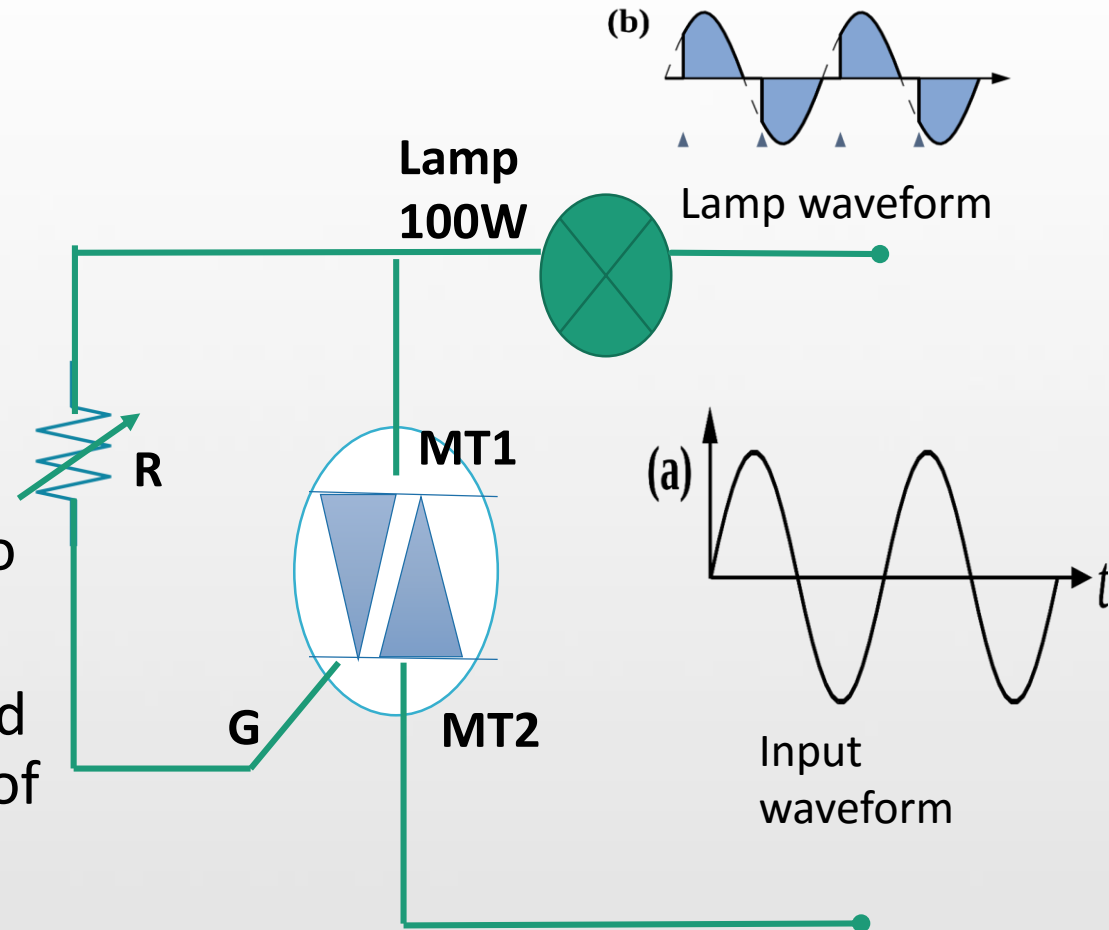
## An application of a Triac

- At input zero the Triac is cut off and the lamp will not light up.
- As the input voltage increases, a small gate current (a few mA) flowing through the gate (G) and the Triac starts to activate.
- The lamp will light up and give total output power of 100 watts.
- The brightness of the lamp can be controlled by varying the resistor R.




# DIAC

- A Diac is a bi-directional semiconductor switch that can conduct in both forward and reverse polarities once, the breakover voltage is reached.
- The name Diac comes from the words **Diode AC** switch.
- The Diac is widely used to assist the triggering of a Triac when used in AC switches.
- Application include in light dimmers such as those used in domestic lighting and are also widely used in starter circuits for fluorescent lamps.


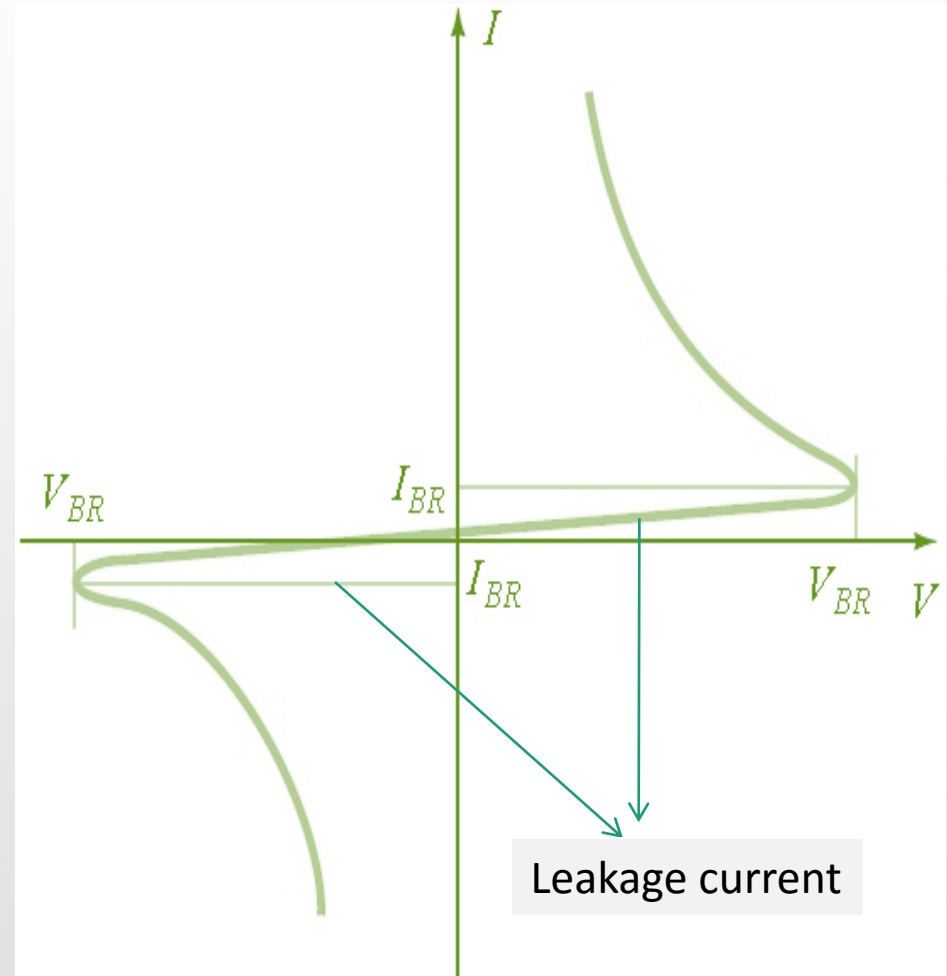
# Characateristic of a Diac

- As the voltage is increased from zero in either direction, a small amount of leakage current occurs, as shown in characteristic curve.
- When  $V_{BR}$  is reached in either direction, the Diac, starts to conduct and current will flow that produces very small internal resistance.


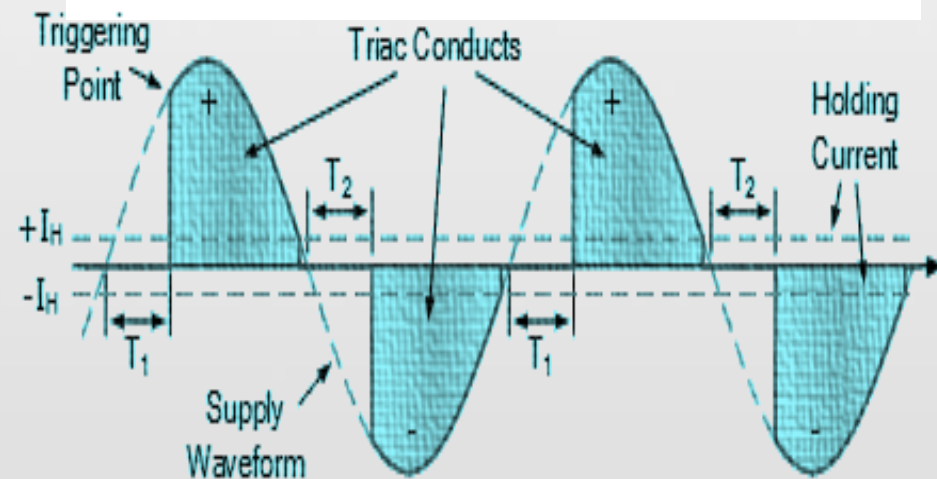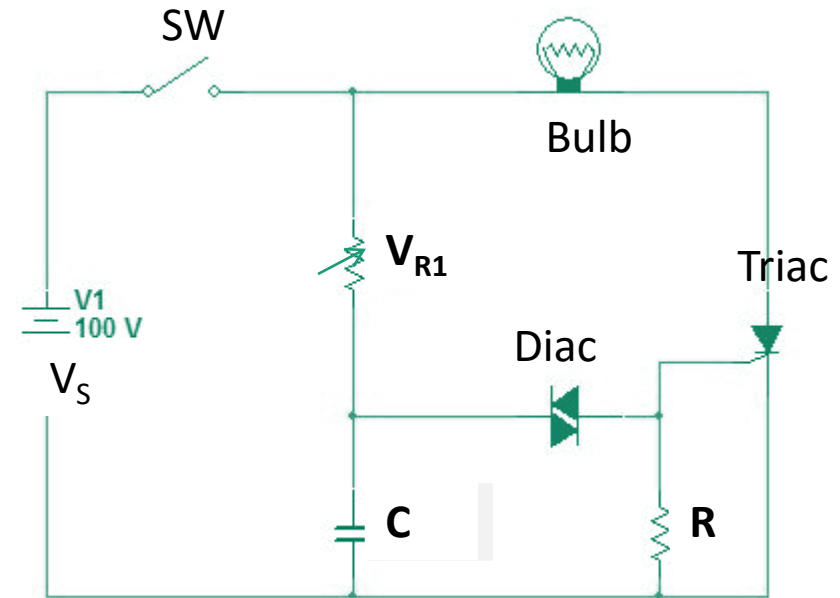
## Application Circuit of Triac and Diac

- When the switch SW is closed, the capacitor charging voltage reaches the breakover voltage of the Diac (about 30 V), the Diac starts conducting and trigger the Triac.
- The phase angle at which the Triac is triggered can be varied using  $V_{R1}$ , which controls the charging rate of the capacitor.
- The bulb will light up depends on the voltage supplied to it.



# References

1. Electronic Devices and Circuit Theory , Robert L. Boylestad & Louis Nashelsky , 9<sup>th</sup> Edition, 2006
2. Electronic Devices, Thomas L. Floyd, 5<sup>th</sup> Edition, 1999
3. Wikimedia Commons for images
4. Multisim Version 13.0