

INDUSTRIAL ELECTRONICS

DDPE 3103

TOPIC 5




RELAXATION OSCILLATOR

**PROF MADYA DR MORINA ABDULLAH | ENCIK KAMARUDDIN TAWI UTM
KUALA LUMPUR CAMPUS**

RELAXATION OSCILLATOR


- A **relaxation oscillator** is a circuit that produces output which repeatedly alternates between two states with a period that depends on the charging of a capacitor.
- Two devices commonly used as relaxation oscillator is the Unijunction transistor (**UJT**) and Programmable Unijunction transistor (**PUT**).
- **UJT** and **PUT** circuit generates pulses.

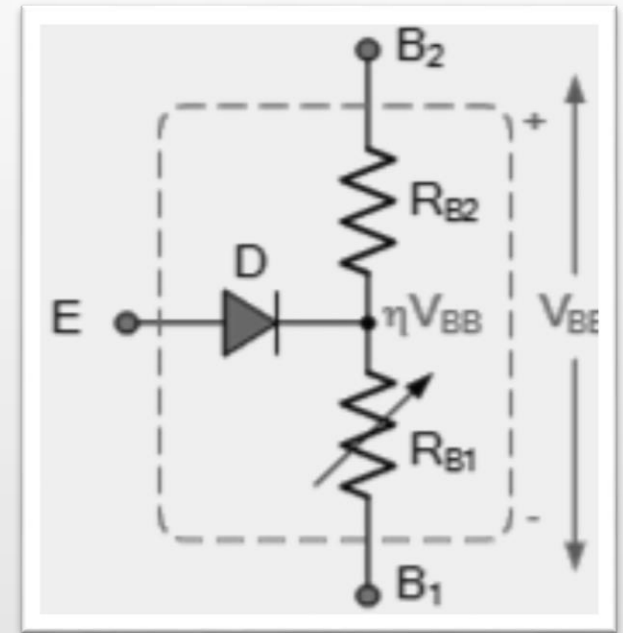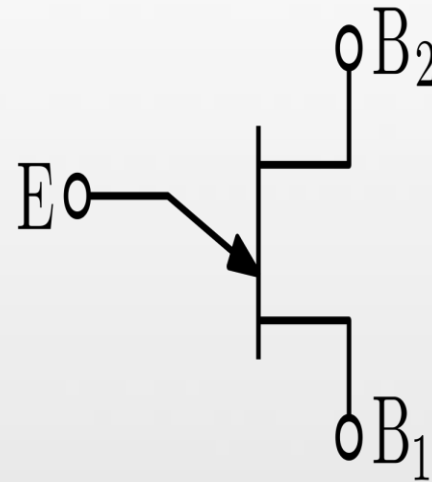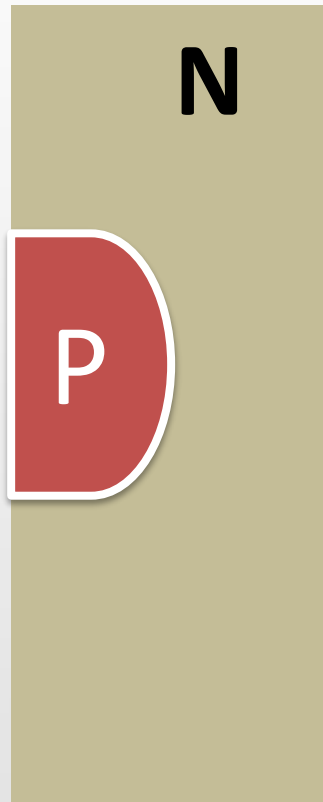UNIUNTION TRANSISTOR SYMBOL AND CONSTRUCTION




Three terminal : Base₁ (B₁),
 Base₂ (B₂) and Emitter (E)

Characteristic of a UJT

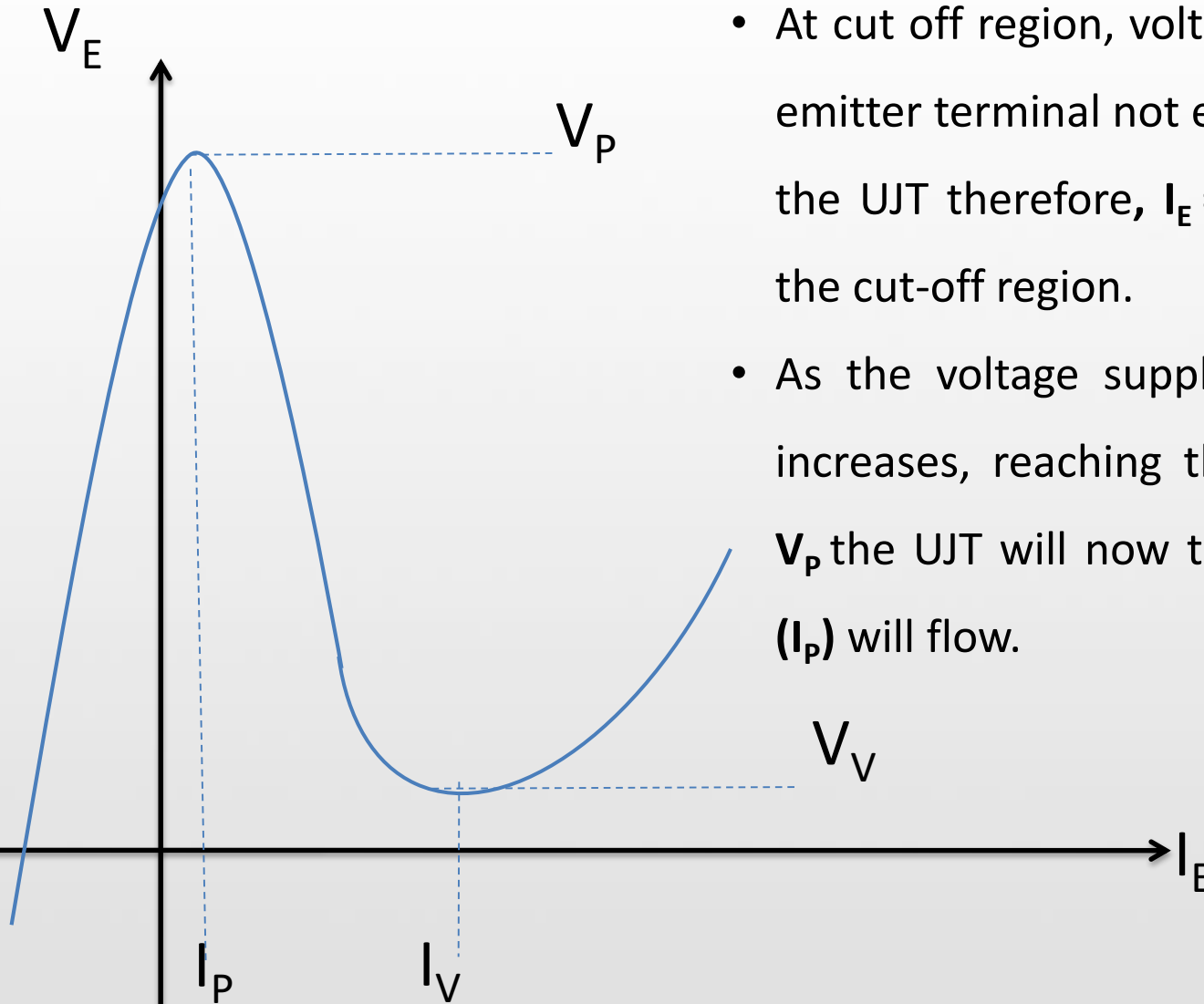

- At cut off region, voltage supply to the emitter terminal not enough to turn on the UJT therefore, $I_E = 0$ and UJT is in the cut-off region.
- As the voltage supply across emitter increases, reaching the **peak voltage**, V_P the UJT will now turn on and I_{peak} , (I_P) will flow.

Characteristic of a UJT

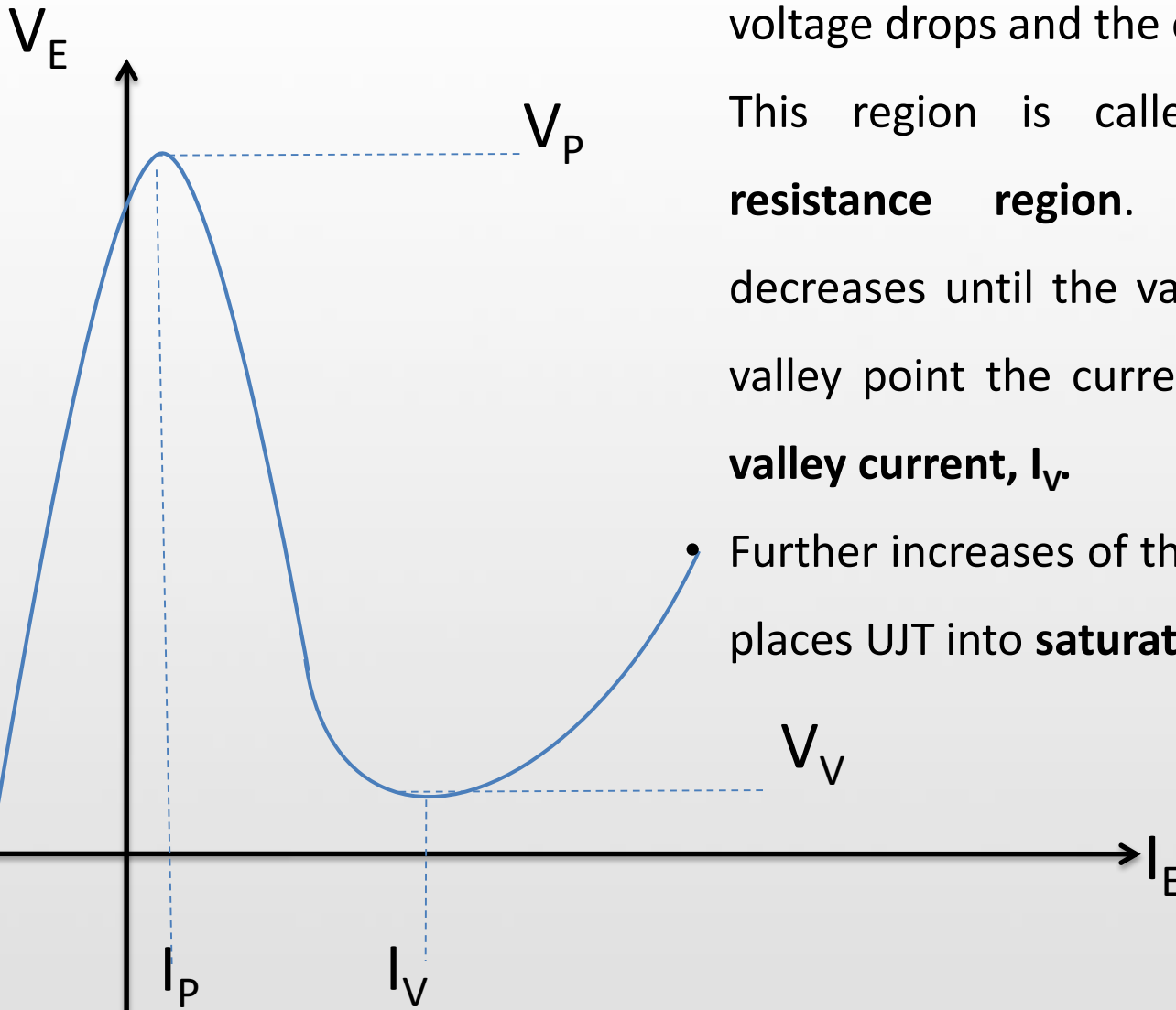


Between V_P to the **valley point (V_V)** the voltage drops and the current increases.

This region is called the **negative resistance region**. The voltage decreases until the value of V_V .

At the valley point the current produce is the **valley current, I_V** .


Further increases of the emitter current, places UJT into **saturation region**.

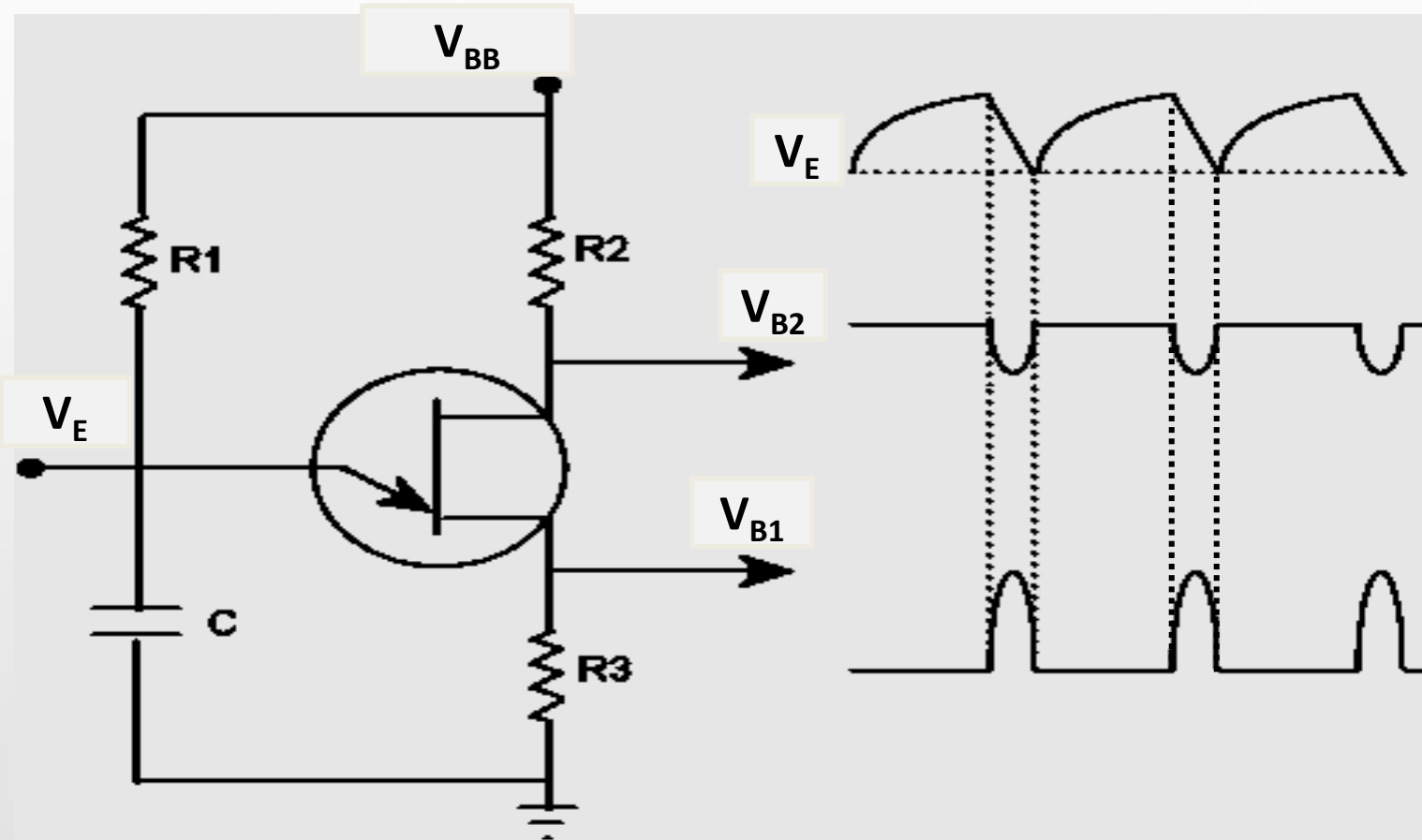Unijunction transistor as relaxation oscillator





Programmable Unijunction Transistor (PUT)

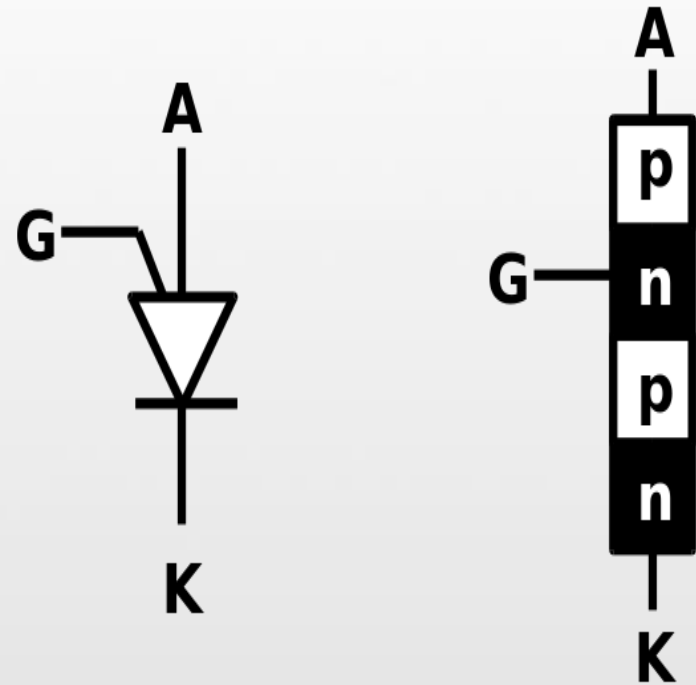- In a UJT, the parameters such as V_p , η and etc are fixed and cannot be change.
- However, for a PUT these parameters can be programmed with the help of two external resistor.



PUT AS RELAXATION OSCILLATOR

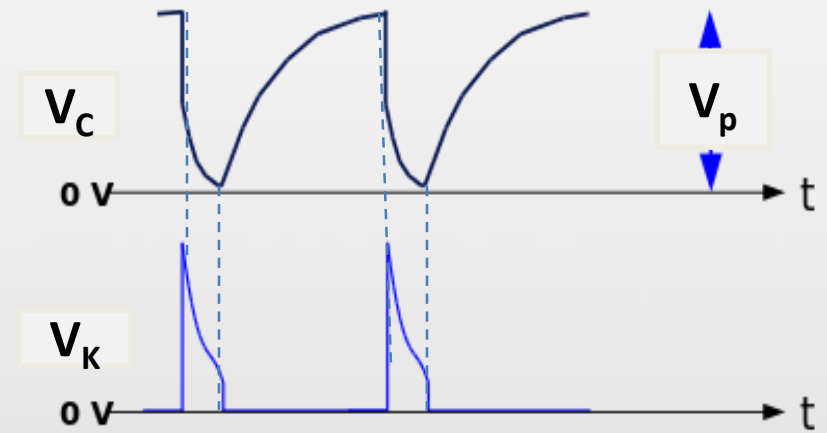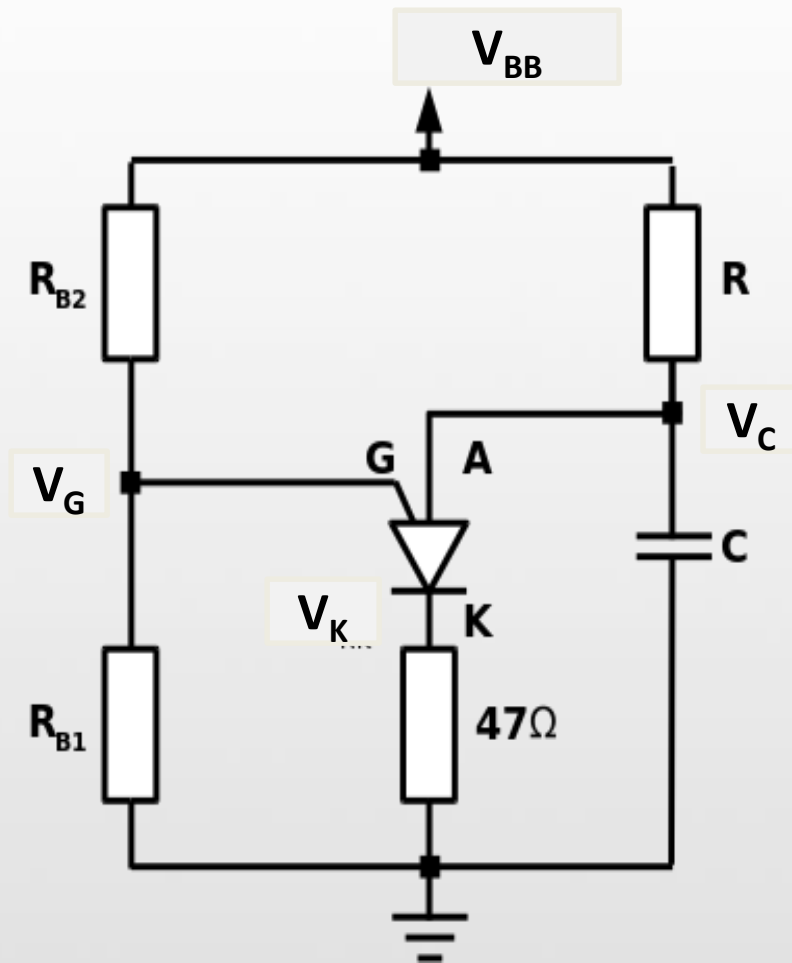

References

1. Electronic Devices and Circuit Theory , Robert L. Boylestad & Louis Nashelsky , 9th Edition, 2006
2. Electronic Devices, Thomas L. Floyd, 5th Edition, 1999
3. Wikimedia Commons for images