

SEE 3243/4243

Digital System

Lecturers :

Muhammad Mun'im Ahmad Zabidi


Muhammad Nadzir Marsono

Kamal Khalil

***Week 3: Logic Design Using MSI Components
& Memory***



Multiplexers/Selectors

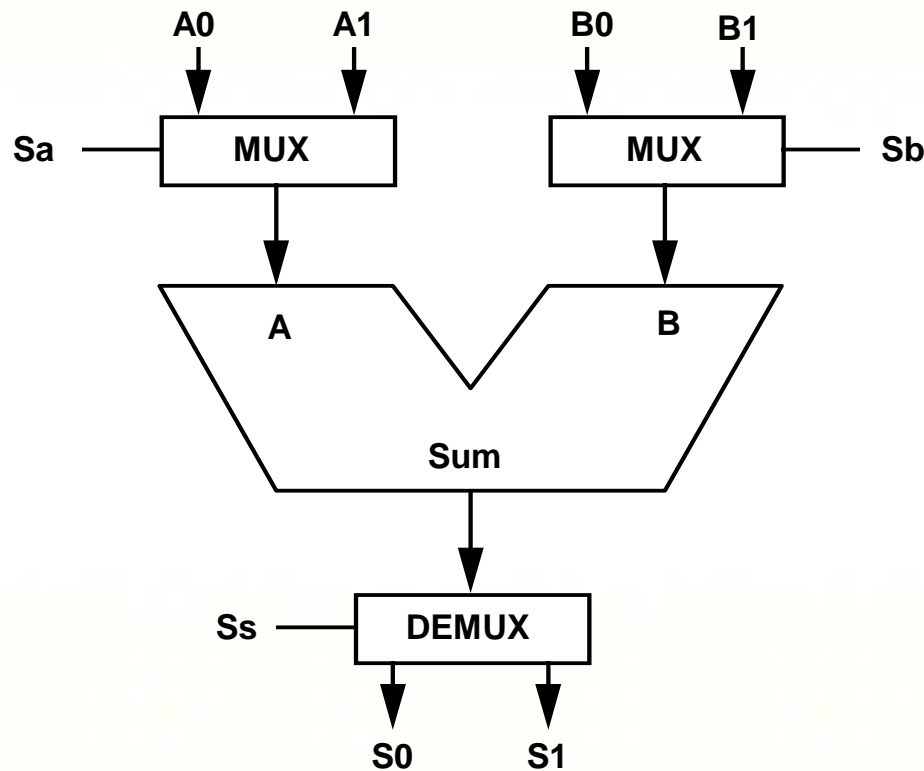

Multiple input sources

Multiple output destinations

Multiplexers/Selectors: General Concept

- 2^n data inputs, n control inputs, 1 output
- used to connect 2^n points to a single point
- control signal pattern form binary index of input connected to output

$$Z = A' I_0 + A I_1$$

Functional form


Logical form

A	Z
0	I_0
1	I_1


I_1	I_0	A	Z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

*Two alternative forms
for a 2:1 Mux Truth Table*


Multiplexers/Selectors

 

$$Y = A' I_0 + A I_1$$

 

 
$$Y = A' B' I_0 + A' B I_1 + A B' I_2 + A B I_3$$



$$Y = A' B' C' I_0 + A' B' C I_1 + A' B C' I_2 + A' B C I_3 + A B' C' I_4 + A B' C I_5 + A B C' I_6 + A B C I_7$$


Multiplexer/Selector: Expansion

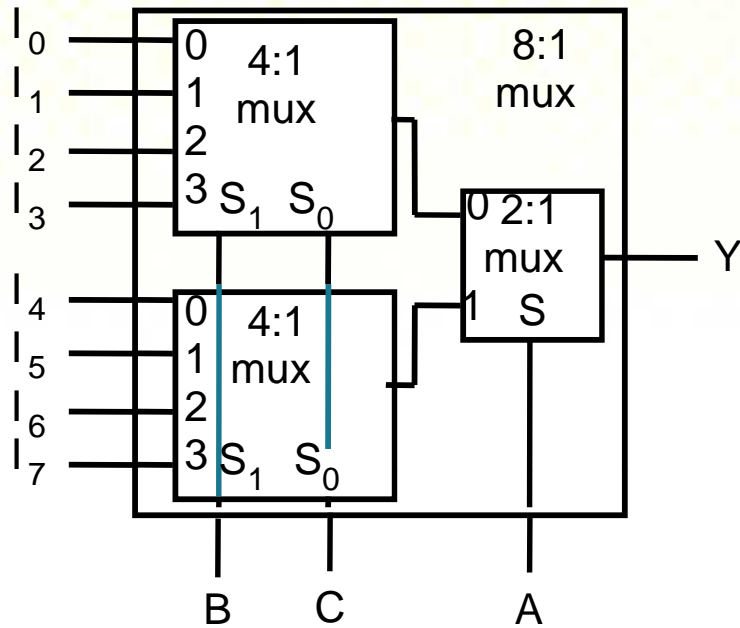

Alternative 8:1 Mux Implementation

Control signals B and C simultaneously choose one of I_0 - I_3 and I_4 - I_7

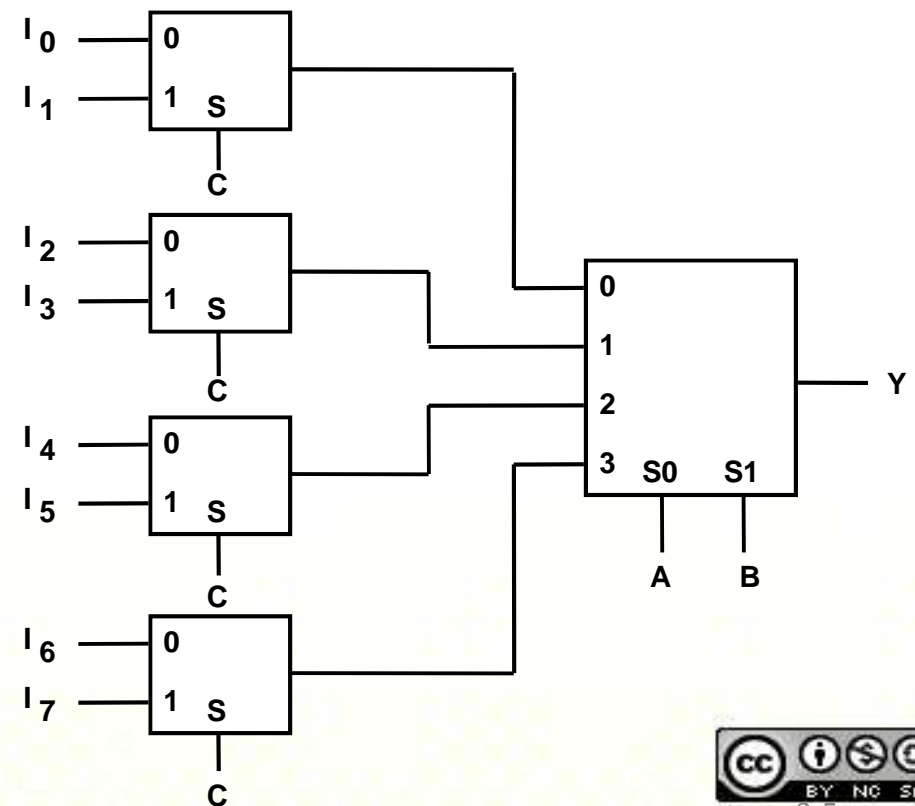Control signal A chooses which of the upper or lower MUX's output to gate to Y




Multiplexer/Selector

$2^{n-1} : 1$ multiplexer can implement any function of n variables


$n-1$ control variables; remaining variable is a data input to the mux

 Example:

$$\begin{aligned}
 F(A,B,C) &= m_0 + m_2 + m_6 + m_7 \\
 &= A' B' C' + A' B C' + A B C' + A B C \\
 &= A' B' (C') + A' B (C') + A B' (0) + A B (1)
 \end{aligned}$$




A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

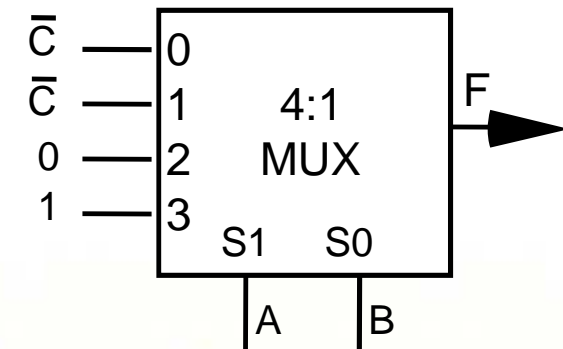


Decoders

- General decoder

 


- Typically n inputs, 2^n outputs
 - 2-to-4, 3-to-8, 4-to-16, etc
- Control inputs (called select S) represent Binary index of output to which the input is connected
- Data input usually called "enable" (G)

Binary 2-to-4 decoder

 


Inputs			Outputs			
EN	I1	I0	Y3	Y2	Y1	Y0
0	x	x	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0

 


Note "x" (don't care) notation.


Complete 74x139 Decoder

 

A is LSB selector

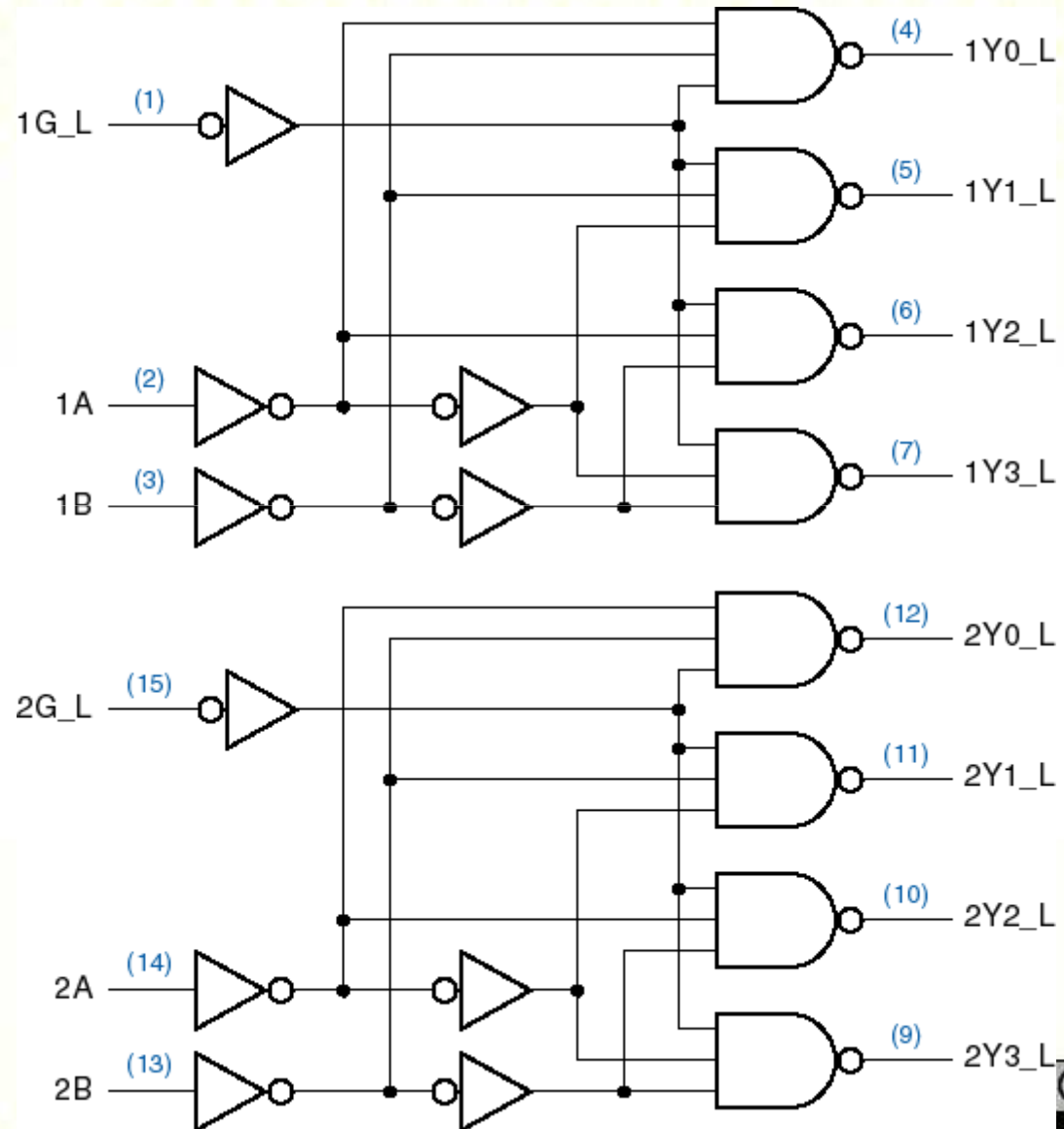


74x138 3-to-8-decoder symbol

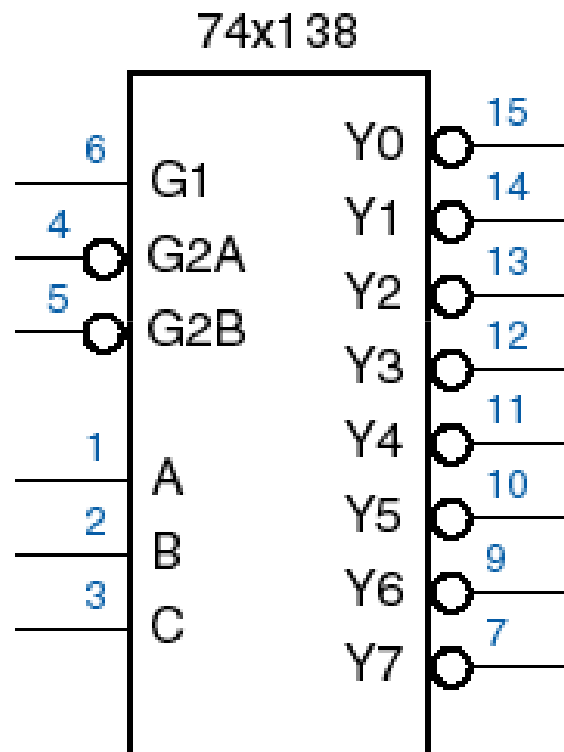


A is LSB selector

Decoder cascading

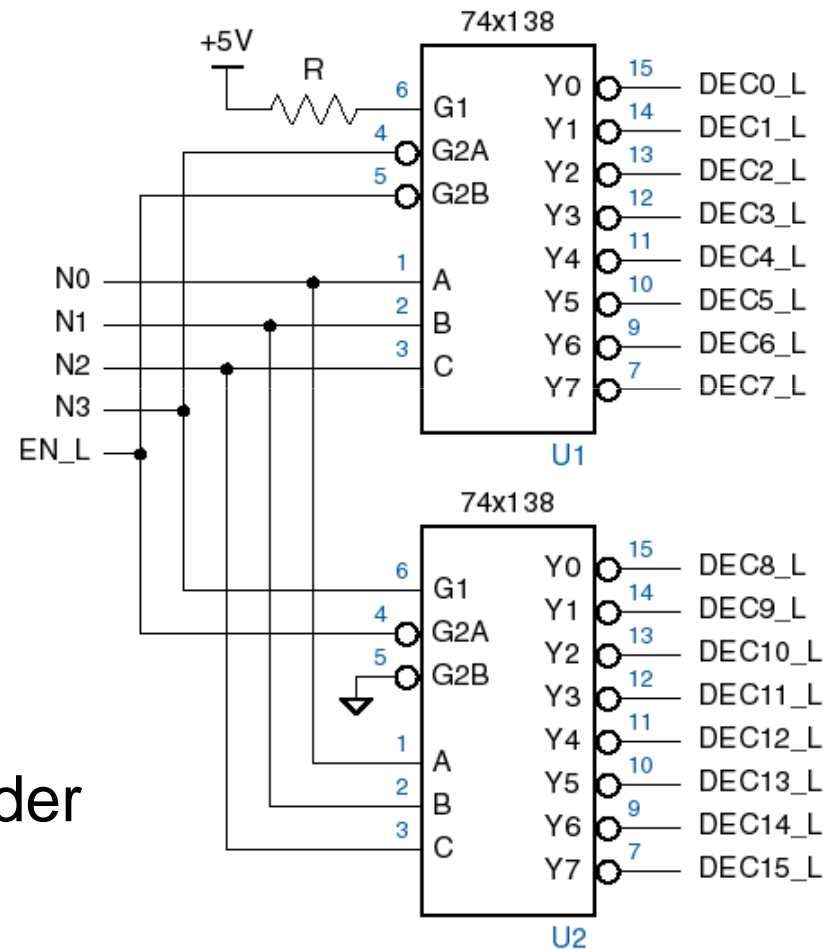

4-to-16 decoder

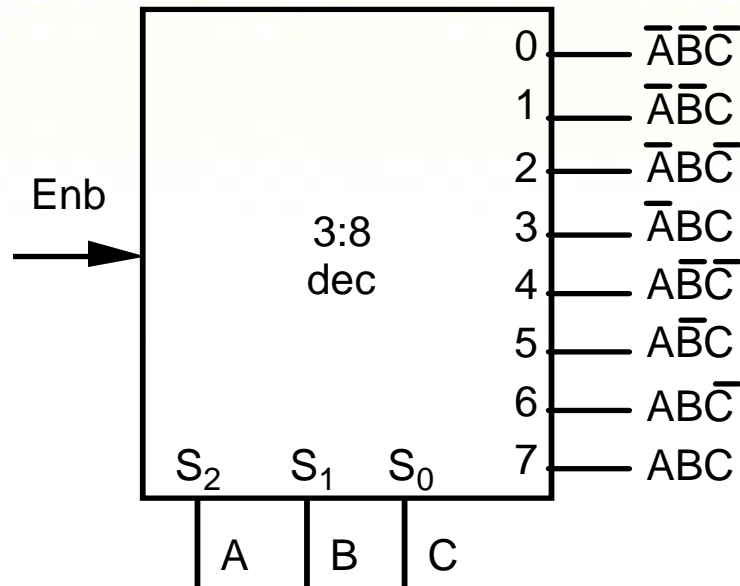Decoder/Demultiplexer: Logic Building Block



Decoder Generates Appropriate
Minterm based on Control Signals


Example Function:

$$F1 = A' B C' D + A' B' C D + A B C D$$


$$F2 = A B C' D' + A B C$$

$$F3 = (A' + B' + C' + D')$$



Decoder/Demultiplexer:

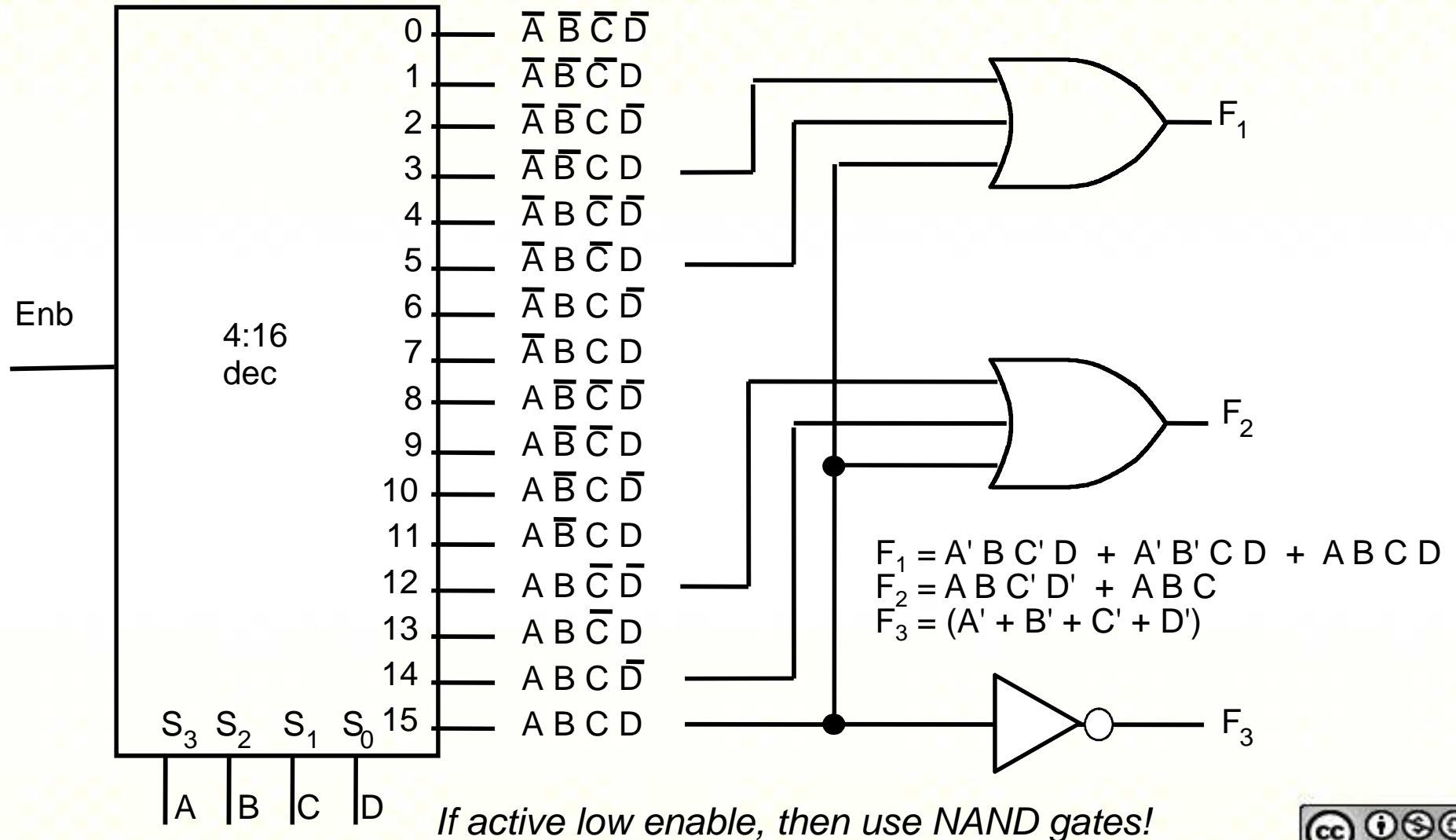

Need priority in most applications

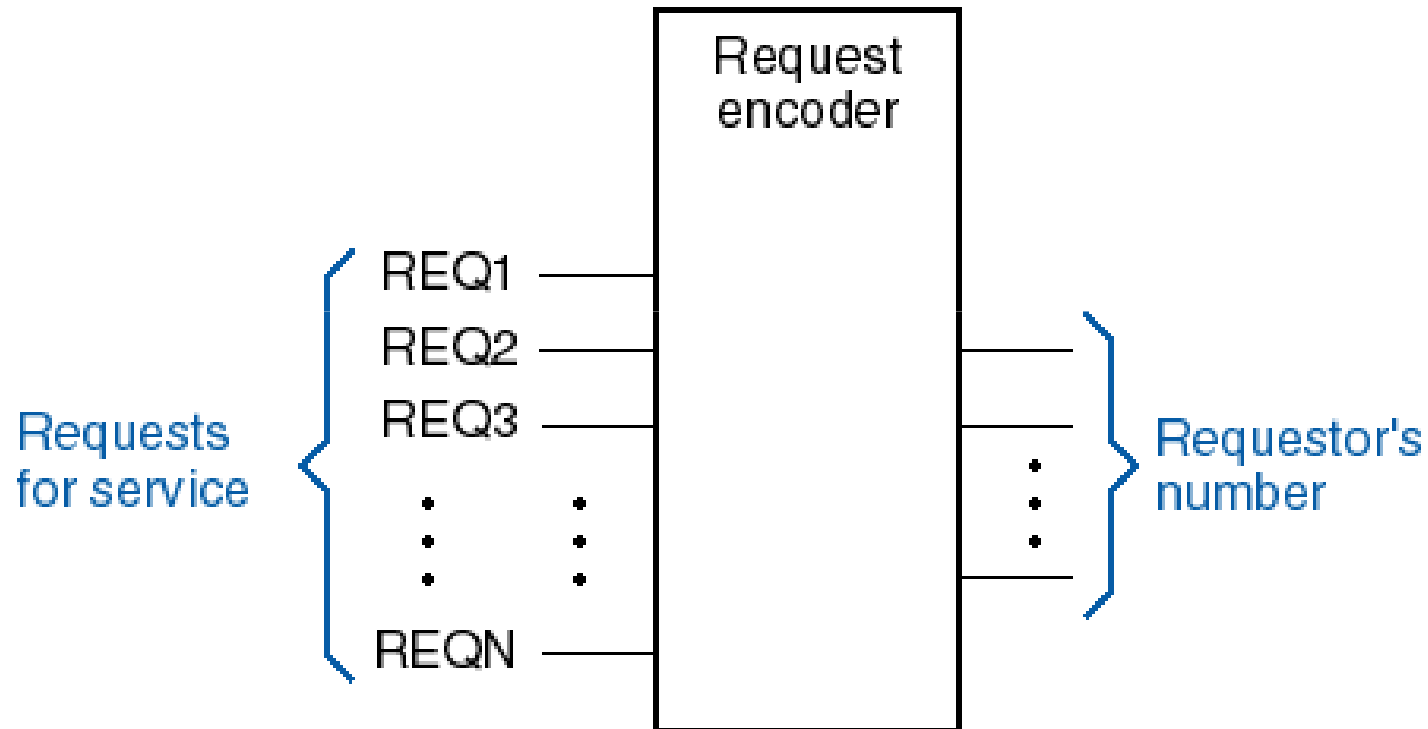

74x148 8-input priority encoder

  

- Active-low I/O
- Enable Input
- “Got Something”
Enable Output

Priority-encoder logic equations

$$H7 = I7$$

$$H6 = I6 \cdot I7'$$

$$H5 = I5 \cdot I6' \cdot I7'$$

...

$$H0 = I0 \cdot I1' \cdot I2' \cdot I3' \cdot I4' \cdot I5' \cdot I6' \cdot I7'$$

$$A2 = H4 + H5 + H6 + H7$$


$$A1 = H2 + H3 + H6 + H7$$

$$A0 = H1 + H3 + H5 + H7$$

$$\begin{aligned} \text{IDLE} &= (I0 + I1 + I2 + I3 + I4 + I5 + I6 + I7)' \\ &= I0' \cdot I1' \cdot I2' \cdot I3' \cdot I4' \cdot I5' \cdot I6' \cdot I7' \end{aligned}$$

Multi-input XOR


- Sum modulo 2
- Parity computation

 

- Used to generate and check parity bits in computer systems.
 - Detects any single-bit error

Parity tree

- Faster with balanced tree structure

 


Tri-State

- Logic States: "0", "1"
- Don't Care/Don't Know State: "X" (must be some value in real circuit!)
- Third State: "Z" — high impedance resistance, no connection
- Tri-state gates:
 - output values are "0", "1", and "Z"
 - additional input: output enable (OE)
- Can tie multiple outputs together, if at most one at a time is driven.

A	0	1
X	Z	Z
0	1	0
1	1	1


Tri-State

 Using tri-state gates to implement an economical multiplexer:



- When S is asserted high
 - I_1 is connected to F
- When S is driven low
 - I_0 is connected to F
- This is essentially a 2:1 Mux

8:1 Multiplexer Using Tri-States

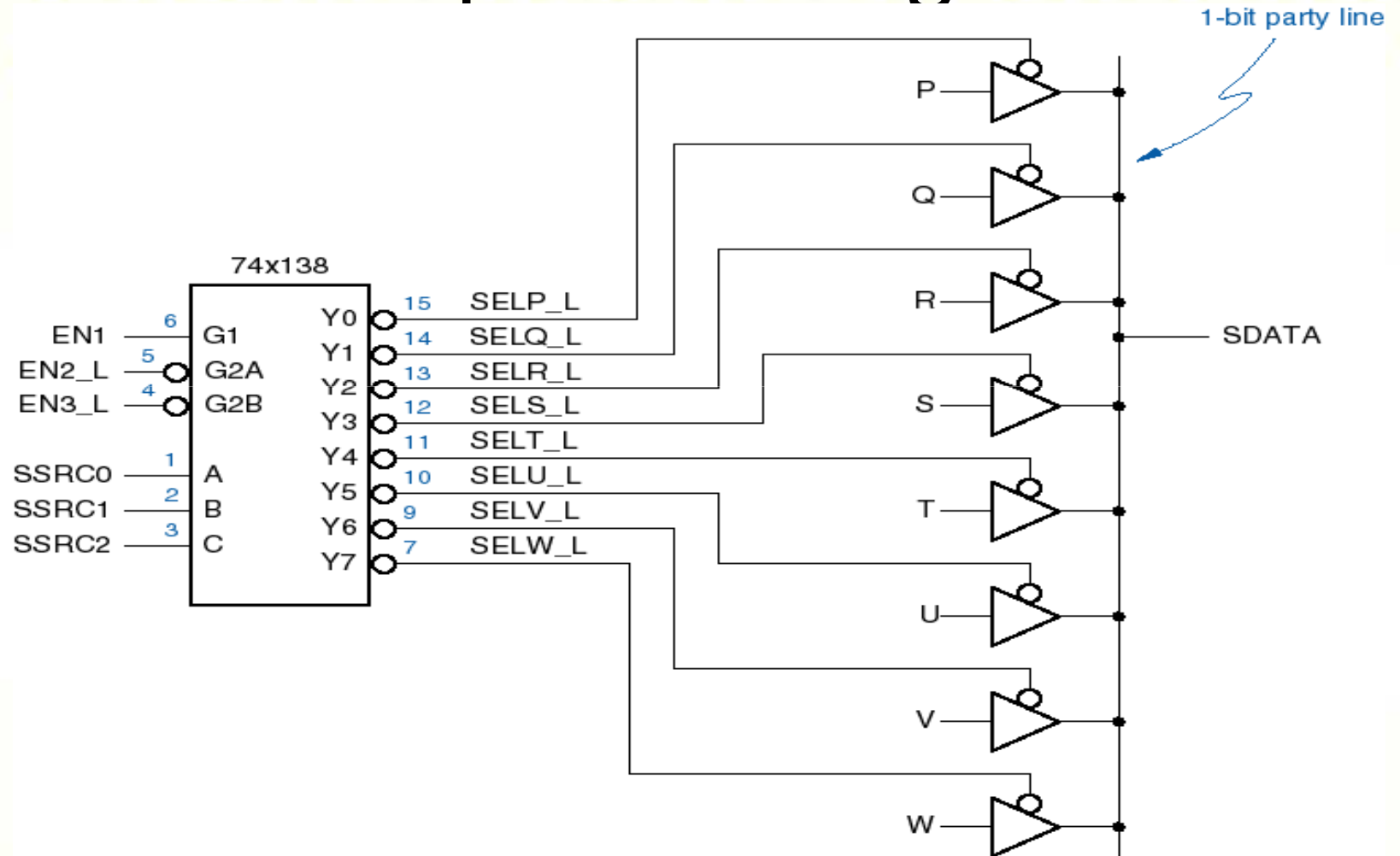


Memory Technology

- Memory chips can store information
- Memory terminologies:
 - **Programmable** : values determined by user
 - **Nonvolatile** : contents retained without power
 - **Read-only memory**: user can read, cannot modify
 - **Random-access Memory**: user can read and write the memory

Read-Only Memory (ROM)

 - A combinational circuit with n inputs and b outputs:



- Two views:



- ROM stores 2^n words of b bits each, or
- ROM stores an n -input, b -output truth table

Example:

$n = 2$		$b = 4$			
A1	A0	D3	D2	D1	D0
0	0	0	1	0	1
0	1	1	1	1	1
1	0	0	0	0	1
1	1	1	0	0	0

← Stores 4 4-bit words, or stores 4 functions of 2 input variables


Logic Implementation Using ROM

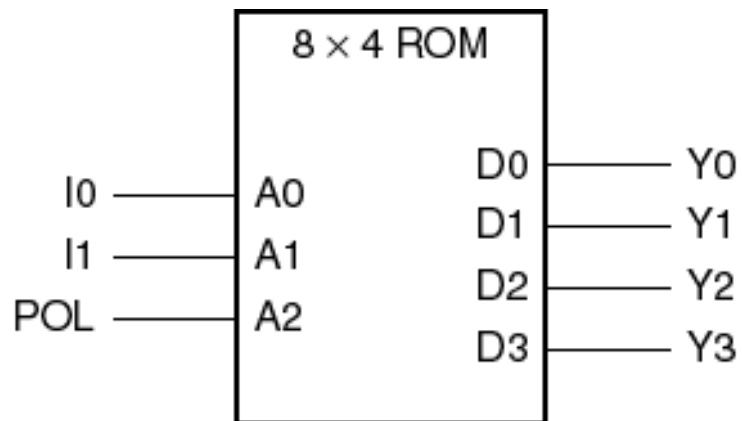 

Function: 2-to-4 Decoder with Polarity Control

A2 = Polarity (0 = active Low, 1 = active High)
 A1, A0 = I1, I0 (2-bit input)
 D3...D0 = Y3...Y0 (4-bit decoded output)

Inputs			Outputs			
A2	A1	A0	D3	D2	D1	D0
0	0	0	1	1	1	0
0	0	1	1	1	0	1
0	1	0	1	0	1	1
0	1	1	0	1	1	1
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0

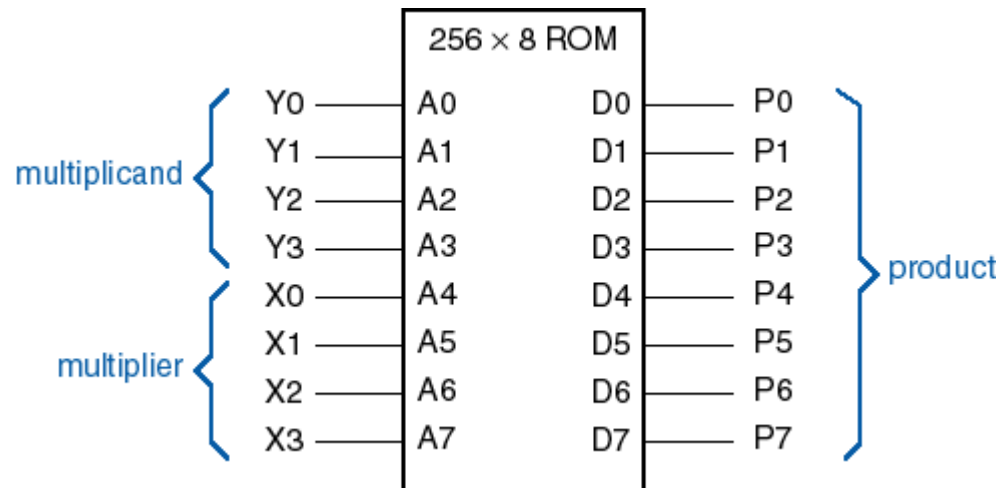


4x4 multiplier example

```

00: 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00
10: 00 01 02 03 04 05 06 07 08 09 0A 0B 0C 0D 0E 0F
20: 00 02 04 06 08 0A 0C 0E 10 12 14 16 18 1A 1C 1E
30: 00 03 06 09 0C 0F 12 15 18 1B 1E 21 24 27 2A 2D
40: 00 04 08 0C 10 14 18 1C 20 24 28 2C 30 34 38 3C
50: 00 05 0A 0F 14 19 1E 23 28 2D 32 37 3C 41 46 4B
60: 00 06 0C 12 18 1E 24 2A 30 36 3C 42 48 4E 54 5A
70: 00 07 0E 15 1C 23 2A 31 38 3F 46 4D 54 5B 62 69
80: 00 08 10 18 20 28 30 38 40 48 50 58 60 68 70 78
90: 00 09 12 1B 24 2D 36 3F 48 51 5A 63 6C 75 7E 87
A0: 00 0A 14 1E 28 32 3C 46 50 5A 64 6E 78 82 8C 96
B0: 00 0B 16 21 2C 37 42 4D 58 63 6E 79 84 8F 9A A5
C0: 00 0C 18 24 30 3C 48 54 60 6C 78 84 90 9C A8 B4
D0: 00 0D 1A 27 34 41 4E 5B 68 75 82 8F 9C A9 B6 C3
E0: 00 0E 1C 2A 38 46 54 62 70 7E 8C 9A A8 B6 C4 D2
F0: 00 0F 1E 2D 3C 4B 5A 69 78 87 96 A5 B4 C3 D2 E1




```

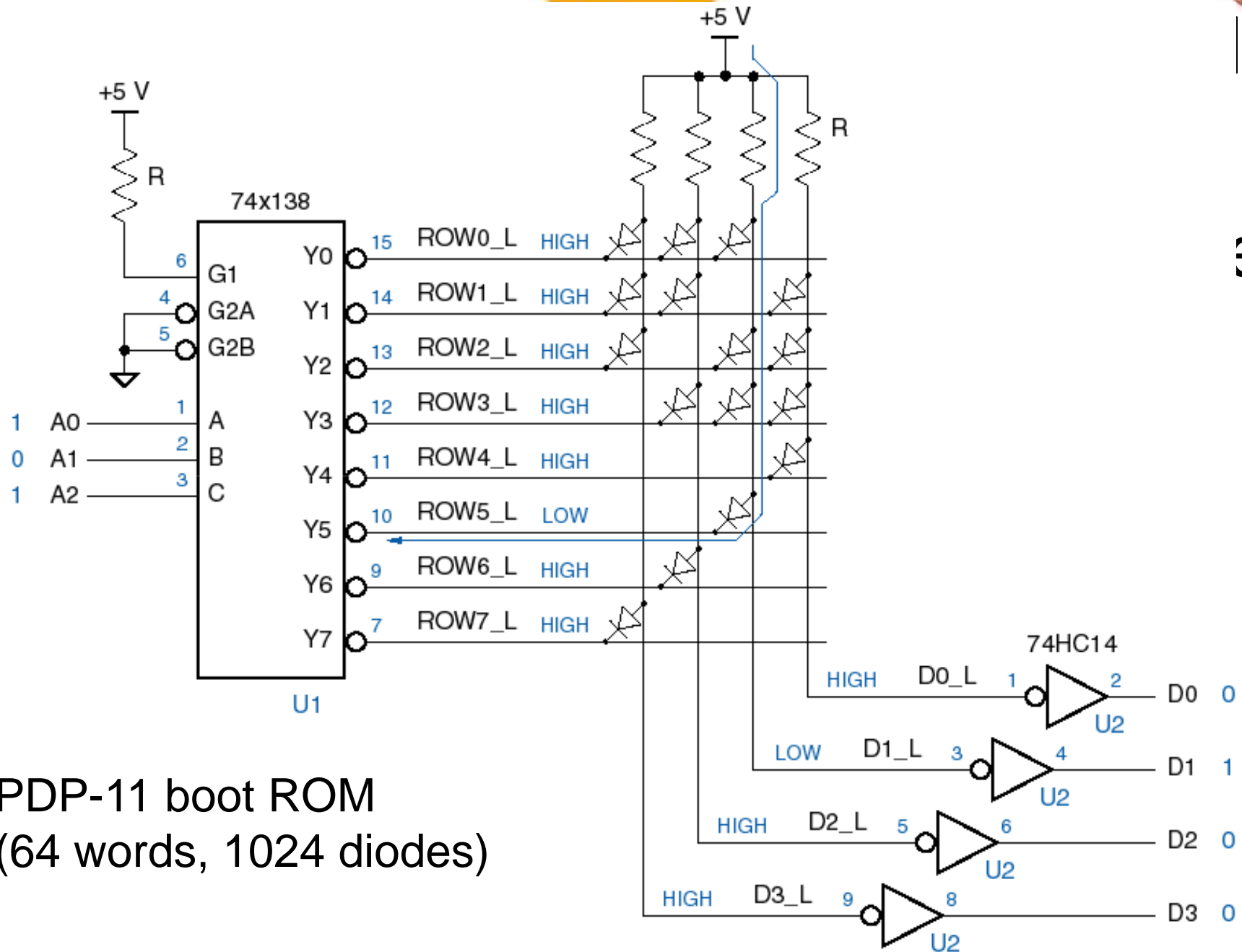

PDP-11 boot ROM
(64 words, 1024 diodes)


Types Of ROMs (1)

- Mask ROM
 - Programming using **mask** by memiconductor vendor
 - The only type that cannot be programmed by user
 - Expensive setup cost
 - Several weeks for delivery
 - Needs high volume to be cost-effective
- PROM
 - **Programmable ROM**
 - Vaporize (blow) fusible links with PROM programmer using high voltage/current pulses
 - Once blown, fuse cannot revert to original state
- EPROM
 - **Erasable Programmable ROM**
 - Charge trapped on extra “floating gate” of MOS transistors
 - Exposure to UV light removes charge
 - 10-20 minutes
 - Quartz Lid = expensive package
 - Limited number of erasures (10-100)

   

Types of ROMs (3)

- OTP ROM
 - One Time Programmable ROM
 - EPROM packaged in cheaper plastic packaging
 - Cannot erase once programmed
 - Used together with EPROM
 - Use regular EPROM for R&D, engineers need to reprogram it
 - Use OTP for shipping product, consumers do not reprogram chips
- EEPROM (E²PROM)
 - Electrically Erasable PROM
 - Floating gates charged/discharged electrically
 - Cannot replace RAM! (slow write)
 - Limited number of charge/discharge cycles (10,000)
- Flash Memory
 - Electronically erasable in blocks
 - 100,000 erase cycles
 - Simpler and denser than EEPROM
 - Very popular in digital cameras, handphones, thumb drives, etc

 


ROM Type Summary

Type	Technology	Read Cycle	Write Cycle	Comments
Mask ROM	NMOS, CMOS	20-200 ns	4 weeks	Write once; low power
Mask ROM	Bipolar	<100 ns	4 Weeks	Write once; high power, low density
PROM	Bipolar	<100 ns	5 minutes	Write once; high power; no mask charge
EPROM	NMOS, CMOS	52-200 ns	5 minutes	Reusable; low power; no mask charge
EEPROM	NMOS	50-200 ns	10 ms/byte	10,000 writes/location limit
FLASH	CMOS	25-200 ns	10 ms/block	100,000 erase cycles

Random Access Memory (RAM)


- Better name should be Read/Write Memory (RWM)
- Can store and retrieve data at the same speed
- Two types:
 - **Static RAM (SRAM)** retains data in latches (while powered)
 - **Dynamic RAM (DRAM)** stores data as capacitor charge; all capacitors must be recharged periodically.
- Static RAM:
 - Fast
 - Simple interface
 - Moderate bit density (4 to 6 transistors per bit)
 - Moderate cost/bit
 - For small systems or very fast requirements (eg cache memory)
- Dynamic RAM:
 - Moderate speed
 - Complex interface
 - High bit density (1 transistor cell per bit)
 - Low cost/bit
 - For large memories (eg main memory in PC, servers)

Basic Structure of SRAM

 

- Address/Control/Data Out lines like a ROM (Reading)
+ Write Enable (WE) and Data In (DIN) (Writing)

One Bit of SRAM

 

Control Input	Chip Function
SEL and WR asserted	IN data stored in D-latch (Write)
SEL only asserted	D-latch output enabled (Read)
SEL not asserted	No operation

A worked Example

- Given these functions
$$X(A,B,C,D) = m(1,3,5,7,8,9,11)$$
$$Y(A,B,C,D) = m(0,2,4,5,7,8,10,11,12)$$
$$Z(A,B,C,D) = m(1,2,3,5,7,10,12,13,14,15)$$
 - Implement X using AND/OR
 - Implement Y using NAND/NAND
 - Implement Z using NOR/NOR
 - Implement Y using 8:1 multiplexer
 - Implement XYZ using 74x138 decoder and NAND gates
 - Implement XYZ using ROM


Implement

$$X(A,B,C,D) = m(1,3,5,7,8,9,11)$$

Using AND/OR gates

		<i>CD</i>			
	<i>AB</i>	00	01	11	10
00		0	1	1	0
01		0	1	1	0
11		0	0	0	0
10		1	1	1	0

 Solving the K-map we get $X = A'D + B'D + AB'C'$



Implement using NAND gates



$$Y(A,B,C,D) = \sum m(0,2,4,5,7,8,10,11,12)$$

		CD			
	AB	00	01	11	10
00	1	0	0	1	
01	1	1	1	0	
11	1	0	0	0	
10	1	0	1	1	

Solving the K-map we get
 $Y = C'D' + B'D' + A'BD$

Exercise:

Implement Y using NOR gates

  

Implement using NOR gates


$$Z(A,B,C,D) = \sum m(1,2,3,5,7,10,12,13,14,15)$$

		CD			
		00	01	11	10
AB	00	0	1	1	1
	01	0	1	1	0
	11	1	1	1	1
	10	0	0	0	1

Solving the K-map using POS gives
 $Z = (A' + B + D')(A + B' + D)(B + C + D)$

Exercise:

Implement Z using NAND gates

 


Implement using 8:1 MUX

$$Y(A,B,C,D) = \sum m(0,2,4,5,7,8,10,11,12)$$

A B	C D			
	00	01	11	10
00	1	0	0	1
01	1	1	1	0
11	1	0	0	0
10	1	0	1	1



A B	C	
	0	1
00	D'	D'
01	1	D
11	D'	0
10	D'	1

 

Exercise 1:

Implement Y using 8:1 MUX but with C connected to S2, B to S1, and A connected to S0.

Exercise 2:

Implement Y using 8:1 MUX but with B connected to S2, C to S1, and D connected to S0.



Implement using 74x138

$$X(A,B,C,D) = m(1,3,5,7,8,9,11)$$

$$Z(A,B,C,D) = m(1,2,3,5,7,10,12,13,14,15)$$

Exercise 1:


Implement X but with input B, C, D connected to decoder selectors C, B, A respectively.

Exercise 2:

Implement Z but with input B, C, D connected to decoder selectors C, B, A respectively.

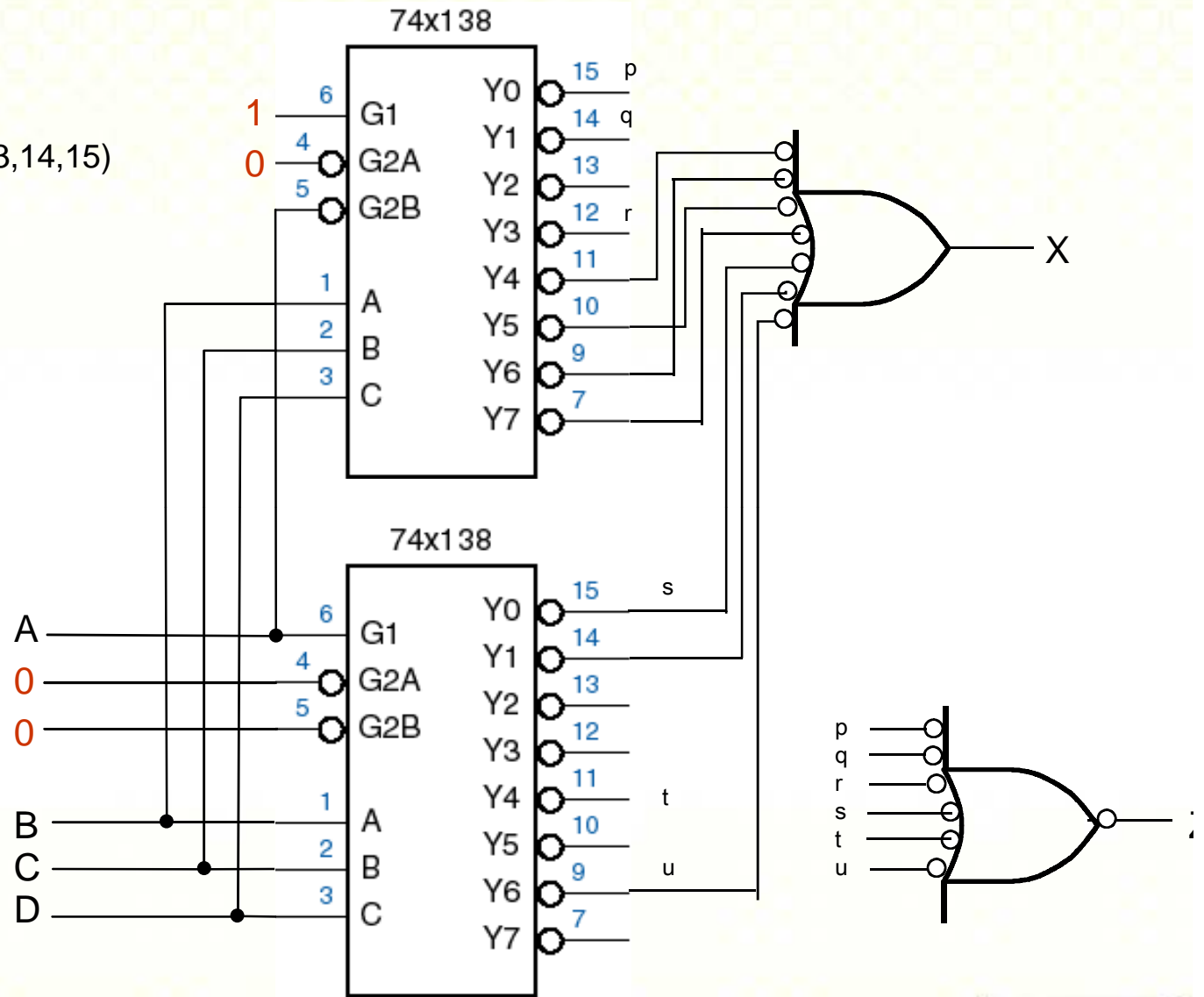Exercise 3:

Implement Z with input B, C, D connected to decoder selectors C, B, A respectively, but you must use a 10-input NAND gate.




Implement

$$X(A,B,C,D) = m(1,3,5,7,8,9,11)$$

$$Y(A,B,C,D) = m(0,2,4,5,7,8,10,11,12)$$

$$Z(A,B,C,D) = m(1,2,3,5,7,10,12,13,14,15)$$

Using ROM

 

Input				Output		
A3	A2	A1	A0	D2	D1	D0
0	0	0	0	0	1	0
0	0	0	1	1	0	1
0	0	1	0	0	1	1
0	0	1	1	1	0	1
0	1	0	0	0	1	0
0	1	0	1	1	1	1
0	1	1	0	0	0	0
0	1	1	1	1	1	1
1	0	0	0	1	1	0
1	0	0	1	1	0	0
1	0	1	0	0	1	1
1	0	1	1	1	1	0
1	1	0	0	0	1	1
1	1	0	1	0	0	1
1	1	1	0	0	0	1
1	1	1	1	0	0	1