

# SEE3243

## Digital System

**Lecturers :**

**Muhammad Mun'im Ahmad Zabidi**

**Muhammad Nadzir Marsono**

**Kamal Khalil**


### *Chapter 2: Logic Theory*



# Implicant, Prime Implicant and Essential Prime Implicant

- **Implicant** - a single minterm or group of minterms that can be combined together on the K-map. **A'B'C'**, **A'BC'**, **A'BC**, **ABC**, **A'C'**, **A'B**, and **BC**.
- **Prime Implicant** - Implicant that can not be combined with another one to remove a literal. **A'C'**, **A'B**, **BC**.
- **Essential Prime Implicant** - A prime implicant that includes a minterm not covered by any other prime implicant. **A'C'** and **BC**. Why? **A'B'C'** only covered by **A'C'** and **ABC** only covered by **BC**.

$$F(A,B,C) = \sum m(0,2,3,7)$$

 

## Finding Minimum Expression

- Draw the K-map and put 1's in each square that corresponds to a minterm of the function.
- Find the ***prime implicants***. Groups must be a power of 2.
- Find the ***essential prime implicants***. An essential prime implicant is a prime implicant that includes 1's that are not covered by any other prime implicants.
- Write down the minimized expression. First write down all essential prime implicants. If there are any 1's not covered by prime implicants, *carefully* select prime implicants to cover the remaining 1's. Note, you may have to try several selections to find the minimal form of the expression.

## Confuse with the steps? Another example

- Use a K-map to simplify the following Boolean function:

$$F(A,B,C,D) = \prod M(0,1,2,4,9,11,15)$$

$$F(A,B,C,D) = \sum m(3,5,6,7,8,10,12,13,14)$$

AB \ CD		0	0	11	1
		0	1		0
0	0	0	1	1	0
	1	1	1	1	1
1	0	1	1	1	1
	1	1	1	1	1
11	0	1	1	1	1
	1	1	1	1	1
1	0	1	1	1	1
	1	1	1	1	1
0	0	1	1	1	1
	1	1	1	1	1

Prime Implicants

AB \ CD		0	0	11	1
		0	1		0
0	0	0	1	1	0
	1	1	1	1	1
1	0	1	1	1	1
	1	1	1	1	1
11	0	1	1	1	1
	1	1	1	1	1
1	0	1	1	1	1
	1	1	1	1	1
0	0	1	1	1	1
	1	1	1	1	1

Essential Prime Implicants

AB \ CD		0	0	11	1
		0	1		0
0	0	0	1	1	0
	1	1	1	1	1
1	0	1	1	1	1
	1	1	1	1	1
11	0	1	1	1	1
	1	1	1	1	1
1	0	1	1	1	1
	1	1	1	1	1
0	0	1	1	1	1
	1	1	1	1	1

Final Expression

$$F(A,B,C,D) = BC'D + AD' + A'CD + BCD'$$

# Entered Variable K-Map (EVM)

- EVM extends map for function with too many variable for a ordinary Karnaugh Map
- Let say ordinary K Map has  $n$  map variable. So far we've looked to 4 map variables, max.
- If a function has  $(m+n)$  variables, to be fit into  $n$ -bit K-map,  $m$ -bit must reside into  $n$ -bit minterm in K map as ***entered variable***.
- Fortunately, in this lecture,  $m = 1$
- Confuse?


## An example

- $F = A'BCD + A'B'CDE + ABC'D'E' + A'BC'DE'$
- A,B,C,D - *map variables*.
- E - *entered variable*. The entered variable completes the expression represented by the map variables.
- The second term is loaded in the 0011 cell because of  $A'B'CD$ . The cell is loaded with E to complete the term.
- The final 2 terms are treated in the same way. For  $ABC'D'E'$ , the 1100 cell is loaded with E. For  $A'BC'DE'$  the 0101 cell is loaded with E'.

		CD			
		00	01	11	10
AB	00	0	1	3 E	2
	01	4	5 E'	7 1	6
	11	12 E'	13	15	14
	10	8	9	11	10
 
# SOP example

- In this example, a function with 4 variables need to be re-organise in K-map with 3 map variables only.
- In the above K-map, in every combination of A,B and C, we will compare the output with variable D.
- If the output is the complement of D, put  $D'$  inside that particular cell.
- Another way is by using truth table first, then into 3-bit K map.



# SOP example

- From previous function, let say  $F$ , we first organise it into a truth table.
- Then find the entered variables.
- Reorganise into 3-bit K map.

		CD			
		0	0	11	1
AB	0	0	1	3	2
	0	1	7	6	
0	4	5	7	6	
0	1			1	
1	12	13	15	14	
11	1	1		1	
1	8	9	11	10	
0		1	1		

		BC			
		0	0	11	1
A	0	0	1	3	2
	0	0	D	D'	D'
0	4	5	7	6	
1	D	D	D'	1	

A	B	C	D	F	EV
0	0	0	0	0	0
0	0	0	1	0	
0	0	1	0	0	D
0	0	1	1	1	
0	1	0	0	1	D'
0	1	0	1	0	
0	1	1	0	1	D'
0	1	1	1	0	
1	0	0	0	0	D
1	0	0	1	1	
1	0	1	0	0	D
1	0	1	1	1	
1	1	0	0	1	1
1	1	0	1	1	
1	1	1	0	1	D'
1	1	1	1	0	



## How to minimise EVM

### EVM grouping rules

- Entered variables can be grouped with
  - Other identical entered variables
  - 1s
- Find and circle all the single EV's which cannot be grouped
- Find and group all single EV's which can be grouped in only one way with other entity
- Find and group all single EV's which can be grouped in more than one way.  
Group these variables
  - first with another identical ungrouped entered variable
  - second with uncovered or partially covered 1
  - **make arbitrary choice when needed**

## Example 1

- Still the same function.
- '1' in ABC' can be decomposed to  $D+D'$ .
- Then, group the identical entered variables.
- Follow the procedure.
- $F(A,B,C,D) = BD' + B'CD + AC'D$

	BC	00	01	11	10
A	0	0 <sup>0</sup> 0	D <sup>1</sup>	D' <sup>3</sup>	D' <sup>2</sup>
	1	D <sup>4</sup>	D <sup>5</sup>	D' <sup>7</sup>	1 <sup>6</sup>

	BC	00	01	11	10
A	0	0 <sup>0</sup> 0	D <sup>1</sup>	D' <sup>3</sup>	D' <sup>2</sup>
	1	D <sup>4</sup>	D <sup>5</sup>	D' <sup>7</sup>	D'+D <sup>6</sup>

- Now, compare function F from EVM in previous slide with the minimisation result from the original 4-bit K map.
- Do you get the same answer?

		CD			
		00	01	11	10
AB	00	0	1	3 1	2
	01	4 1	5	7	6 1
	11	12 1	13 1	15	14 1
	10	8	9 1	11 1	10

$F(A,B,C,D) =$  \_\_\_\_\_

## Example 2

- Lets call this function G.
  - ‘1’ in  $A'B'C'$  can be decomposed to  $D+D'$ .
  - Then, group the identical entered variables.

		CD			
		00	01	11	10
AB	00	0 1	1 1	3 1	2
	01	4	5	7 1	6 1
	11	12	13	15 1	14 1
	10	8 1	9	11 1	10

		BC			
		00	01	11	10
A	0	0 1	1 D	3 1	2 0
	1	4 D'	5 D	7 1	6 0

		BC			
		00	01	11	10
A	0	0 1	1 D	3 1	2 0
	1	4 D'	5 D	7 1	6 0

- Follow the procedure.
  - $F(A,B,C,D) = CD + B'C'D' + BC + A'B'D$

- Now, compare function G from EVM in previous slide with the minimisation result from the original 4-bit K map.
- Do they yield the same answer?

		CD			
		00	01	11	10
AB	00	0 1	1 1	3 1	2
	01	4	5	7 1	6 1
	11	12	13	15 1	14 1
	10	8 1	9	11 1	10

$G(A,B,C,D) =$  \_\_\_\_\_

## Example 3


- Change 1 to E+E'
- Then group entries with neighbour cells that have the same entered variable
- Note that all the entities are covered
- $F = ABC'D'E' + A'BDE' + A'CDE$

		CD			
		00	01	11	10
AB	00	0	1	3	2
	01	4	5	7	6
	11	12	13	15	14
	10	8	9	11	10

		CD			
		00	01	11	10
AB	00	0	1	3	2
	01	4	5	7	6
	11	12	13	15	14
	10	8	9	11	10
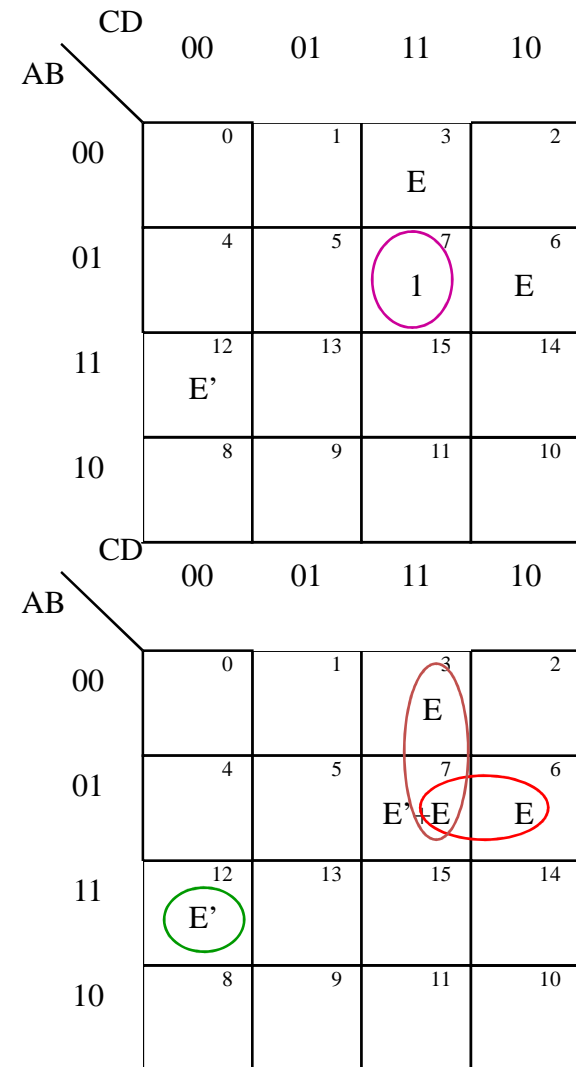
## Example 4

- What if not all entities covered?
- In this example, partially covered '1' at  $A'BCD$  must be covered (so that the  $E'$  variable is covered).
- Thus,  $F = ABC'D'E' + A'BCE + A'CDE + A'BCD$



## Example 5

- F is a function of A,B,C,D,E.
- Let E become entered variable

		CD			
		00	01	11	10
AB	00	0 1	1	3	2 1
	01	4	5 E'	7	6 E'
	11	12	13 E'	15 E	14
	10	8 1	9 E'	11 E'	10 1

$$\begin{aligned}
 &F(A,B,C,D,E) \\
 &= B'D' + AB'E' + BC'DE' + \\
 &\quad A'CD'E' + ABCDE
 \end{aligned}$$

A	B	C	D	E	F		A	B	C	D	E	F
0	0	0	0	0	1		1	0	0	0	0	1
0	0	0	0	1	1		1	0	0	0	1	1
0	0	0	1	0	0		1	0	0	1	0	1
0	0	0	1	1	0		1	0	0	1	1	0
0	0	1	0	0	1		1	0	1	0	0	1
0	0	1	0	1	1		1	0	1	0	1	1
0	0	1	1	0	0		1	0	1	1	0	1
0	0	1	1	1	0		1	0	1	1	1	0
0	1	0	0	0	0		1	1	0	0	0	0
0	1	0	0	1	0		1	1	0	0	1	0
0	1	0	1	0	1		1	1	0	1	0	1
0	1	0	1	1	0		1	1	0	1	1	0
0	1	1	0	0	1		1	1	1	0	0	0
0	1	1	0	1	0		1	1	1	0	1	0
0	1	1	1	0	0		1	1	1	1	0	0
0	1	1	1	1	0		1	1	1	1	1	1



# How to solve EVM in POS?

- Almost the same procedure like solving EVM in SOP.
- The differences,
  - Group identical EV
  - Substitute '0' with EV.EV' (Example D.D').
  - Except for 0-0 grouping, complement EV when writing in SOP.
- Complement using De-Morgan
- More confused? You should.

## Example 1

- Lets call this function H.
- Note that in cell  $A'B'C'$ , the EV is '0', and written as  $D'.D$ .

		CD			
		00	01	11	10
AB	00	0 0	1 0	3 0	2 0
	01	4	5 0	7 0	6
	11	12	13	15 0	14
	10	8 0	9	11	10 0

		BC			
		00	01	11	10
A	0	$D'.D^0$	$D^1$	$D'^3$	$D'^2$
	1	$D^4$	$D^5$	$D'^7$	$1^6$

$$H'(A,B,C,D) = B'D' + A'C'D + BCD$$

$$H(A,B,C,D) = (B+D)(A+C+D')(B'+C'+D')$$

- Now, compare function H from EVM in previous slide with the minimisation result from the original 4-bit K map.
- Do they yield the same answer?

		CD			
		00	01	11	10
AB	00	0 0	1 0	3	2 0
	01	4	5 0	7 0	6
	11	12	13	15 0	14
	10	8 0	9	11	10 0

$$H'(A,B,C,D) = \underline{\hspace{10em}}$$

$$H(A,B,C,D) = \underline{\hspace{10em}}$$

# DIY

- Now, you try.
- Check your answer with 4-bit K map POS minimisation.

## EVM

$$H'(A,B,C,D) = \underline{\hspace{10cm}}$$

$$H(A,B,C,D) = \underline{\hspace{10cm}}$$

## 4-bit K map

$$H'(A,B,C,D) = \underline{\hspace{10cm}}$$


$$H(A,B,C,D) = \underline{\hspace{10cm}}$$

		CD			
		0	0	11	1
AB	0	0	1	3	2
	0	4	5	7	6
	1	0	0		
	11	12	13	15	14
		0	0		
	1	8	9	11	10
	0		0		0

		BC			
		00	01	11	10
A	0	0	1	3	2
	1	4	5	7	6
 
## Logic Transformation


- By performing transformation operations, different (and possibly simpler) gate networks for the same function are possible.
- Simple equivalencies:







- Based on DeMorgan's Theorems
  - $(AB)' = A' + B'$
  - $(A + B)' = A'B'$
- Thus, AND-OR networks can be transformed to OR-NAND, NAND-NAND, NOR-OR, etc.
 
## Example


- This transformation changes AND-OR form into OR-NAND form.
- However, usually we are interested in transforming circuit (SOP or POS) into negative logics (yes.. NAND, NOR, Inverter).
- Why? Negative logic is extensively used in VLSI.



## Another Example (NAND-NAND)

    

## Another Example (NOR-NOR)

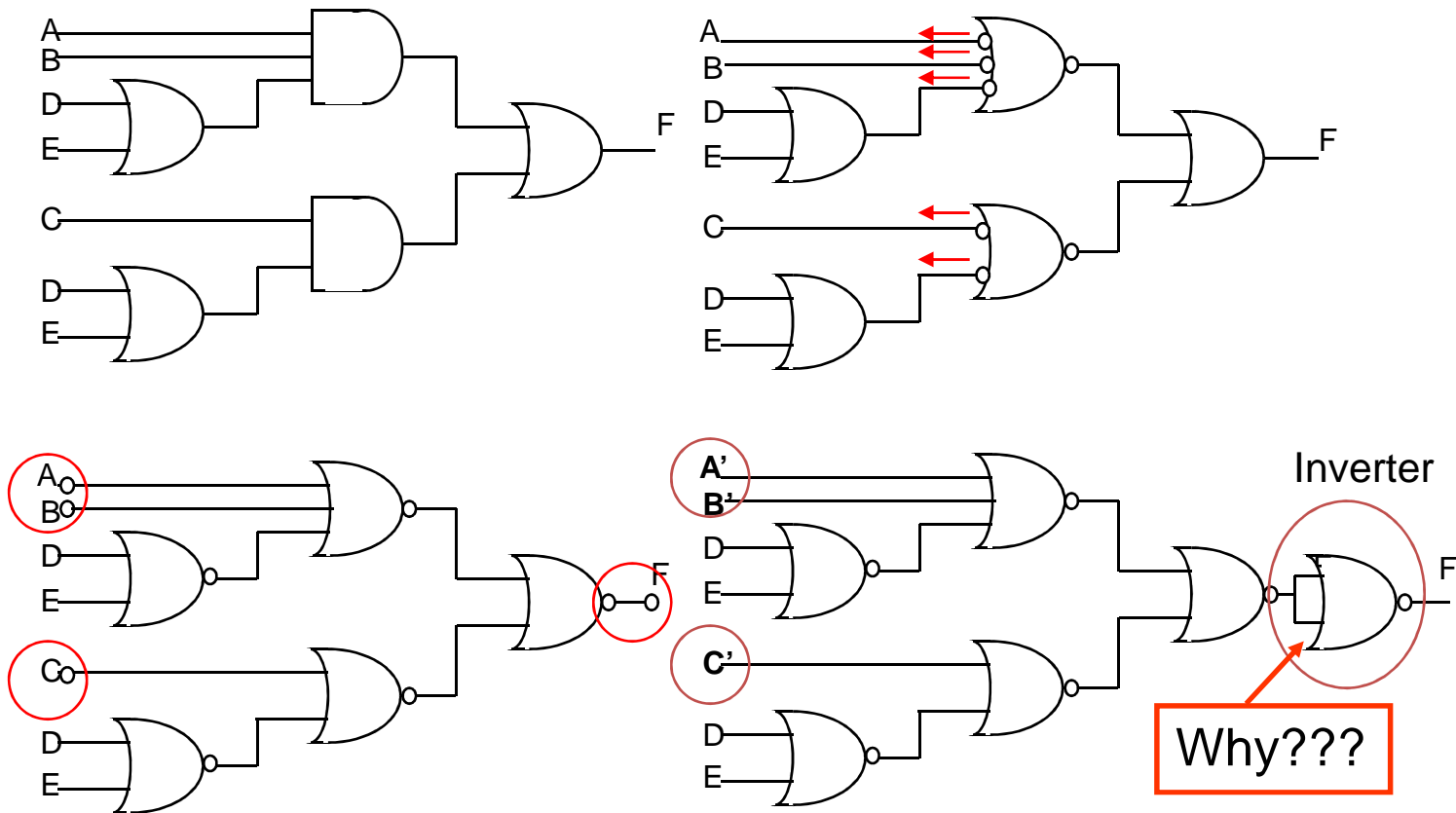





## Transformation: General Rules (AND-OR-INVERTER Network only)

- To convert to NAND-only form
  - Begin with SOP form with an OR gate output (if not, add inverter at the output *later*)
  - AND (odd level) and OR (even level) gates must alternate between levels! (1,2,..n)
  - Level 0 for input
  - Replace all gates with NAND gates
  - Put inverter if no gate between  $2k$  ( $k = 1,2,..m$ ) level.
- Algorithm for NOR-form is similar, but start with POS form, OR (odd level) and AND (even level). Still, if the output is not AND gate, add inverter later.

# Example 1 (NAND-NAND)

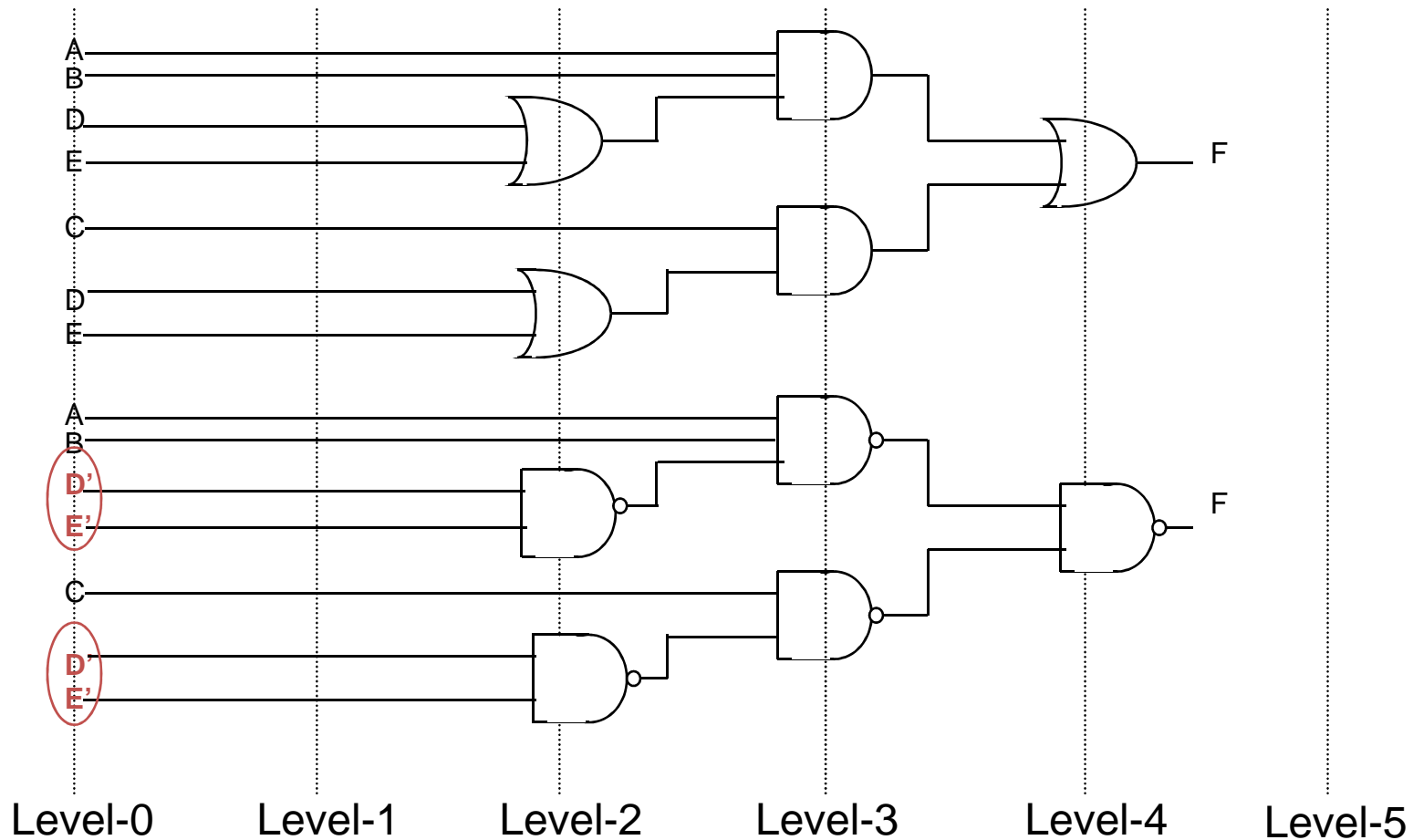

## Example 2 (NOR-NOR)

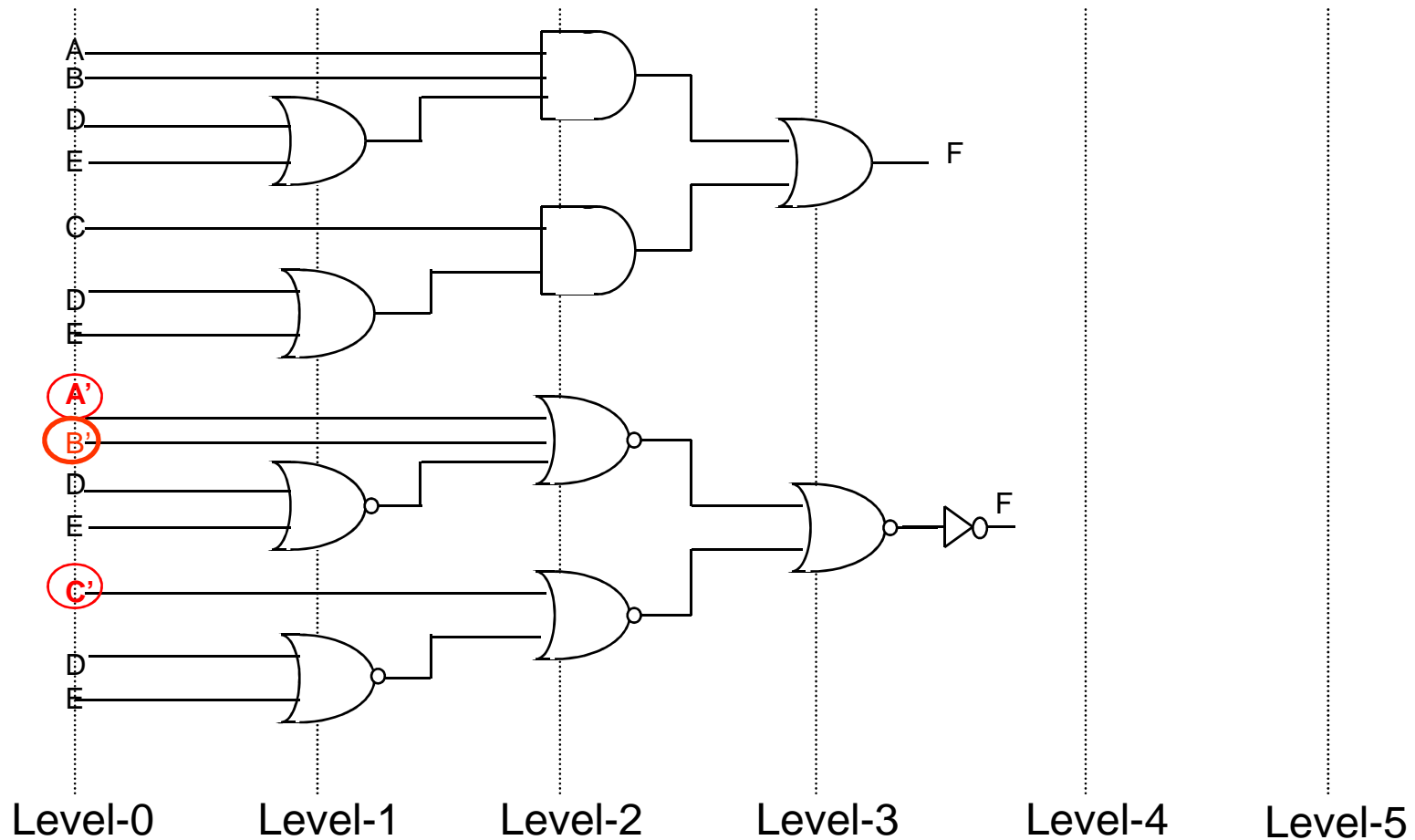

## DIY 1

- Implement this function using NAND-NAND transformation (don't derive the K-map or the truth table)

$$F(A,B,C,D,E,F,G,H,I,J) = ((A+B)+C+DE).((G+H).F.I).(J)$$

## DIY 2

- Implement this function using NOR-NOR transformation
- $F(A,B,C,D) = (B+D)(A+C+D')(B'+C'+D')$

# DIY3

- Transform this equation into NOR-NOR gates
  - $F(A,B,C,D) = (AB'(C'+BD'))+A'(BC+D(A'+B))$

# DIY 4

- Transform this equation into NAND-NAND gates

$$- F(A,B,C,D) = (AB'(C'+BD'))+A'(BC+D(A'+B))$$


## Introduction to Hazard and Glitch

- A ***hazard*** is a characteristic of a circuit.
- A ***glitch*** is an unwanted pulse that may occur in a circuit with a hazard.
- A circuit with a hazard may or may not glitch.
- As an ***analogy*** a wet floor at the supermarket is a hazard. It's not a problem unless someone slips and falls which would be a glitch.
- The state of a circuit and the pattern of input values determines if a circuit with a hazard will cause glitch.



 
## Types of Hazards

- A static hazard is when the output should remain static but experiences an unwanted pulse.
- A dynamic hazard is when the output should go through a smooth transition but changes more than once before settling at the new value.





## Example 1

- $F(A,B,C) = AB' + BC$

 



## Example 2

- $F(A,B,C) = (A + B)(B' + C)$

  
 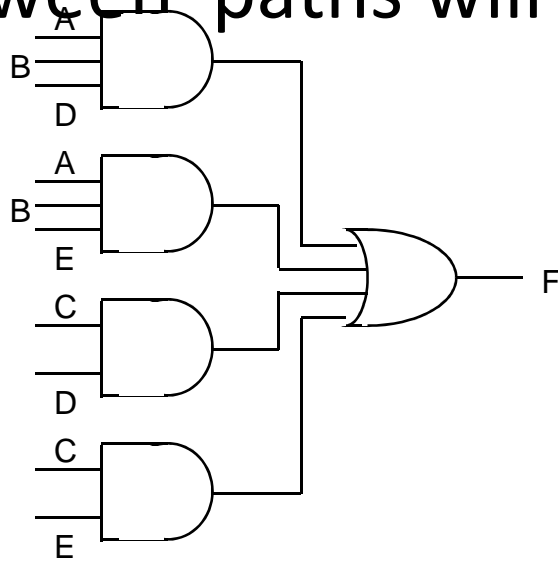
## Example 3

- $F = ABD + ABE + CD + CE$
- 5 gates, 14 inputs
- It can be factored: simpler but has short and long delay paths. Inequalities of delays between paths will contribute to hazards



# What's Next

- You will look at the MSI design. How to use standard devices to realise digital circuitry.
- Make sure you understand this chapter first.