

SEE 3243

Digital System

Lecturers :

Muhammad Mun'im Ahmad Zabidi

Muhammad Nadzir Marsono

Kamal Khalil

Week 4:

Programmable Logic Devices (PLDs)



Problems by Using Basic Gates

- Many components on PCB
- As no. of components rise, nodes interconnection complexity grow exponentially
- Growth in interconnection will cause increase in interference, PCB size, PCB design cost, and manufacturing time




Solution: use PLDs

Types of Programmable Logic Devices

- SPLDs (Simple Programmable Logic Devices)
 - ROM (Read-Only Memory)
 - PLA (Programmable Logic Array)
 - PAL (Programmable Array Logic)
 - GAL (Generic Array Logic)


Device	AND-array	OR-array
PROM	Fixed	Programmable
PLA	Programmable	Programmable
PAL	Programmable	Fixed
GAL	Programmable	Fixed

Basic Configuration of Three Simple PLDs

   


AND PLD Notation

Programming is done by blowing the fuse

 


AND gate before programming

 


AND gate after programming

OR PLD Notation

Programming is done by blowing the fuse

 


OR gate before programming

 


OR gate after programming


PROM Notation

 

PROM Implementation

 

PLA Notation

 

A virgin PLA has X at all AND and OR junctions

PLA Implementation

X_2	X_1	X_0	F_1	F_2
0	0	0	1	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	0
1	0	0	0	1
1	0	1	1	0
1	1	0	0	1
1	1	1	1	0

$x_2 \setminus x_1x_0$	00	01	11	10
0	1	1	0	1
1	0	1	1	0

$$F_1 = X_2 X_0 + X_2' X_0' + X_2' X_1' X_0$$


$x_2 \setminus x_1x_0$	00	01	11	10
0	0	1	0	1
1	1	0	0	1

$$F_2 = X_2 X_0' + X_1 X_0' + X_2' X_1' X_0$$

reused

PLA Implementation

 
Try to implement both functions using minimum number of total terms (product sharing). Hence F_1 has 3-input term.



$$F_1 = X_2 X_0 + X_2' X_0' + X_2' X_1' X_0$$

$$F_2 = X_2' X_1' X_0 + X_2 X_0' + X_1' X_0$$

PAL Notation

 

Each AND gate is permanently connected to a certain OR gate

PAL Implementation

x2	x1	x0	F1	F2
0	0	0	1	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	0
1	0	0	0	1
1	0	1	1	0
1	1	0	0	1
1	1	1	1	0


x2 \ x1x0	00	01	11	10
0	1	1	0	1
1	0	1	1	0

$$F_1 = X_2 X_0 + X_2' X_0' + X_1' X_0$$

x2 \ x1x0	00	01	11	10
0	0	1	0	1
1	1	0	0	1

$$F_2 = X_2' X_1' X_0 + X_2 X_0' + X_1' X_0$$

PAL Implementation


 


$$F_1 = X_2 X_0 + X_2' X_0' + X_1' X_0$$

$$F_2 = X_2' X_1' X_0 + X_2 X_0' + X_1' X_0$$


A Real P

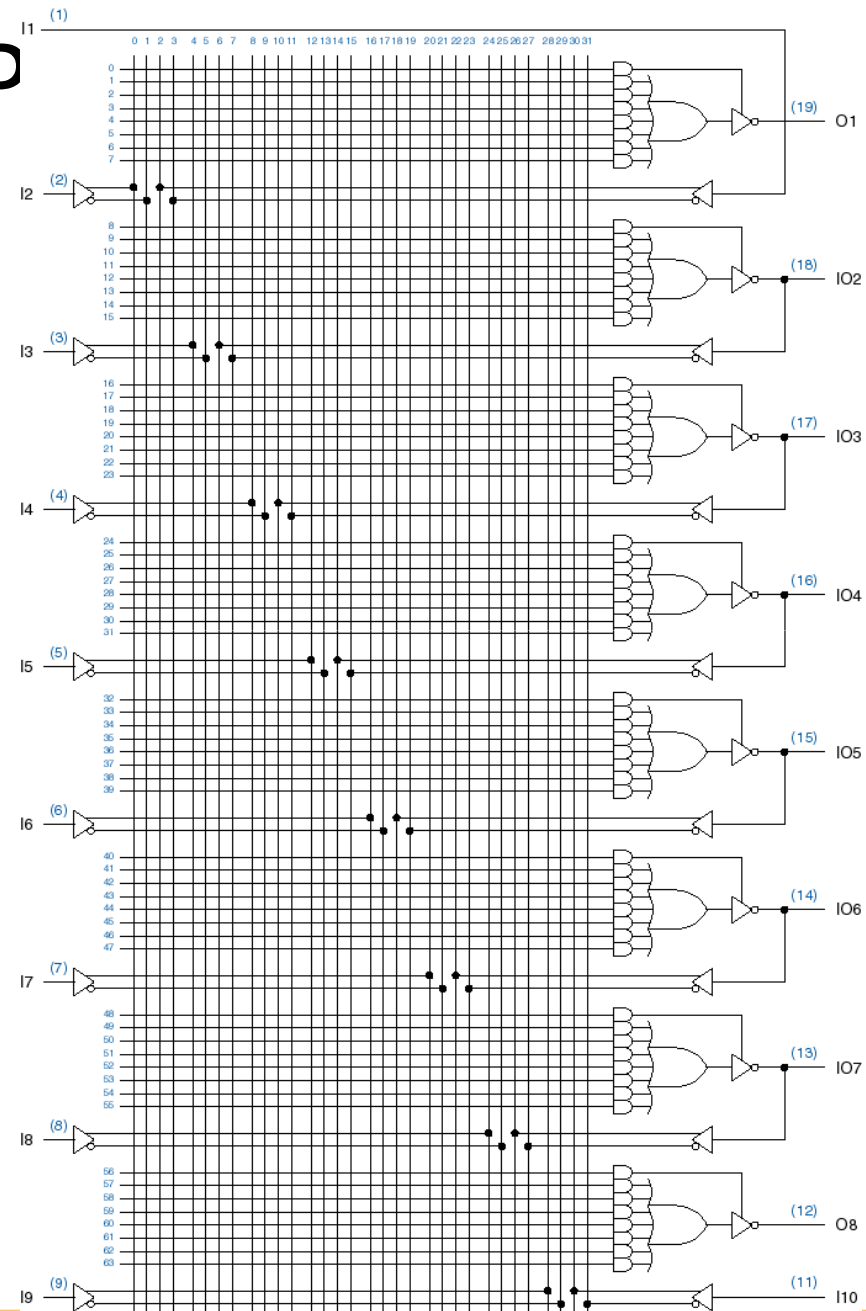 - There're 64 AND gates
- Each AND gate can have 32 inputs (16 variables & complements)
- There're 8 outputs
- Don't count the I/O pins!
- Three common output configs:
 - L = pure combinational
 - R = registered
 - V = macrocell



Sequential PALs

- 16R8
- Notice 8 flip-flops at output

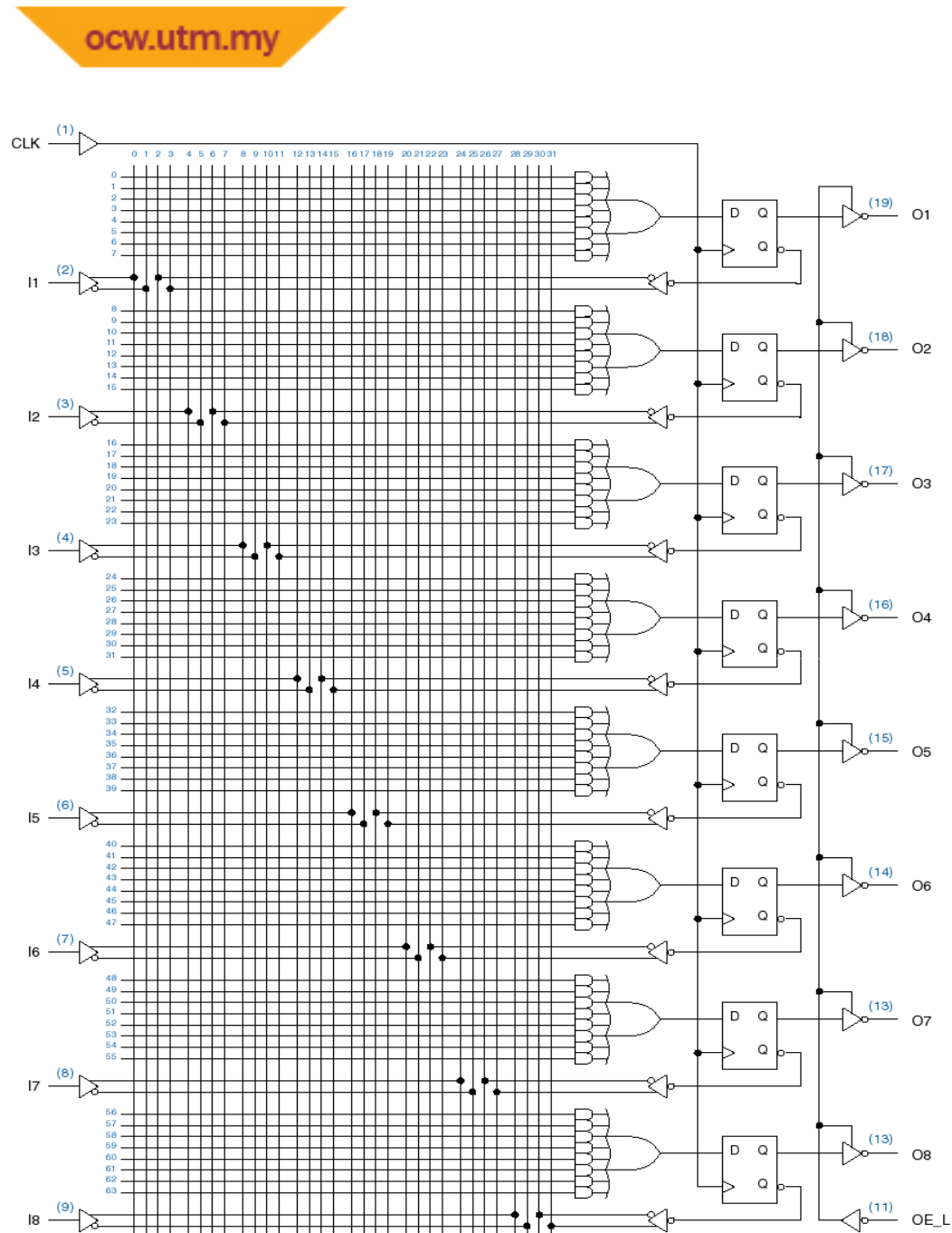

GAL (Generic Array Logic)

- GAL can emulate a number of PALs
- No need for PAL anymore!

	PAL	GAL
Device technology	Fuse	Electrically erasable cell
Reconfigurability	One-time programmable	Erasable, reprogrammable
I/O	Fixed function	Selectable: input/output, combinational/registered


Oh, by the way...

GAL is trademark of Lattice Semiconductor: example GAL22V10

Universal PAL is the trademark of Vantis: example PALCE22V10 (but it's the same thing!)


GAL16V8

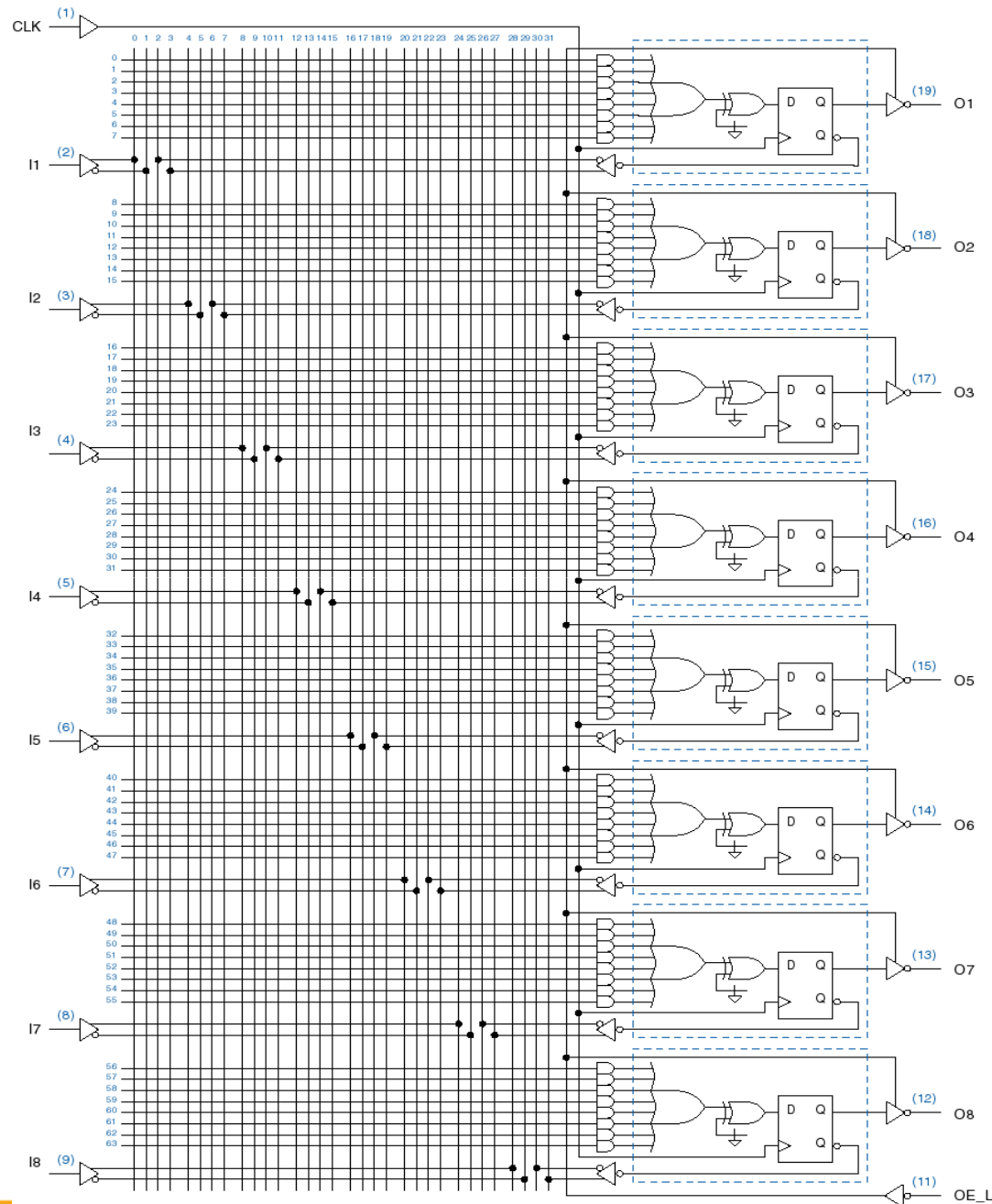- Each output is programmable as combinational or registered
- Also has programmable output polarity




OLMC

 - OLMC = Output Logic Macrocell
- Simplified, equivalent circuits:




a. Registered/active LOW

$S_1 = 0$
 $S_0 = 0$

 


b. Registered/active HIGH

$S_1 = 0$
 $S_0 = 1$

 

c. Combinatorial/active LOW


$S_1 = 1$
 $S_0 = 0$

 

d. Combinatorial/active HIGH

$S_1 = 1$
 $S_0 = 1$

Simplified GAL Representation

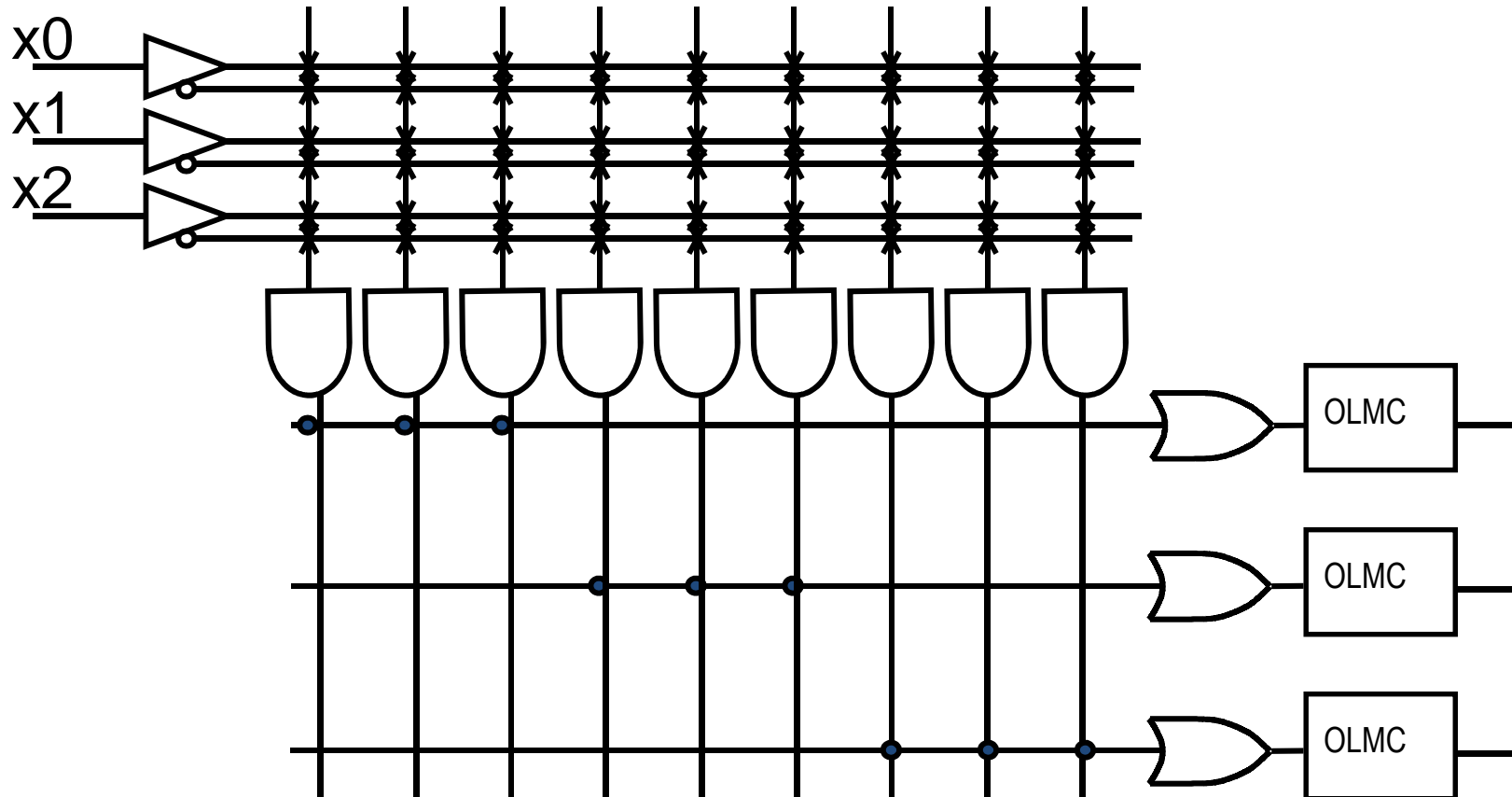


PLD programming unit (courtesy of Data IO Corp)




Problems Using SPLD

- Current trend is
 - Increasing gate count
 - Increase design complexity
 - Requirement for smaller size due to lower cost, lower power and higher reliability
 - Fast prototyping for quick design verification
 - PROM, PLA and PAL not used much except in small designs!
- Solution:
 - CPLD for intermediate complexity
 - FPGA for very complex designs (up to millions of gates)


Structure of CPLD

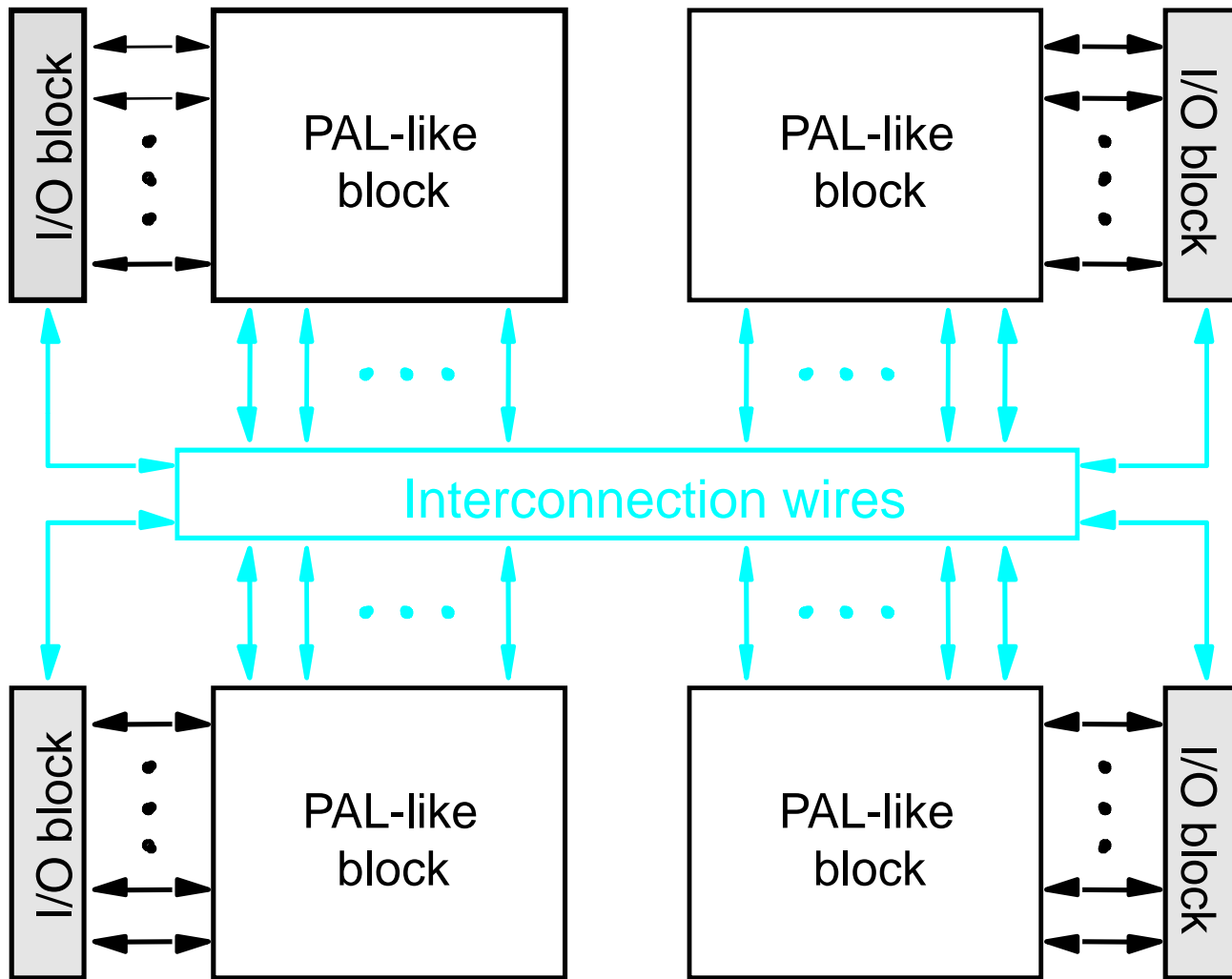

CPLD Packaging and Programming

 

 (a) CPLD in a Quad Flat Pack (QFP) package



(b) JTAG programming


Advantages of CPLDs

- Reduced circuit board space utilization, and significant cost savings

A 44-pin CPLD is equivalent to 600 gates



=

 

Some CPLDs have gate equivalents in the millions and over 1000 pins


Advantages of CPLDs

- Easiest to modify
 - Use appropriate CAD tools
- Direct entry of conceptual design into functional circuit
 - Streamlined design to prototype process




Advantages of CPLDs

 - Universal inventory, as one IC can be programmed for various applications




- Easy to duplicate

 

Advantages of CPLDs

 - Reprogrammability
 - CPLD can be reprogrammed hundreds of times.



- Number of I/Os
 - CPLDs have large amounts of programmable input/output contacts.


Advantages of CPLDs

- **Software and Language**
 - Manufacturers of CPLDs supply design software (software like Altera Quartus II is a free download)
 - VHDL is a standards-based language that most manufacturers conform to
- **Simple Interface**
 - Devices can be interfaced directly to a computer with a serial or USB connection
- **In-circuit modifications**
 - With the proper interface connections, the CPLD logic can be edited in-circuit
- **Transportable design**
 - As a designer you may easily exchange your designs and design modifications (e-mail, CD, web site, etc. ...)

CPLDs and FPGAs


CPLD

Complex Programmable Logic Device

 

FPGA

Field-Programmable Gate Array

 

Architecture

PAL/22V10-like
More Combinational

Gate array-like
More Registers + RAM

Density

Low-to-medium
0.5-10K logic gates

Medium-to-high
1K to 1M system gates

Performance

Predictable timing
Up to 250 MHz today

Application dependent
Up to 150 MHz today


Interconnect

“Crossbar Switch”

Incremental


CPLDs vs. FPGAs

- CPLD architecture

 

□ = input/output block

FPGA architecture

 


- Much larger number of smaller programmable logic blocks.
 - Xilinx calls them CLB (Configurable Logic Block)
 - Altera calls them LAB (Logic Array Block) and EAB (Embedded Array Block)
- Embedded in a sea of lots and lots of programmable interconnects.

Design Flow

① **Design Entry** in schematic and/or HDL (ABEL, VHDL, Verilog). Vendors include Altera, Synopsys, Aldec (Xilinx Foundation), Mentor Graphics, Cadence, Viewlogic, etc.

② **Implementation** includes Placement & Routing. Also, analyze timing, view layout, and more.

 Download directly to the hardware device(s) with almost unlimited reconfigurations!!



Development Process

