

MSI Circuits



- Multiplexers (Mux)
 - 2x1, 4x1, and 8x1 muxes
 - 74x151, 74x153, 74x157 devices
- Demultiplexers (Demux), Decoders, and Encoders
 - 74x138 and 74x139 decoders
 - Encoder and priority encoder
 - BCD to 7-segment decoder and the 7447 device
 - Logic functions using muxes and decoders
- Adders and Comparators
 - Half, full and ripple carry adders
 - The 74x83 devices
 - Comparator and the 74x85 devices

Demultiplexers (Demux)

- Reverse of the multiplexing function
- Takes data from one line and distributes to a given number of output lines
- Demux can be designed as 1x2, 1x4, 1x8, etc.

Demux (cont.)

- 1x2 Demux

  

Function:

$D_0 = D, D_1 = 0$ when $S = 0$

$D_1 = D, D_0 = 0$ when $S = 1$




$$D_0 = D \cdot \bar{S}$$

$$D_1 = D \cdot S$$

Demux (cont.)

- 1x4 Demux

 

$$D_0 = D \cdot \overline{S_1} \cdot \overline{S_0}$$

$$D_1 = D \cdot \overline{S_1} \cdot S_0$$

$$D_2 = D \cdot S_1 \cdot \overline{S_0}$$

$$D_3 = D \cdot S_1 \cdot S_0$$

Can you draw the logic circuit?


Data at D is distributed to D_0 to D_3 depending on select S_1 and S_0

Decoders

- Detect the presence of a specified combination of bits (code) on its inputs and to indicate the presence of that code by a specified output level
- Standard decoders are designed as 1x2, 2x4, 3x8, 4x16, etc
- Other decoders include the BCD to 7-segment LED decoder, gray code decoder, etc.

Decoders

 - 2x4 Decoder: only one output is active at one time




Active high output decoder

Function:

$$\begin{aligned}
 O_3 O_2 O_1 O_0 = 0001 \text{ when } \mathbf{A_1 A_0} = \mathbf{00} &\longrightarrow O_0 = \overline{A_1} \cdot \overline{A_0} \\
 O_3 O_2 O_1 O_0 = 0010 \text{ when } \mathbf{A_1 A_0} = \mathbf{01} &\longrightarrow O_1 = \overline{A_1} \cdot A_0 \\
 O_3 O_2 O_1 O_0 = 0100 \text{ when } \mathbf{A_1 A_0} = \mathbf{10} &\longrightarrow O_2 = A_1 \cdot \overline{A_0} \\
 O_3 O_2 O_1 O_0 = 1000 \text{ when } \mathbf{A_1 A_0} = \mathbf{11} &\longrightarrow O_3 = A_1 \cdot A_0
 \end{aligned}$$

Decoders (cont.)

 - Decoders are typically designed as active low



Bubble at output denotes active low output

Function:

$$O_3 O_2 O_1 \mathbf{O}_0 = 1110 \text{ when } \mathbf{A_1 A_0} = \mathbf{00} \longrightarrow O_0 = A_1 + \underline{A_0}$$


$$O_3 O_2 \mathbf{O}_1 O_0 = 1101 \text{ when } \mathbf{A_1 A_0} = \mathbf{01} \longrightarrow O_1 = \underline{A_1} + A_0$$

$$O_3 \mathbf{O}_2 O_1 O_0 = 1011 \text{ when } \mathbf{A_1 A_0} = \mathbf{10} \longrightarrow O_2 = \underline{A_1} + \underline{A_0}$$

$$\mathbf{O}_3 O_2 O_1 O_0 = 0111 \text{ when } \mathbf{A_1 A_0} = \mathbf{11} \longrightarrow O_3 = \underline{A_1} + \underline{A_0}$$

Decoders (cont.)

- 3x8 Decoder

 

Function:

$$O_7 O_6 O_5 O_4 O_3 O_2 O_1 O_0 = 1111\ 1110 \text{ when } A_2 A_1 A_0 = 000$$

$$O_7 O_6 O_5 O_4 O_3 O_2 O_1 O_0 = 1111\ 1101 \text{ when } A_2 A_1 A_0 = 001$$

$$O_7 O_6 O_5 O_4 O_3 O_2 O_1 O_0 = 1111\ 1011 \text{ when } A_2 A_1 A_0 = 010$$

$$O_7 O_6 O_5 O_4 O_3 O_2 O_1 O_0 = 1111\ 0111 \text{ when } A_2 A_1 A_0 = 011$$

$$O_7 O_6 O_5 O_4 O_3 O_2 O_1 O_0 = 1110\ 1111 \text{ when } A_2 A_1 A_0 = 100$$

$$O_7 O_6 O_5 O_4 O_3 O_2 O_1 O_0 = 1101\ 1111 \text{ when } A_2 A_1 A_0 = 101$$

$$O_7 O_6 O_5 O_4 O_3 O_2 O_1 O_0 = 1011\ 1111 \text{ when } A_2 A_1 A_0 = 110$$

$$O_7 O_6 O_5 O_4 O_3 O_2 O_1 O_0 = 0111\ 1111 \text{ when } A_2 A_1 A_0 = 111$$

How does the logic circuit look like?

- Can we use K-Map?

Decoders (cont.)


- Decoder IC's
 - 2x4 Decoder → 74139
 - 3x8 Decoder → 74138

BCD to 7 Segment Decoder

- 74247 BCD to 7 Segment Decoder

Converts 4-bit BCD (A_3, A_2, A_1, A_0) to 7-segment LED (a,b,c,d,e,f,g)

Logic Symbol

 


V_{CC} = Pin 16
GND = Pin 8

Input: A_3, A_2, A_1, A_0

Control Input: LT, RBI, RBO

Output: a, b, c, d, e, f, g


**** note that output is active low**

 


BCD to 7 Segment Decoder (cont.)

- What is the output of 74247 if input $(A_3A_2A_1A_0)=0110$?

Logic Symbol

 

V_{CC} = Pin 16
GND = Pin 8

 


a	b	c	d	e	f	g
0	1	0	0	0	0	0


BCD to 7 Segment Decoder (cont.)

- What is the output of 74247 if input $(A_3A_2A_1A_0)=0011$?

Logic Symbol

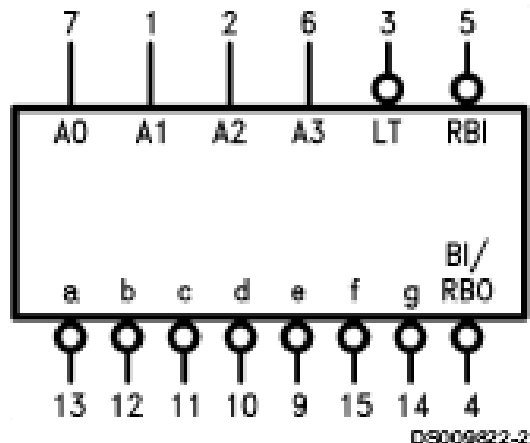

V_{CC} = Pin 16
GND = Pin 8

 


a	b	c	d	e	f	g
0	0	0	0	1	1	0

Encoders

- Performs reverse decoder function
- Only one input can be active at one time

4x2 Encoder

 

Function:

$$A_1A_0 = 00 \text{ when } D_3D_2D_1D_0 = 1110$$

$$A_1A_0 = 01 \text{ when } D_3D_2D_1D_0 = 1101$$

$$A_1A_0 = 10 \text{ when } D_3D_2D_1D_0 = 1011$$

$$A_1A_0 = 11 \text{ when } D_3D_2D_1D_0 = 0111$$

Which implies,

$$A_1 = D_3\overline{D_2}\overline{D_1}D_0 + \overline{D_3}D_2D_1D_0$$


$$A_0 = D_3D_2\overline{D_1}D_0 + \overline{D_3}D_2D_1D_0$$

What happens if more than one input is '0' ($D_0 = 0$ and $D_1 = 0$)?
 - output is invalid, we need a priority encoder

Encoders (cont.)

- Priority Encoder: Output depends on the largest active input

4x2 Priority Encoder

 

Function:

$A_1A_0 = 00$ when $D_3D_2D_1D_0 = 1110$

$A_1A_0 = 01$ when $D_3D_2D_1D_0 = 110x$

$A_1A_0 = 10$ when $D_3D_2D_1D_0 = 10xx$

$A_1A_0 = 11$ when $D_3D_2D_1D_0 = 0xxx$

Can you derive the truth table of the priority encoder?

What happens if more than 1 input is '0' ($D_0 = 0$ and $D_1 = 0$)?


- output $A_1A_0 = 01$

Logic function using Mux


- Any logic function (AND, OR, decoder, encoder, etc) can be realized using mux. All we need is a truth table
- This is the concept widely being used today in FPGA (Field Programmable Gate Array), where any logic functions can be rapidly implemented using Mux

Logic function using Mux (cont.)

- 2-input AND gate using 4x1 Mux

 

X	Y	$Z = X \cdot Y$
0	0	0
0	1	0
1	0	0
1	1	1

 


Logic function using Mux (cont.)

- Implement the following using Mux


$$F(A, B, C) = \sum m(0,1,4,7)$$

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 

Logic function using Decoder

 
- Similar to Mux, any logic function can be realized using decoders
- 2-input AND gate using 2x4 decoder



AND gate

X	Y	$Z = X \cdot Y$
0	0	0
0	1	0
1	0	0
1	1	1

2x4 Decoder

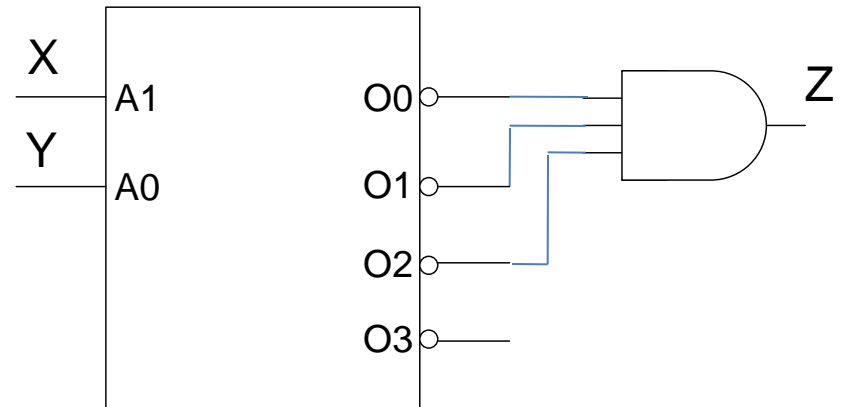


Logic function using Decoder (cont.)

- Implement the following using 74138

$$F(A, B, C) = \prod M(2, 3, 5, 6)$$

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

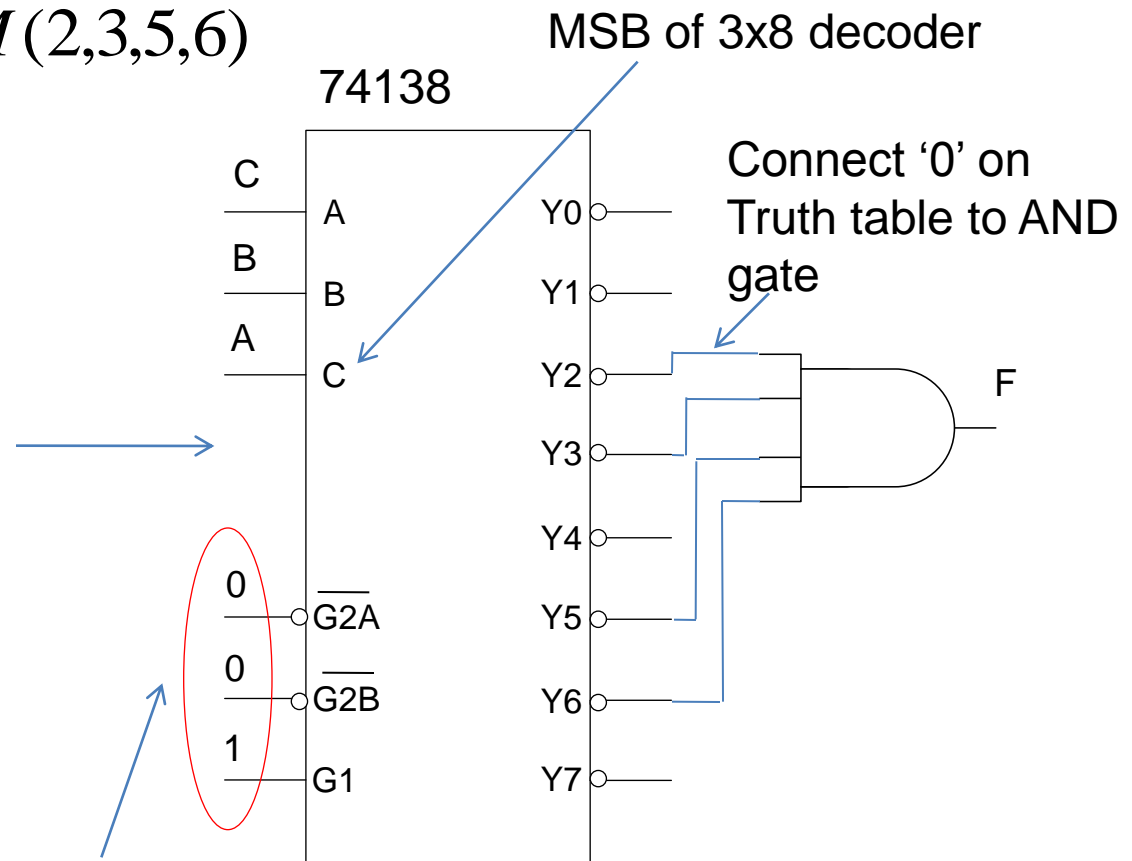

Logic function using Decoder(cont.)

- Logic function of decoders can also be implemented using a NAND gate

$$F(A, B, C) = \prod M(2,3,5,6)$$

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

