

# SEE1223: Digital Electronics

## 6 – Counters and Registers

**Zulkifil Md Yusof**

Dept. of Microelectronics and Computer Engineering  
The Faculty of Electrical Engineering  
Universiti Teknologi Malaysia




# Counter and Registers

- Counters
  - Asynchronous Counters
  - Synchronous Counters
  - Design of Synchronous Counters
  - 74163 devices
- Registers
  - Shift Registers
    - SISO, SIPO, PISO, PIPO
  - Shift Register Counters
    - Johnson and Ring
  - 74164, 74165, 74194, and 74195 devices
 
# Introduction to Counters

- Counters – Circuit that performs the operation of counting at every clock edge



If CLR = 0

$$Q_2Q_1Q_0 = 000$$

Else if CLR = 1

if clk = ↓

$$Q_2Q_1Q_0 = Q_2Q_1Q_0 + 001$$

else

$$Q_2Q_1Q_0 = Q_2Q_1Q_0$$


Clear output

Increment by 1 at every  
Negative edge of clk

Maintain previous value
 
# Introduction to Counters (cont.)

- Draw the output waveforms  $Q_2$ ,  $Q_1$  and  $Q_0$  for a negative edge triggered 3-bit counter with active low clear




# Introduction to Counters (cont.)

- Counter are designed using flip-flops, typically the negative edge triggered
- Counters can be designed as asynchronous or synchronous
- Asynchronous counters – The clock is applied on the first stage. Subsequent stages derive the clock from the previous stage
- Synchronous counters – The clock is applied to all stages using a common clock signal
- Synchronous counters perform better than asynchronous counters, therefore, are widely used in digital systems
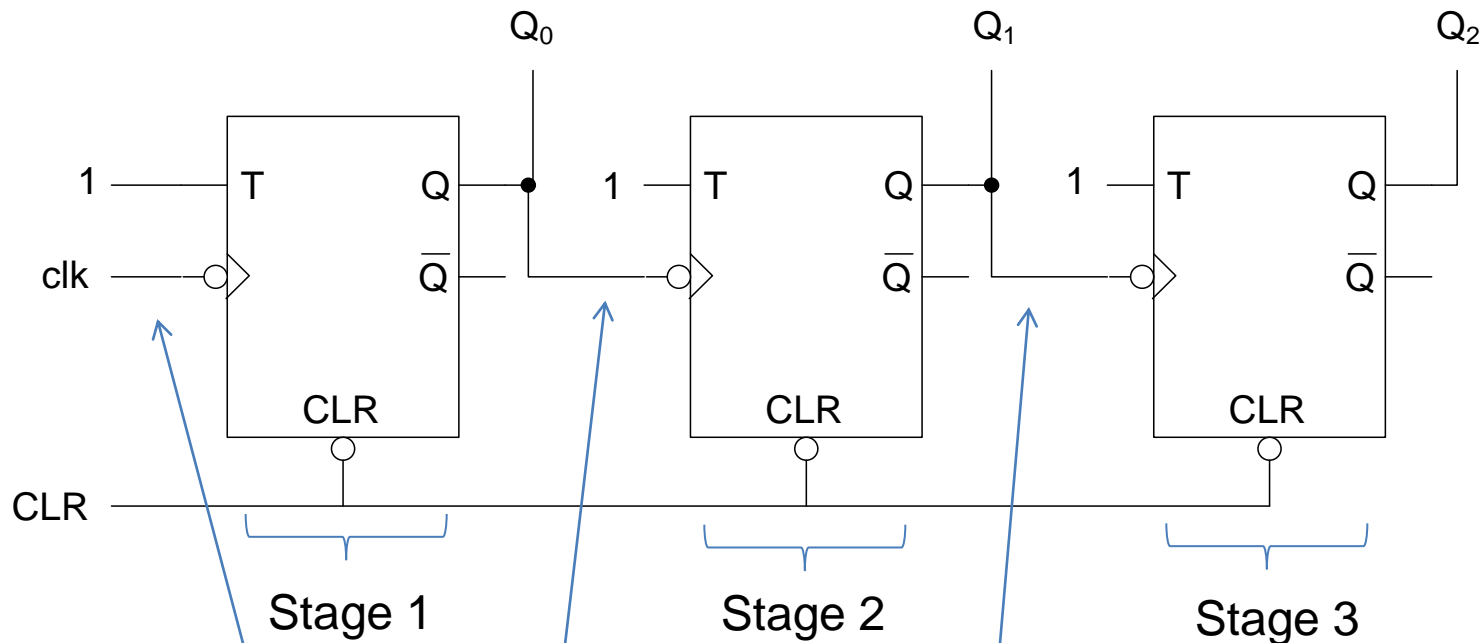
# Asynchronous Counters

- 3-bit asynchronous counter using T Flip-flops




In asynchronous counters, the clk signal is fed to the 1<sup>st</sup> stage only. Subsequent stages take the Q from the previous stage for clk

Can you draw the waveform for Q<sub>2</sub>, Q<sub>1</sub> and Q<sub>0</sub> for 8 clock cycles?  
Can you identify the problem with asynchronous counters?
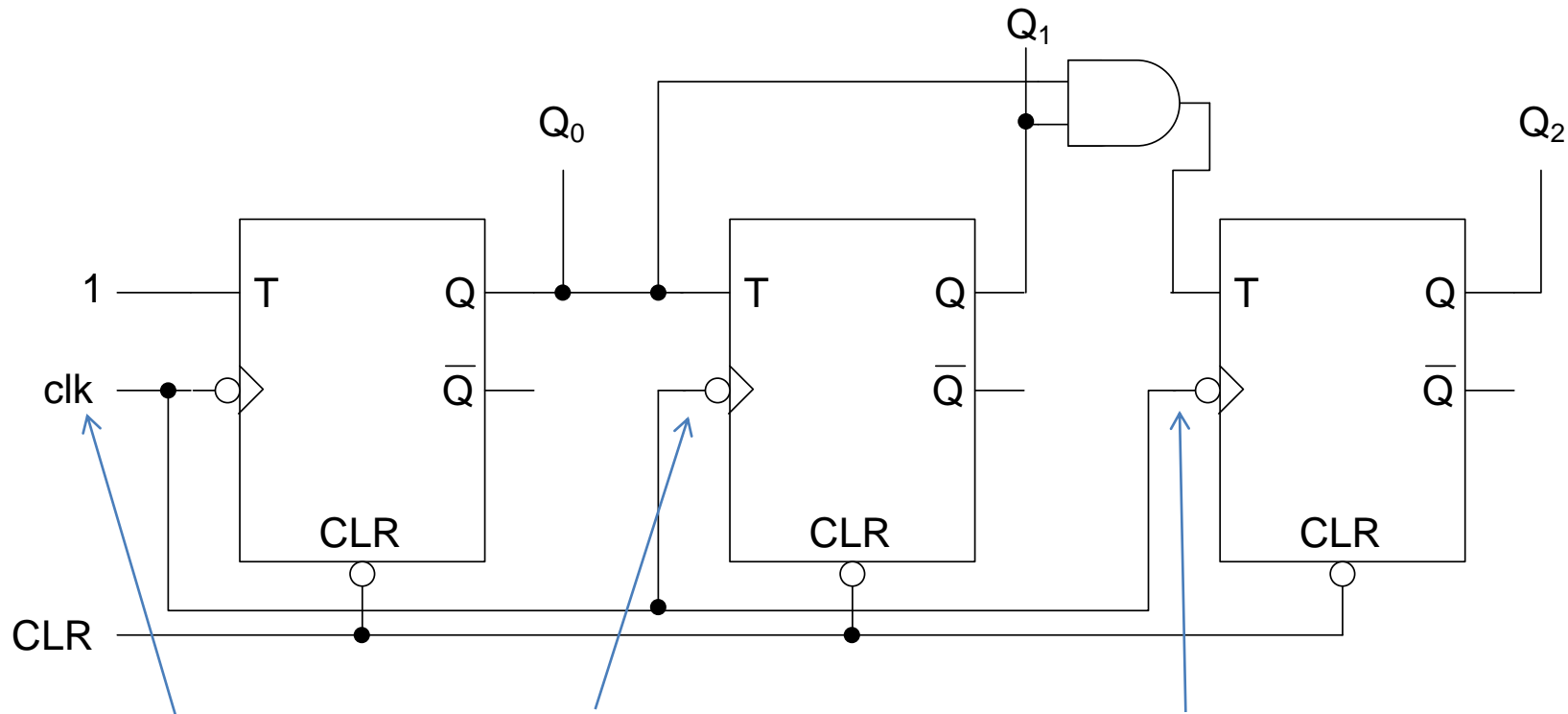
# Synchronous Counters

- 3-bit Synchronous Counter using T Flip-flops



In synchronous counters, a common clk signal is used to clock all flip-flops

Can you draw the waveform for Q<sub>2</sub>, Q<sub>1</sub> and Q<sub>0</sub> for 8 clock cycles?

Why is the synchronous counter superior to asynchronous counters?


# Design of Synchronous Counters

- How to design the 3-bit synchronous counter?
  - There is a systematic procedure of designing synchronous counters
    - Step 1: Derive the state transition diagram
    - Step 2: Derive the next state and state transition table
    - Step 3: Using K-Maps, derive the logic expressions
    - Step 4: Implement the circuit


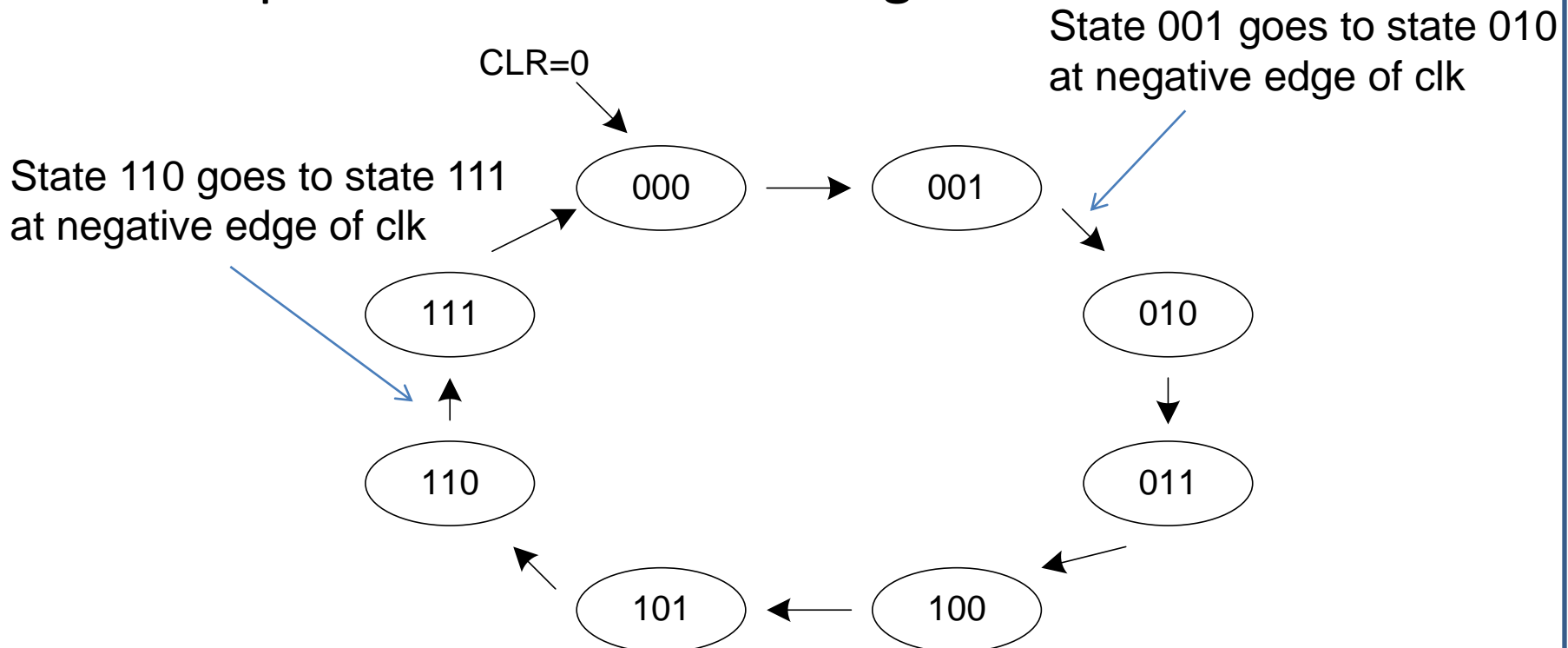
# Design of Synchronous Counters

- The design of negative edge triggered 3-bit synchronous counter using T Flip-flops
  - Step 1: Derive the state diagram



# Design of Synchronous Counters

- Step 2: Derive the next state and state transition table




3-bit counter, we need 3 flip-flops

Using T flip-flops

Present State			Next State			Output Transition			Flip-flop Inputs		
Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	T <sub>2</sub>	T <sub>1</sub>	T <sub>0</sub>
0	0	0	0	0	1	0→0	0→0	0→1	0	0	1
0	0	1	0	1	0	0→0	0→1	1→0	0	1	1
0	1	0	0	1	1	0→0	1→1	0→1	0	0	1
0	1	1	1	0	0	0→1	1→0	1→0	1	1	1
1	0	0	1	0	1	1→1	0→0	0→1	0	0	1
1	0	1	1	1	0	1→1	0→1	1→0	0	1	1
1	1	0	1	1	1	1→1	1→1	0→1	0	0	1
1	1	1	0	0	0	1→0	1→0	1→0	1	1	1

   
# Design of Synchronous Counters

- Step 3: Using K-Maps, derive the logic expressions



# Design of Synchronous Counters

- Step 4: Implement the circuit

 

$$T_0 = 1$$


$$T_1 = Q_0$$

$$T_2 = Q_1 \cdot Q_0$$

Which is the same circuit as before
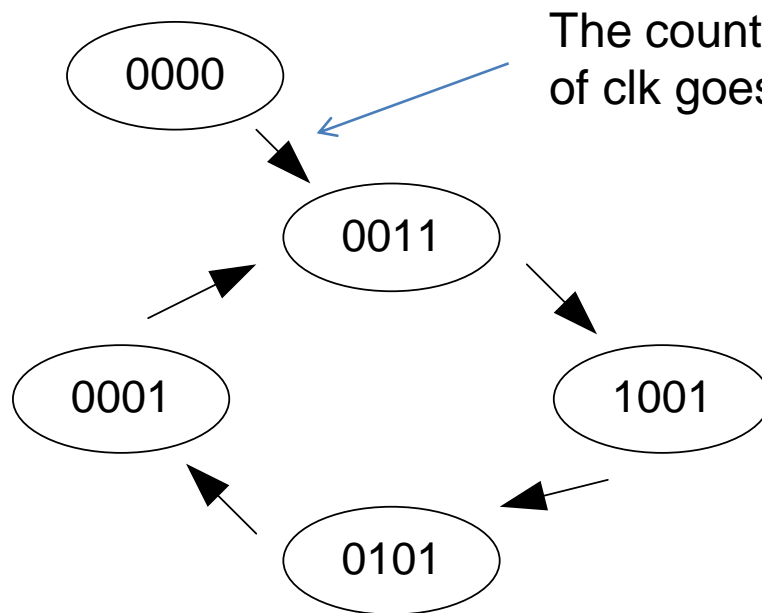
# Design of Synchronous Counters

- Implement the following counter using D Flip-flops and basic gates



The counter starts at 0, at next edge of clk goes to 3

The counter counts with the Sequence of 3-9-5-1

How many D Flip-flops do we need?  
=> 4

Next step: Derive the next state and state transition table

# Design of Synchronous Counters

- Next state and state transition table

Present State				Next State				Output Transition				Flip-flop Inputs			
Q <sub>3</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	Q <sub>3</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	Q <sub>3</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	D <sub>3</sub>	D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>
0	0	0	0	0	0	1	1	0-0	0-0	0-1	0-1	0	0	1	1
0	0	0	1	0	0	1	1	0-0	0-0	0-1	1-1	0	0	1	1
0	0	1	1	1	0	0	1	0-1	0-0	1-0	1-1	1	0	0	1
0	1	0	1	0	0	0	1	0-0	1-0	0-0	1-1	0	0	0	1
1	0	0	1	0	1	0	1	1-0	0-1	0-0	1-1	0	1	0	1

Taking the present state as inputs, use K-Maps to find  $D_3$ ,  $D_2$ ,  $D_1$ , and  $D_0$   
Use don't care conditions when necessary

# Design of Synchronous Counters

Present state  $Q_1Q_0$

$Q_3 Q_2$	$Q_1Q_0$ 00	$Q_1Q_0$ 01	$Q_1Q_0$ 11	$Q_1Q_0$ 10
00	0	0	1	x
01	x	0	x	x
11	x	x	x	x
10	x	0	x	x

K-Map for  $D_3$ 

$$D_3 = Q_1$$

$Q_3 Q_2$	$Q_1Q_0$ 00	$Q_1Q_0$ 01	$Q_1Q_0$ 11	$Q_1Q_0$ 10
00	0	0	0	x
01	x	0	x	x
11	x	x	x	x
10	x	1	x	x

K-Map for  $D_2$ 

$$D_2 = Q_3$$

$Q_3 Q_2$	$Q_1Q_0$ 00	$Q_1Q_0$ 01	$Q_1Q_0$ 11	$Q_1Q_0$ 10
00	1	1	0	x
01	x	0	x	x
11	x	x	x	x
10	x	0	x	x

K-Map for  $D_1$ 

$$D_1 = \overline{Q_3} \cdot \overline{Q_2} \cdot \overline{Q_1}$$

$$= \overline{Q_3 + Q_2 + Q_1}^{10}$$


$Q_3 Q_2$	$Q_1Q_0$ 00	$Q_1Q_0$ 01	$Q_1Q_0$ 11	$Q_1Q_0$ 10
00	1	1	1	x
01	x	1	x	x
11	x	x	x	x
10	x	1	x	x

K-Map for  $D_0$ 

$$D_0 = 1$$

# Design of Synchronous Counters


- Final step: Circuit implementation

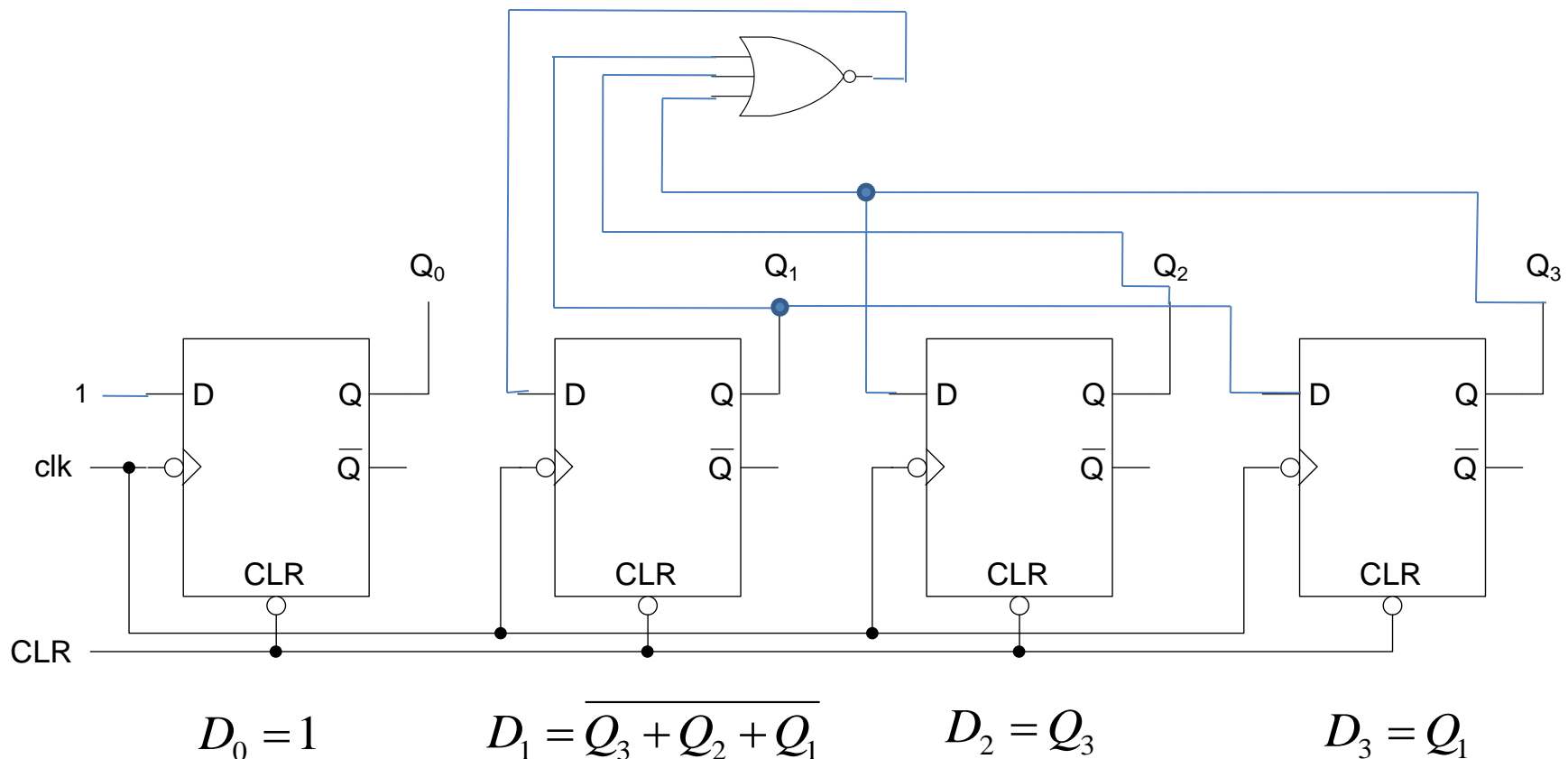


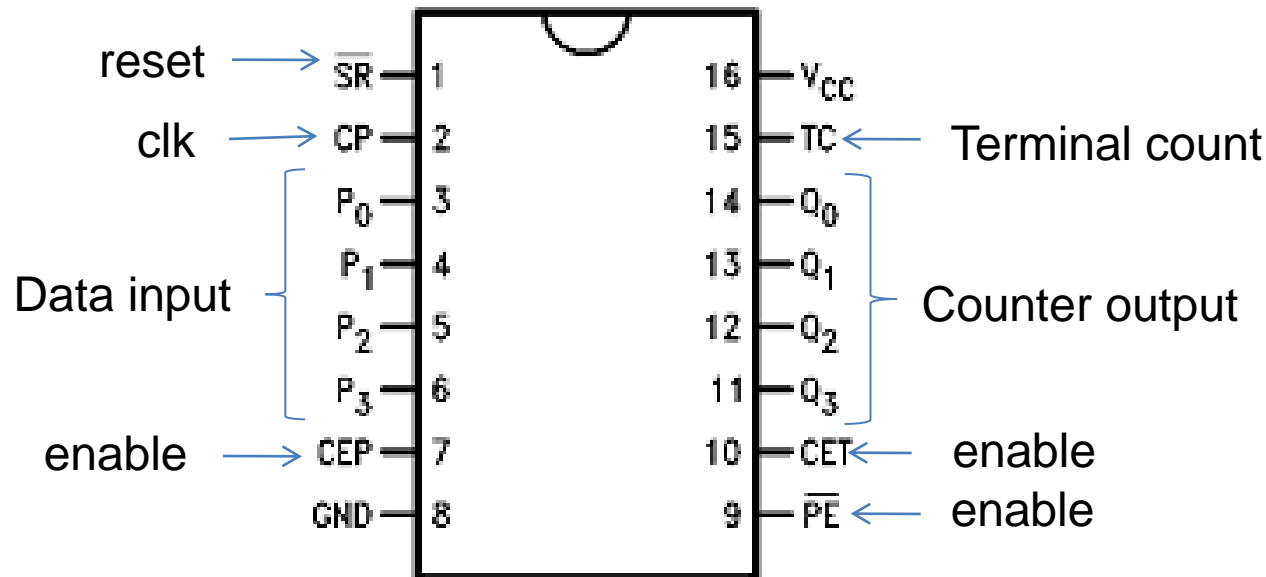
# Counter IC (cont.)

- The 74163 device: 4-bit Synchronous counter
  - Counts from 0 to 15



Refer to datasheet for details