

SEE1223: Digital Electronics

5 – Latches and Flip-Flops

Zulkifil Md Yusof


Dept. of Microelectronics and Computer Engineering
The Faculty of Electrical Engineering
Universiti Teknologi Malaysia

Latches and Flip-Flops

- Introduction to sequential logic
- Latches
 - SR Latch
 - Gated SR Latch
 - Gated D Latch
- Flip-Flops
 - JK Flip-flop
 - D Flip-flop
 - T Flip-flop
 - JK Master-Slave Flip-flop
 - Preset and Clear functions
 - 7474 and 7476 devices

Sequential vs Combinational Logic

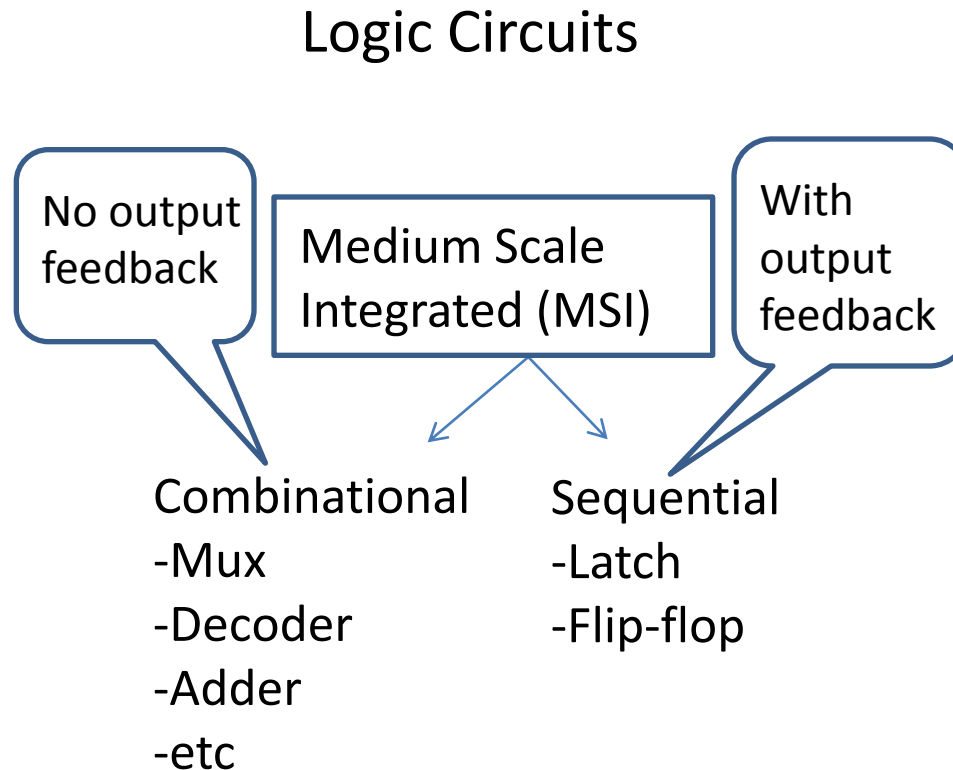- Digital circuits can be categorized into combinational or sequential logic



Latch

- Latch is a type of temporary storage device, where the output feeds back to the input
- It is a basic form of memory, i.e. we can store a value of '1' or '0' in a latch
- Latches however, are considered unstable in modern circuits and rarely used, but crucial in understanding flip-flops
- Flip-flops are the dominant sequential circuit element, and are present in almost all digital systems


SR Latch

- The SR latch (Set-Reset latch) is the most basic type, which can be constructed using NOR or NAND gates
- NOR gate SR latch is an active high input SR latch
- NAND gate SR latch is an active low input SR latch

SR Latch (cont.)

- Active High input SR Latch using NOR gates

Logic circuit

 

Truth table

S R	Q	\bar{Q}
0 0	No change	No change
0 1	0	1
1 0	1	0
1 1	0(invalid)	0(invalid)

When $R = 1$ and $S = 0$, the latch is reset ($Q = 0$)

When $R = 0$ and $S = 1$, the latch is set ($Q = 1$)


When $R = 0$ and $S = 0$, Q and \bar{Q} maintains the previous value

When $R = 1$ and $S = 1$, both Q and \bar{Q} are 0, which is invalid

SR Latch (cont.)

- Active Low input SR Latch using NAND gates

Logic circuit

 

Truth table

S	R	Q	\bar{Q}
0	0	1 (invalid)	1 (invalid)
0	1	1	0
1	0	0	1
1	1	No Change	No Change


When $R = 0$ and $S = 1$, the latch is reset ($Q = 0$)

When $R = 1$ and $S = 0$, the latch is set ($Q = 1$)


When $R = 1$ and $S = 1$, Q and \bar{Q} maintains the previous value

When $R = 0$ and $S = 0$, both Q and \bar{Q} are 1, which is invalid

Gated SR Latch (active high enable)

 

 When $En = 0$ (disable),
 Q and \bar{Q} maintains previous value,
 Regardless of S and R





When $En = 1$ (enable),
 The circuit becomes an active
 High input SR latch


$Q = 1, \bar{Q} = 0$ when $S = 1$ and $R = 0$
 $Q = 0, \bar{Q} = 1$ when $S = 0$ and $R = 1$
 $Q = 1, \bar{Q} = 1$ when $S = 1$ and $R = 1$
 Q, \bar{Q} maintains when $S = 0$ and $R = 0$

Gated SR Latch(cont.)

  
- Draw the output Q for the Gated SR-Latch



Gated D Latch (active high enable)

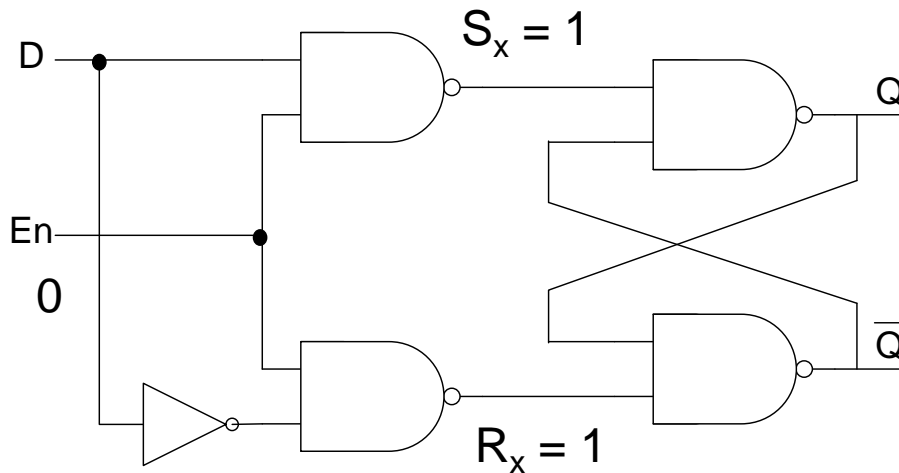

 When $\underline{En} = 0$ (disable),
 Q and \overline{Q} maintains previous value,
 Regardless of D



When $En = 1$ (enable),

$Q = 1, \overline{Q} = 0$ when $D = 1$

$Q = 0, \overline{Q} = 1$ when $D = 0$

Can you derive the truth table of the
 Gated D-latch?

Gated D Latch (cont.)

- Draw the output Q for the Gated D Latch

