

# SEE 3243

## Digital System

**Lecturers :**

**Muhammad Mun'im Ahmad Zabidi**


**Muhammad Nadzir Marsono**

**Kamal Khalil**

***Week 6: Arithmetic Circuits II —  
CLA, Comparators, ALU, Multiplier***




# Full Adder Delay Analysis

 

From A, B to Co for one stage is 4 delays


From Ci to Co is 2 delays for each subsequent stage or  $2n + 2$  for n stages

# Ripple Carry Adder Analysis

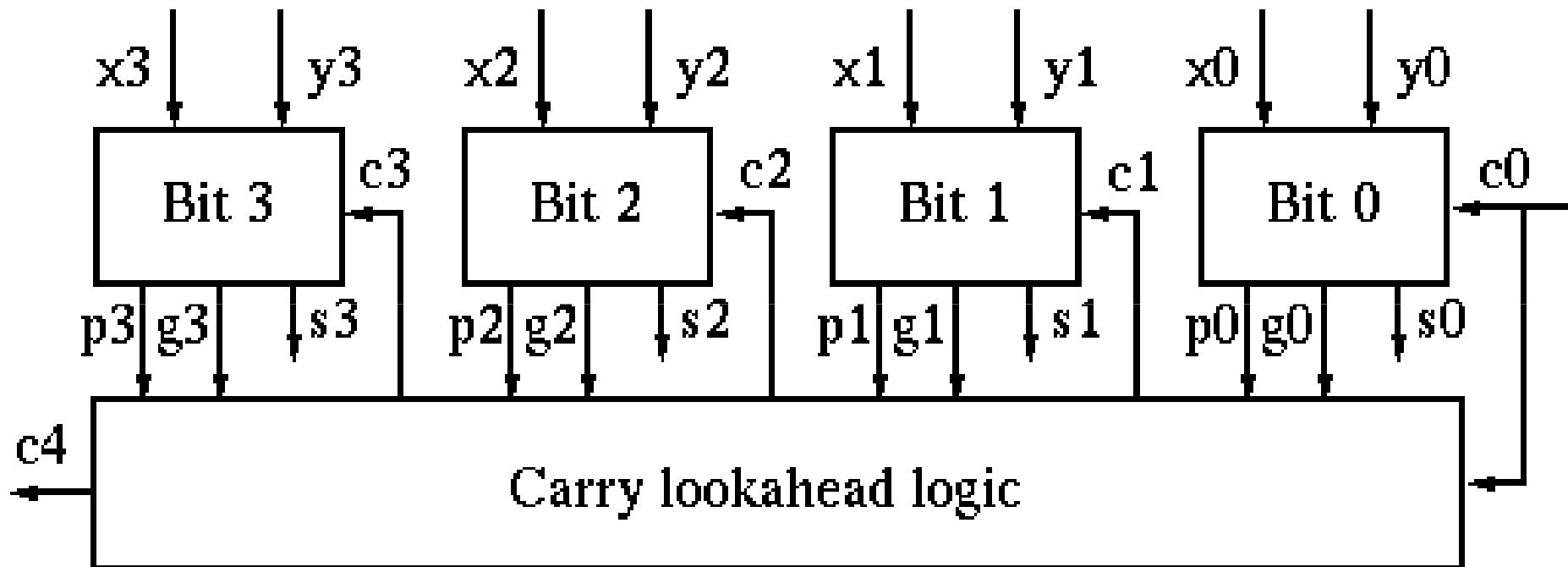

- Total delay for final sum & carry is  $2n+2$  gate delays ( $n = \#$  of stages)
- Assumes XOR is 2 delays
- Delay from  $C_i$  to  $C_{i+1}$  is 2 gate delays (except stage 0, where delay is 4 units)

# Carry Lookahead Adder Analysis

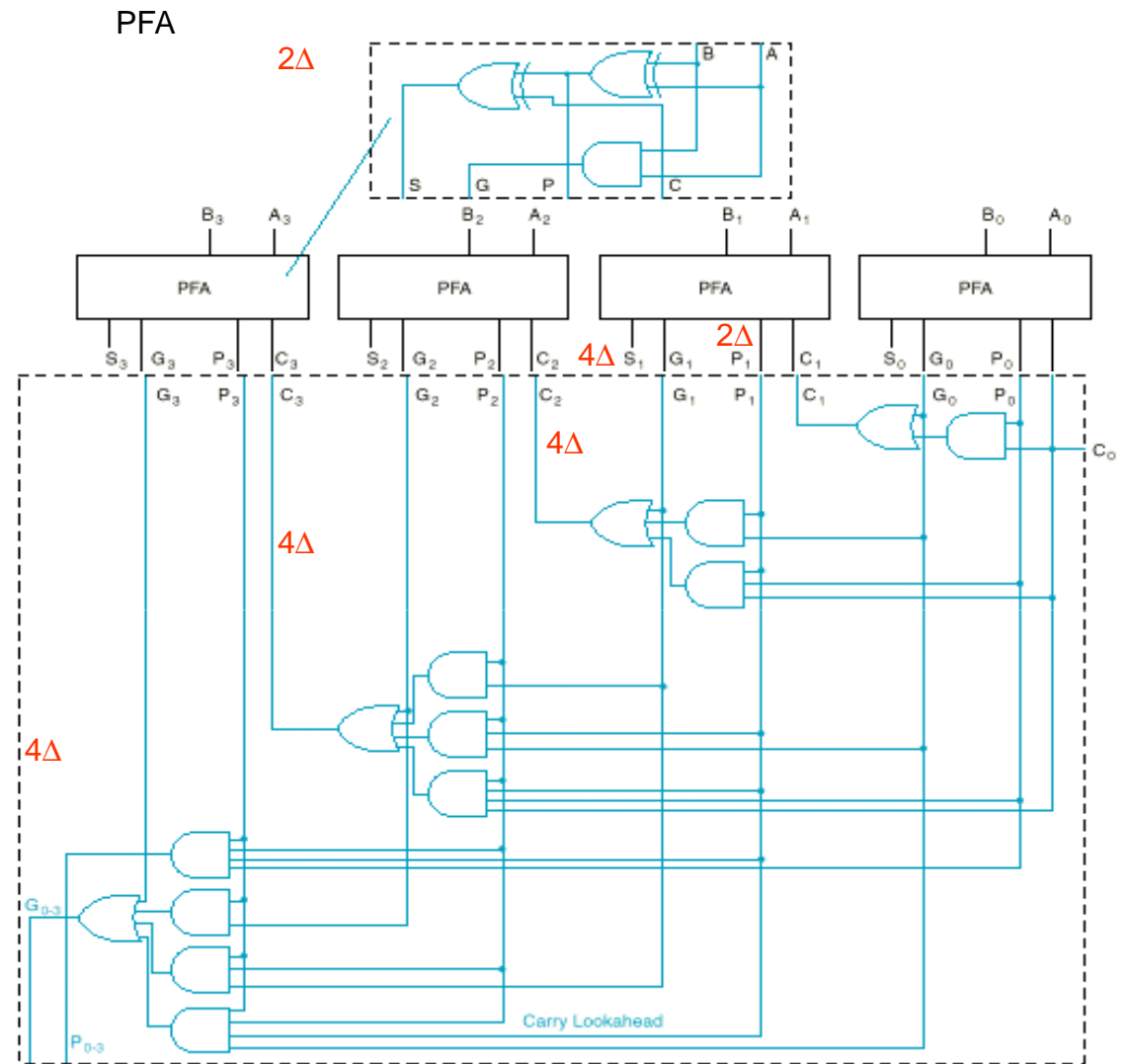

$6\Delta$   $5\Delta$

If we reduce the time to compute  $C_3$ , we can reduce delay to get  $S_3$  (final sum) to 6 gate delays

# Carry Lookahead Logic Derivation

Carry Generate  $G_i = A_i B_i$       *must generate carry when  $A = B = 1$*

Carry Propagate  $P_i = A_i \text{ xor } B_i$

Sum and Carry can be reexpressed in terms of generate/propagate:

$$S_i = A_i \text{ xor } B_i \text{ xor } C_i = P_i \text{ xor } C_i$$

$$\begin{aligned} C_{i+1} &= A_i B_i + A_i C_i + B_i C_i \\ &= A_i B_i + (A_i + B_i) C_i \\ &= A_i B_i + (A_i \text{ xor } B_i) C_i \\ &= G_i + P_i C_i \end{aligned}$$

# Carry Lookahead Logic

- Reexpress the carry logic as follows:

$$C_1 = G_0 + P_0 C_0$$

$$C_2 = G_1 + P_1 C_1$$

$$= G_1 + P_1 G_0 + P_1 P_0 C_0$$

$$C_3 = G_2 + P_2 C_2$$


$$= G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$$

$$C_4 = G_3 + P_3 C_3$$

$$= G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0$$


- Variables are the adder inputs and  $C_0$  (carry in to stage 0)!

# Structure of One Stage in CLA

 

- To compute  $S_i$ , only  $x_{i-1} \dots x_0, y_{i-1} \dots y_0$  and  $c_0$  are needed.
- No need to wait for  $c_{i-1}$

# Alternative CLA Design

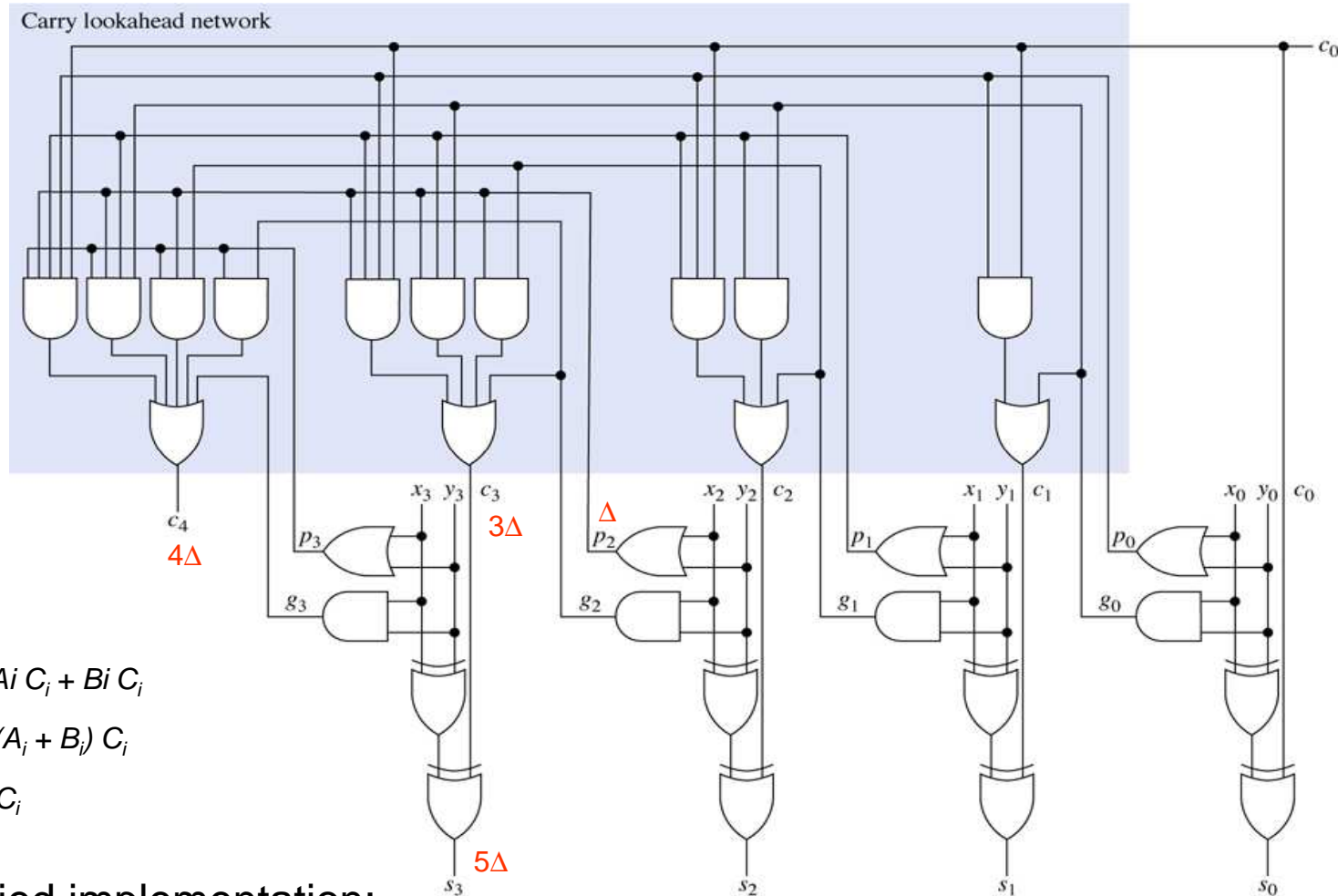

$$\begin{aligned}
 C_{i+1} &= A_i B_i + A_i C_i + B_i C_i \\
 &= A_i B_i + (A_i + B_i) C_i \\
 &= G_i + P_i C_i
 \end{aligned}$$



A modified implementation:

$P_i$  computed using OR gates (slightly faster)



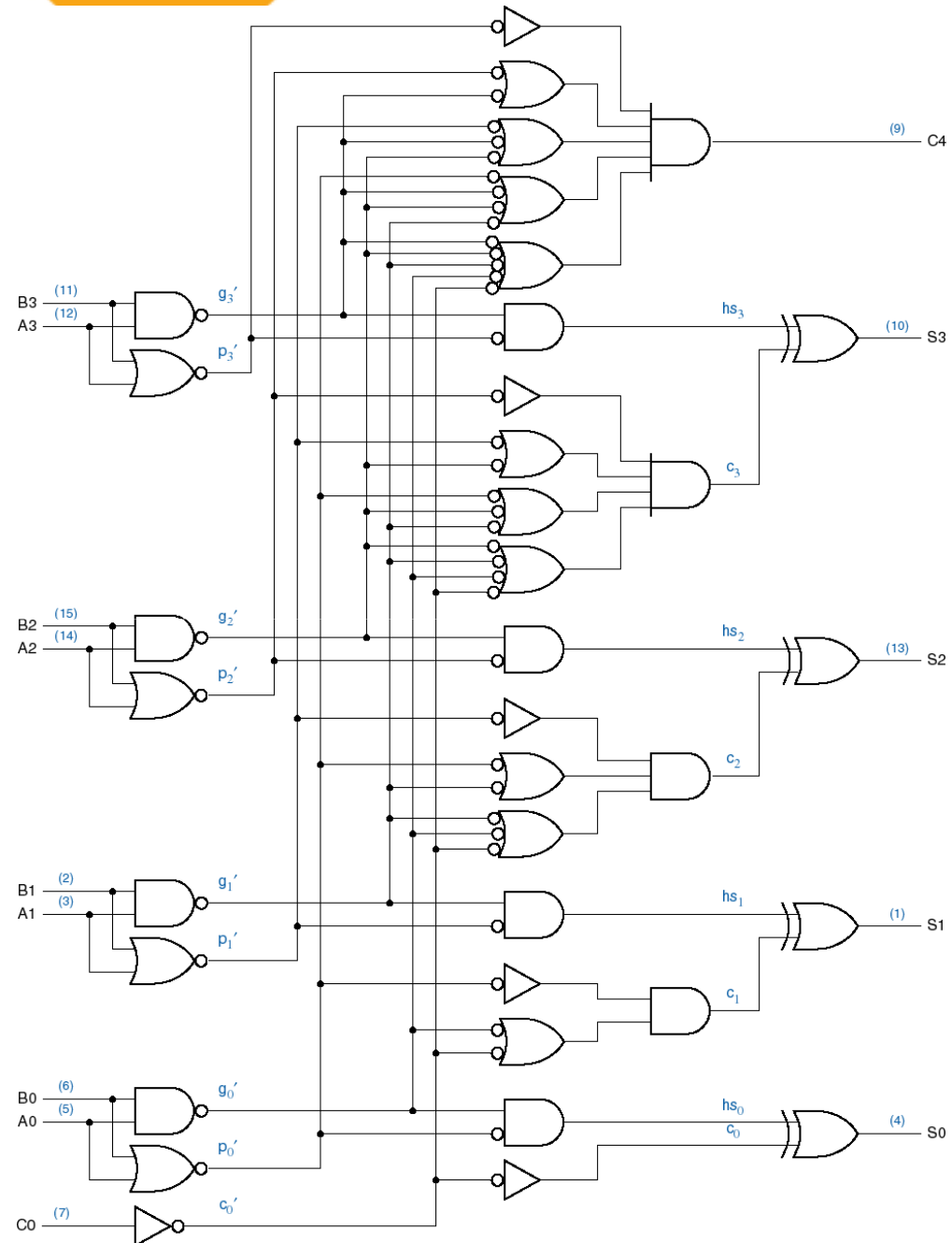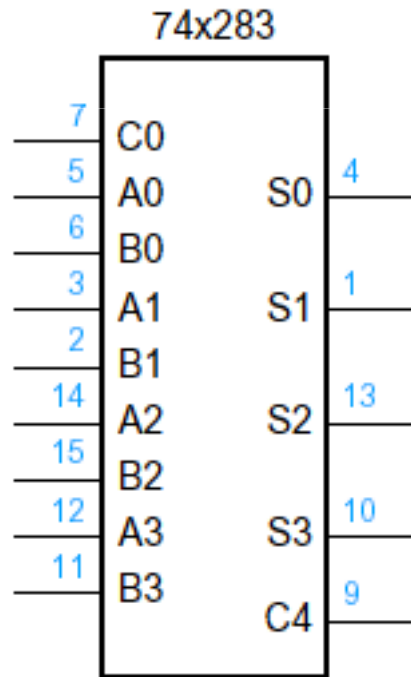
# 74x283

- 4-bit adder
- Uses carry lookahead internally



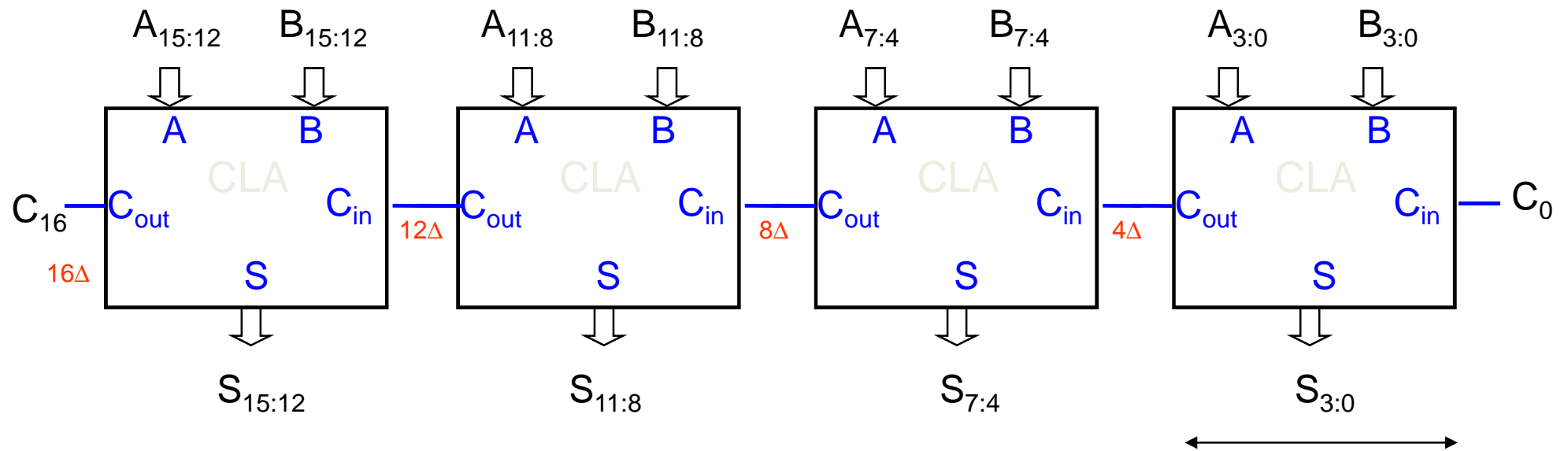
# Cascading CLA

- Similar to ripple adder, but different latency



Delay of each stage  
is 4 gate levels instead  
of 10 for ripple adders


# Hierarchical Carry Lookahead

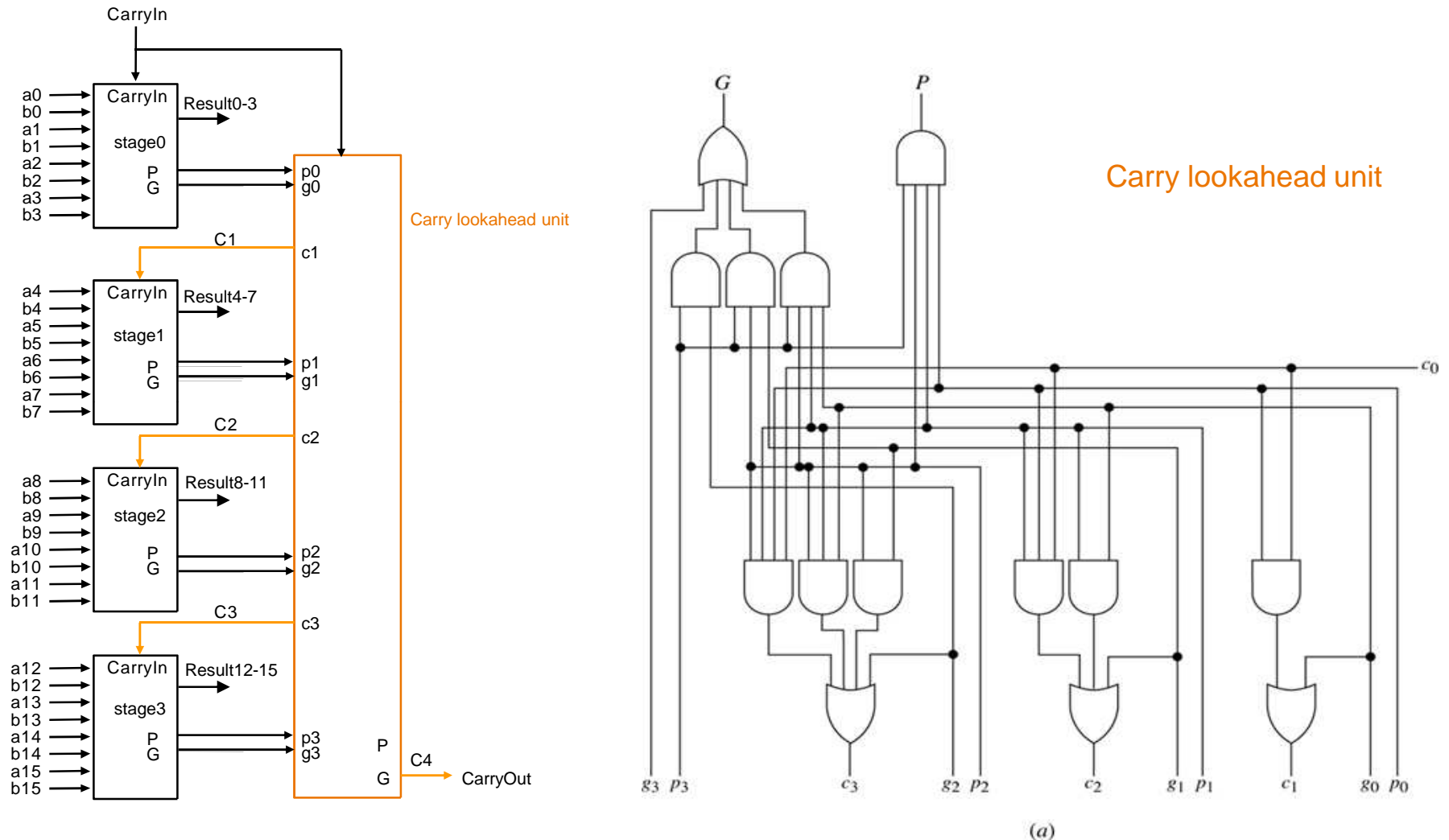

- Second level carry lookahead unit – extends lookahead to 16 bits
- If extended to 64 bits – reduces gate delay from 130 to 14, or improved by a factor of 9

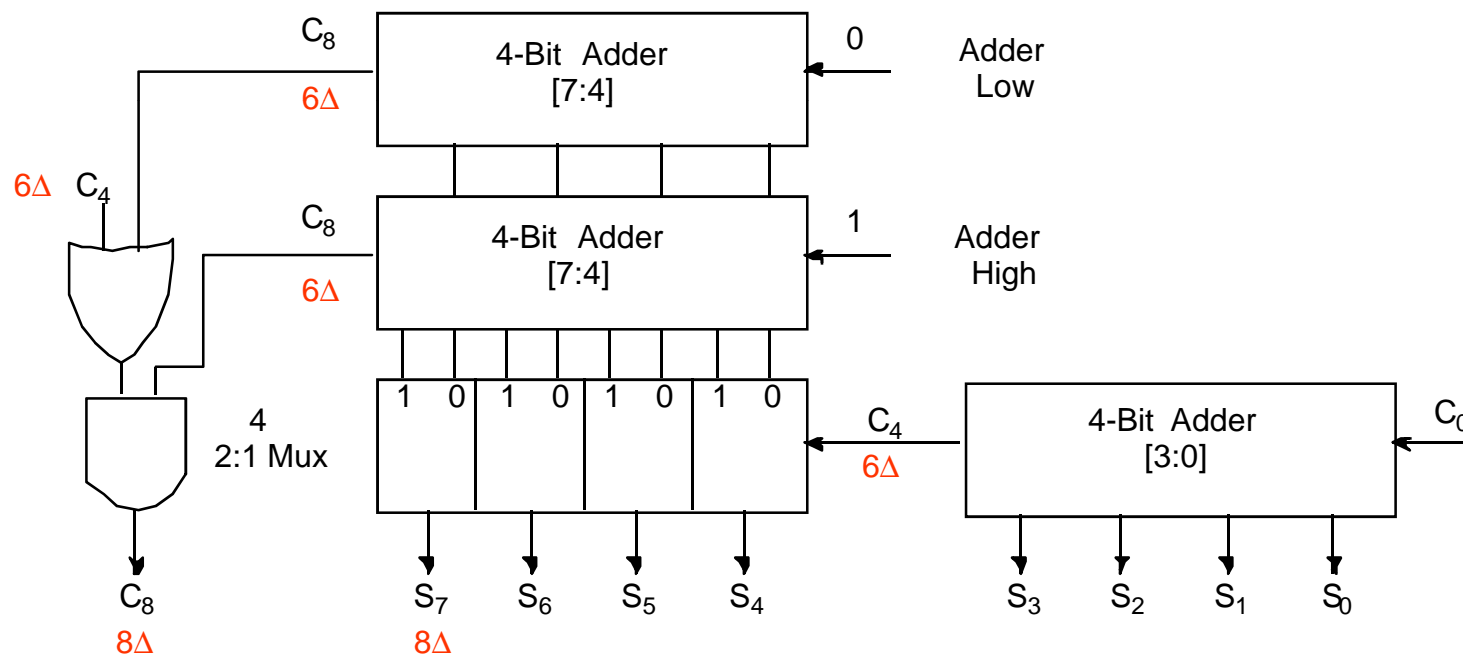
# Carry Select Adder

- Redundant hardware to make carry calculation go faster
- Compute the high order sums in parallel
  - one addition assumes carry in = 0
  - the other assumes carry in = 1




# Equality Comparators



1-bit comparator

 


4-bit comparator

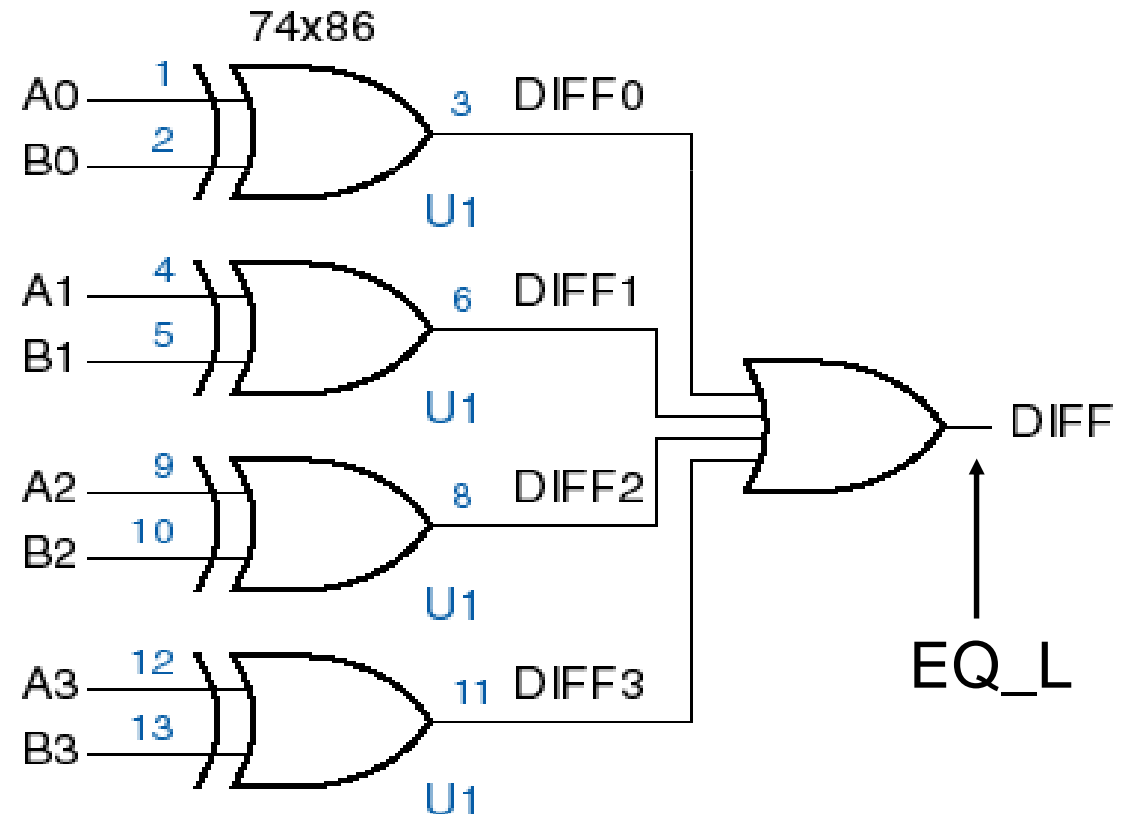

# 8-bit Magnitude Comparator

 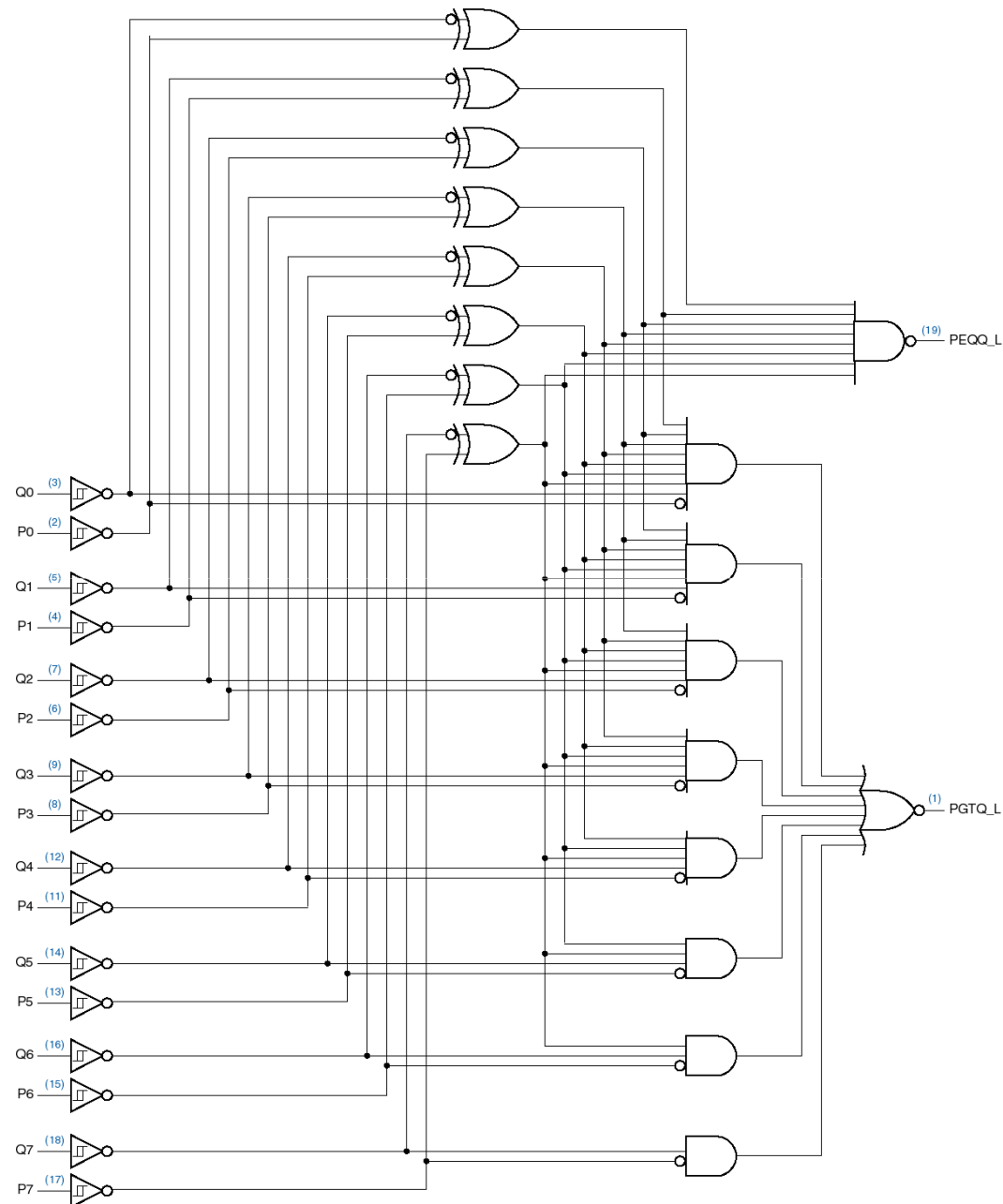


# Iterative Comparator

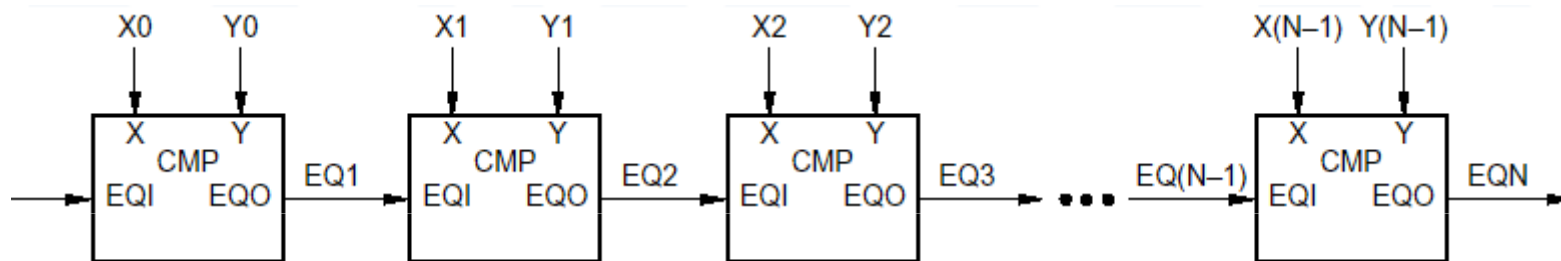
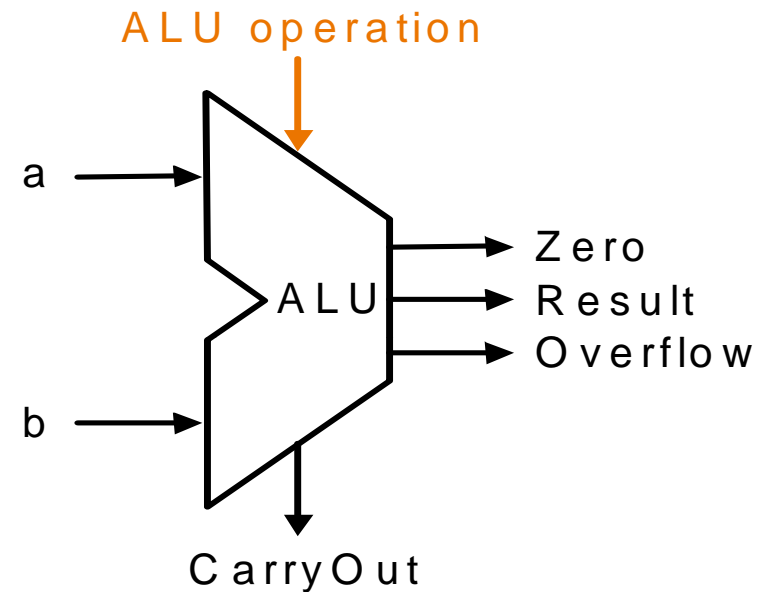
# Arithmetic Logic Unit

- Basic building block of every CPU.
- Combinational circuit.
- Does integer addition, subtraction.
- Also does all 16 bitwise logical operations.
- Does not do multiply, divide. They would be implemented either by a separate unit, or subroutines (slow but cheap).
- Floating operations are also one or more separate units. (More: faster, costlier.)
- Why combine arithmetic & logic?  
They share a lot of circuitry.




*Common symbol for ALU*



# Sample ALU 1: Mux Approach

**Start with  
Simple  
Logical  
Operations**

1. AND gate ( $c = a \cdot b$ )

 

a	b	$c = a \cdot b$
0	0	0
0	1	0
1	0	0
1	1	1


2. OR gate ( $c = a + b$ )



a	b	$c = a + b$
0	0	0
0	1	1
1	0	1
1	1	1
 
## Sample ALU 1

*Use 2:1 MUX to choose 1 of 2 logical operations*




If Operation is 0, then Result = a AND b

If Operation is 1, then Result = a OR b
 
# Sample ALU 1

*Now add Full Adder for arithmetic*


If Op is 0, then Result = a AND b  
If Op is 1, then Result = a OR b  
If Op is 2, then Result = sum of (a + b + CarryIn)


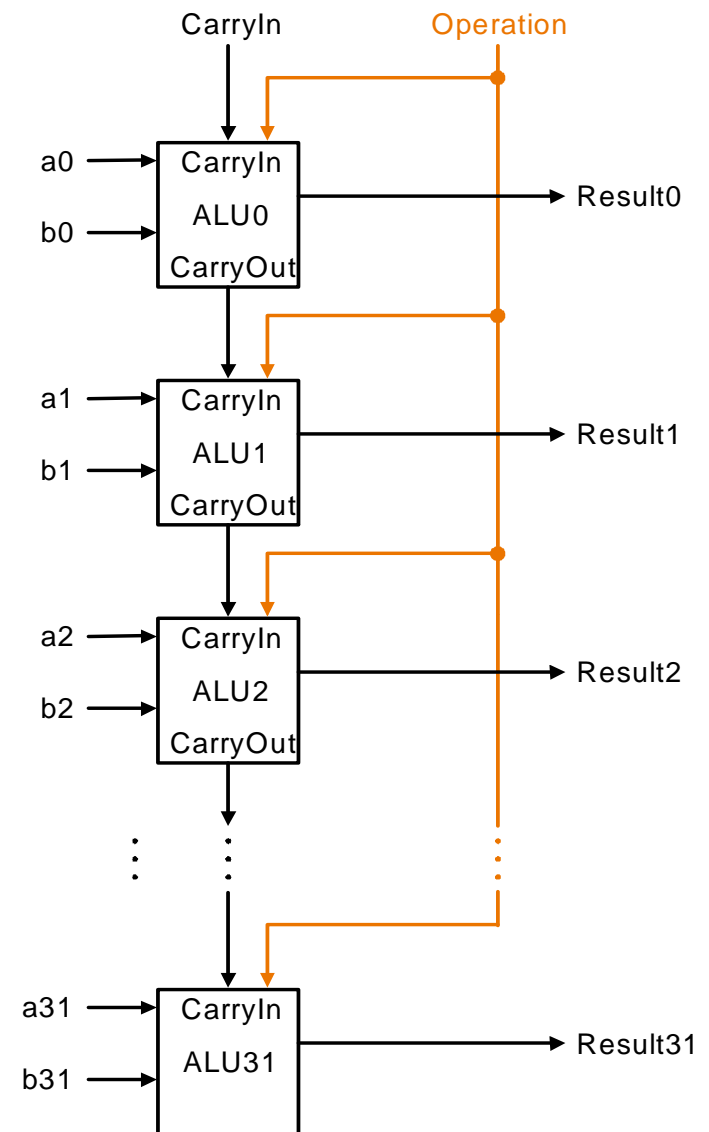
# Sample ALU 1

Repeat the 1-bit ALU 32 times


If Op is 0, then  $\text{Result}_i = a_i \text{ AND } b_i$   
 If Op is 1, then  $\text{Result}_i = a_i \text{ OR } b_i$   
 If Op is 2, then  $\text{Result}_i = \text{sum of } (a_i + b_i)$


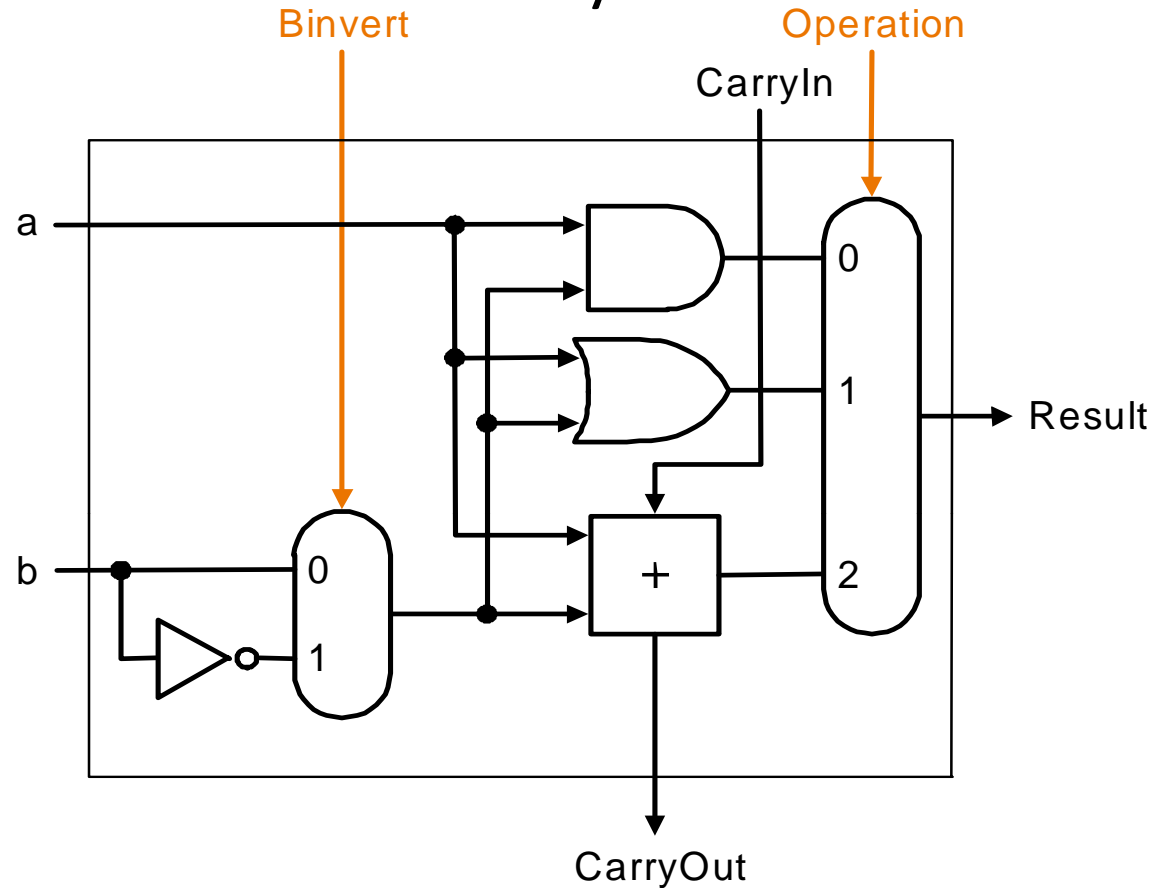
# ALU 1 with Subtraction Ability

If Op is 0, then Result = a AND b  
 If Op is 1, then Result = a OR b

If Op is 2,  
 and if Binvert is 0,  
 then Result = sum (a + b)  
 if Binvert is 1,  
 then Result = sum (a + (-b))




Note that (- b) is 1's comp

Add a 1 into Carryin<sub>0</sub> to get 2's comp

# ALU 1 with Zero Detection

Control Lines	Function
000	and
001	or
010	add
110	sub

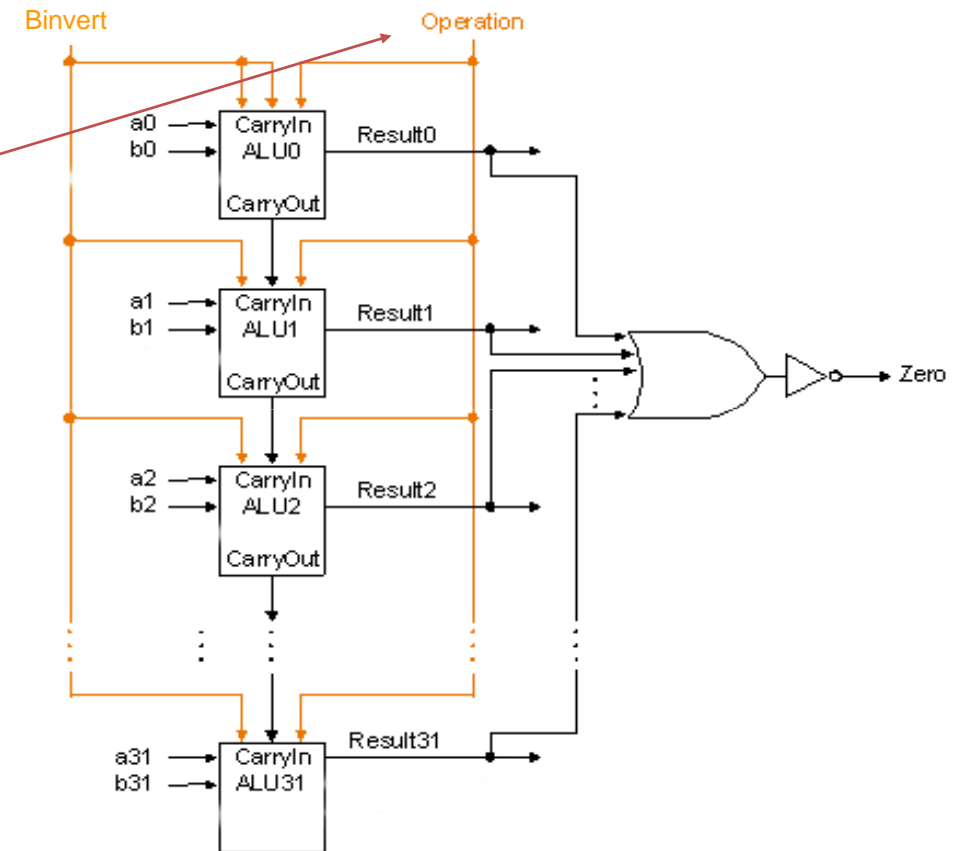

# Sample ALU 2: Truth Table Approach

We want to design an ALU which can do the following operations:

$m_1$	$m_0$	Operation
0	0	A plus B
0	1	A minus B
1	0	A plus 1
1	1	A nor B

Assume inputs A and B are 4-bit 2's complement numbers, and F is output.

One way of obtaining the circuit is by creating the truth table:


$m_1$	$m_0$	$a_3$	$a_2$	$a_1$	$a_0$	$b_3$	$b_2$	$b_1$	$b_0$	$f_3$	$f_2$	$f_1$	$f_0$	
0	0	0	0	0	0	0	0	0	0	0	0	0	0	
0	0	0	0	0	0	0	0	0	1	0	0	0	1	A plus B
0	0	0	0	0	0	0	0	1	0	0	0	1	0	
.	.	.	.	.	.	.	.	.	.	.	.	.	.	
1	1	1	1	1	1	1	1	1	0	0	0	0	0	
1	1	1	1	1	1	1	1	1	1	0	0	0	0	A nor B

A huge truth table. Imagine truth table for 8-bit inputs!

# Sample ALU 2

- Design a universal logic block (called a bit slice) that accepts only 1-bit of the inputs (per logic block).
- We then copy and connect this bit slice as many times as there are input bits.

$m_1$	$m_0$	Operation
0	0	A plus B
0	1	A minus B
1	0	A plus 1
1	1	A nor B

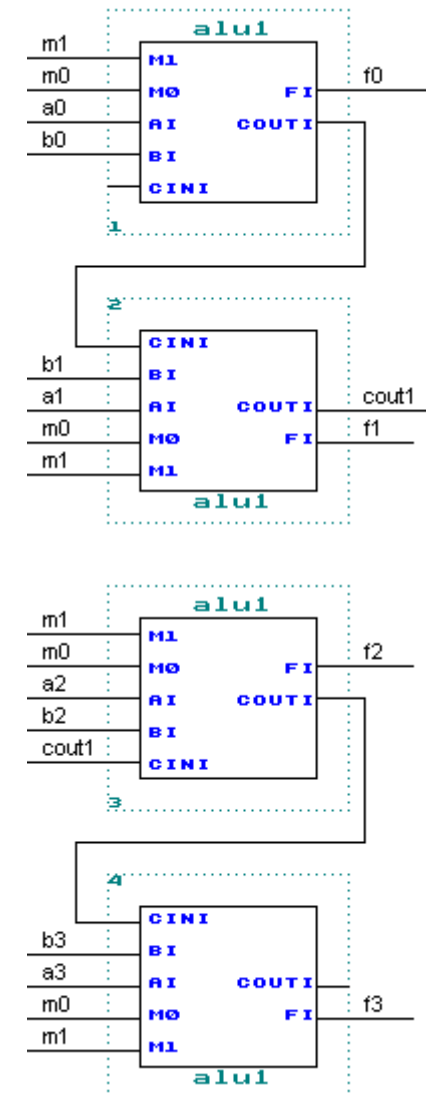



# Sample ALU 2


- Each bit slice has 5 inputs and 2 outputs. Truth table is on the right.
- Remember, the bit slice circuit is universal, i.e. exactly same circuit for all input bits.
- For A plus 1 operation for example, we don't need B input. But remember, it must be universal. Other operations require B input.
- Another example: NOR operation doesn't requirecini input, but the truth table for NOR operation must havecini input.

$m_1$	$m_0$	Operation
0	0	A plus B
0	1	A minus B
1	0	A plus 1
1	1	A nor B

	$m_1$	$m_0$	$a_i$	$b_i$	$c_{ini}$	$f_i$	$c_{outi}$
	0	0	0	0	0	0	0
			0	0	1	1	0
			0	1	0	1	0
A tambah B			0	1	1	0	1
			1	0	0	1	0
			1	0	1	0	1
			1	1	0	0	1
			1	1	1	1	1
	0	1	0	0	0	1	0
			0	0	1	0	1
			0	1	0	0	0
			0	1	1	1	0
A tolak B			1	0	0	0	1
			1	0	1	1	1
			1	1	0	1	0
			1	1	1	0	1
	1	0	0	0	0	0	0
			0	0	1	1	0
			0	1	0	0	0
			0	1	1	1	0
A tambah 1			1	0	0	1	0
			1	0	1	0	1
			1	1	0	1	0
			1	1	1	0	1
	1	1	0	0	X	1	X
A NOR B			0	1	X	0	X
			1	X	X	0	X


# Sample ALU 2

## Bit Slice Circuit for Sample ALU 2

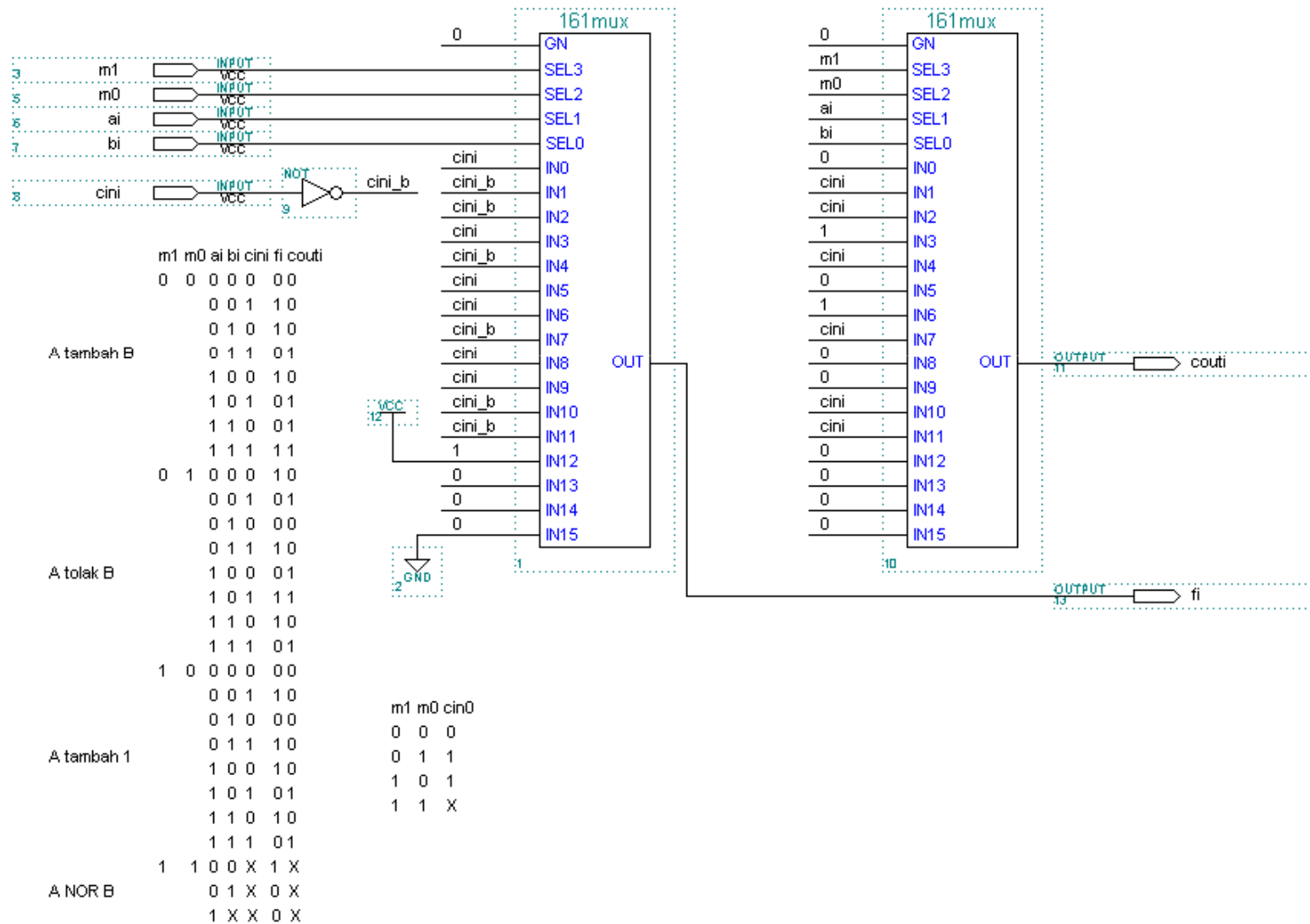
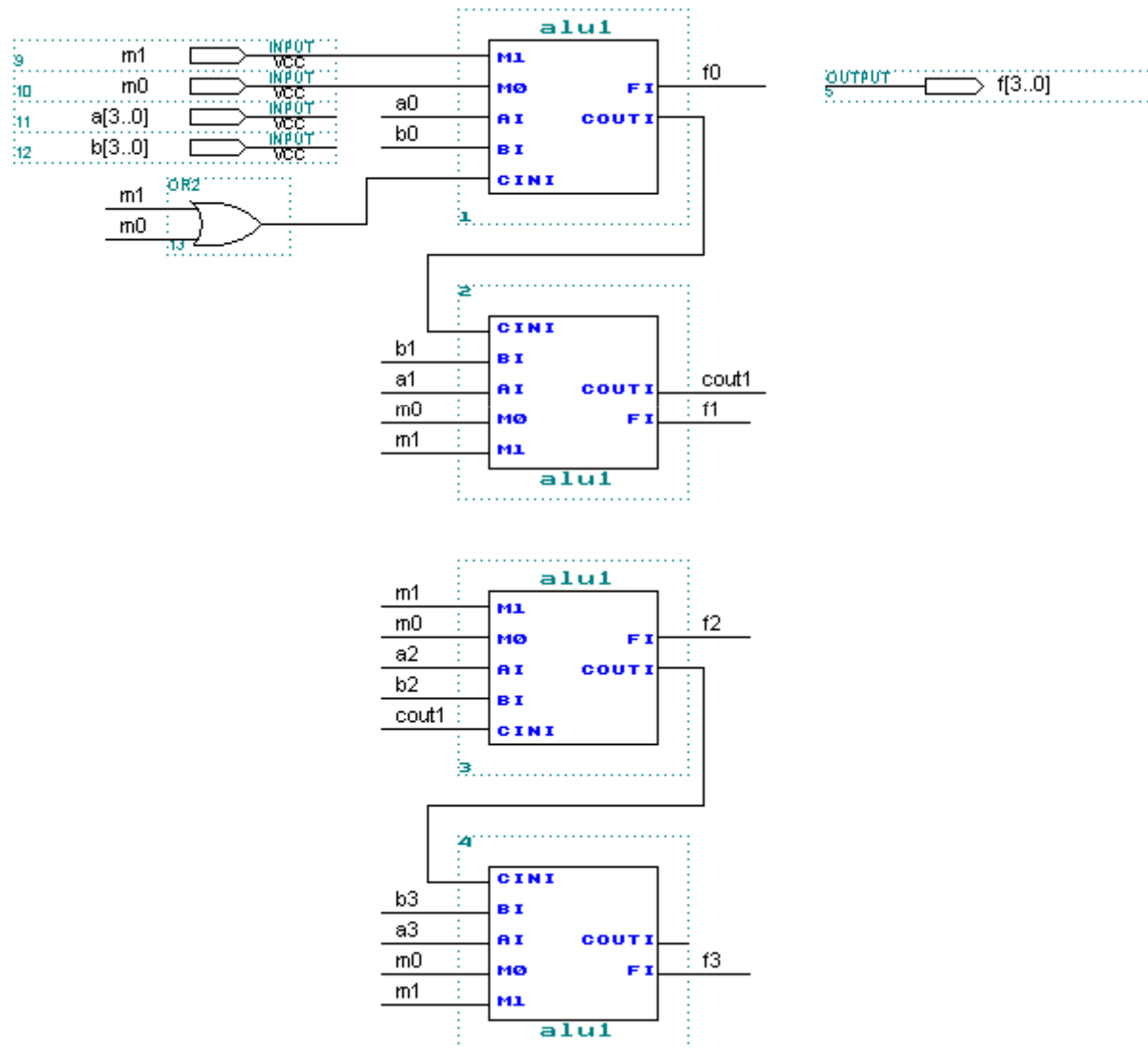
# Sample ALU 2

*Circuit for Sample ALU 2 for 4-Bit Inputs*




# 74x181 TTL ALU

Selection				M = 1	M = 0, Arithmetic Functions	
S3	S2	S1	S0	Logic Function	Cn = 0	Cn = 1
0	0	0	0	$F = \text{not } A$	$F = A \text{ minus } 1$	$F = A$
0	0	0	1	$F = A \text{ nand } B$	$F = A B \text{ minus } 1$	$F = A B$
0	0	1	0	$F = (\text{not } A) + B$	$F = A (\text{not } B) \text{ minus } 1$	$F = A (\text{not } B)$
0	0	1	1	$F = 1$	$F = \text{minus } 1$	$F = \text{zero}$
0	1	0	0	$F = A \text{ nor } B$	$F = A \text{ plus } (A + \text{not } B)$	$F = A \text{ plus } (A + \text{not } B) \text{ plus } 1$
0	1	0	1	$F = \text{not } B$	$F = A B \text{ plus } (A + \text{not } B)$	$F = A B \text{ plus } (A + \text{not } B) \text{ plus } 1$
0	1	1	0	$F = A \text{ xnor } B$	$F = A \text{ minus } B \text{ minus } 1$	$F = (A + \text{not } B) \text{ plus } 1$
0	1	1	1	$F = A + \text{not } B$	$F = A + \text{not } B$	$F = A \text{ minus } B$
1	0	0	0	$F = (\text{not } A) B$	$F = A \text{ plus } (A + B)$	$F = A \text{ plus } (A + B) \text{ plus } 1$
1	0	0	1	$F = A \text{ xor } B$	$F = A \text{ plus } B$	$F = A \text{ plus } B \text{ plus } 1$
1	0	1	0	$F = B$	$F = A (\text{not } B) \text{ plus } (A + B)$	$F = A (\text{not } B) \text{ plus } (A + B) \text{ plus } 1$
1	0	1	1	$F = A + B$	$F = (A + B)$	$F = (A + B) \text{ plus } 1$
1	1	0	0	$F = 0$	$F = A$	$F = A \text{ plus } A \text{ plus } 1$
1	1	0	1	$F = A (\text{not } B)$	$F = A B \text{ plus } A$	$F = AB \text{ plus } A \text{ plus } 1$
1	1	1	0	$F = A B$	$F = A (\text{not } B) \text{ plus } A$	$F = A (\text{not } B) \text{ plus } A \text{ plus } 1$
1	1	1	1	$F = A$	$F = A$	$F = A \text{ plus } 1$


- Due to arithmetic equivalence, active HIGH or active LOW input and outputs are available!
- Not all operations useful, but fall out when doing the useful ones

# 74x181 TTL ALU

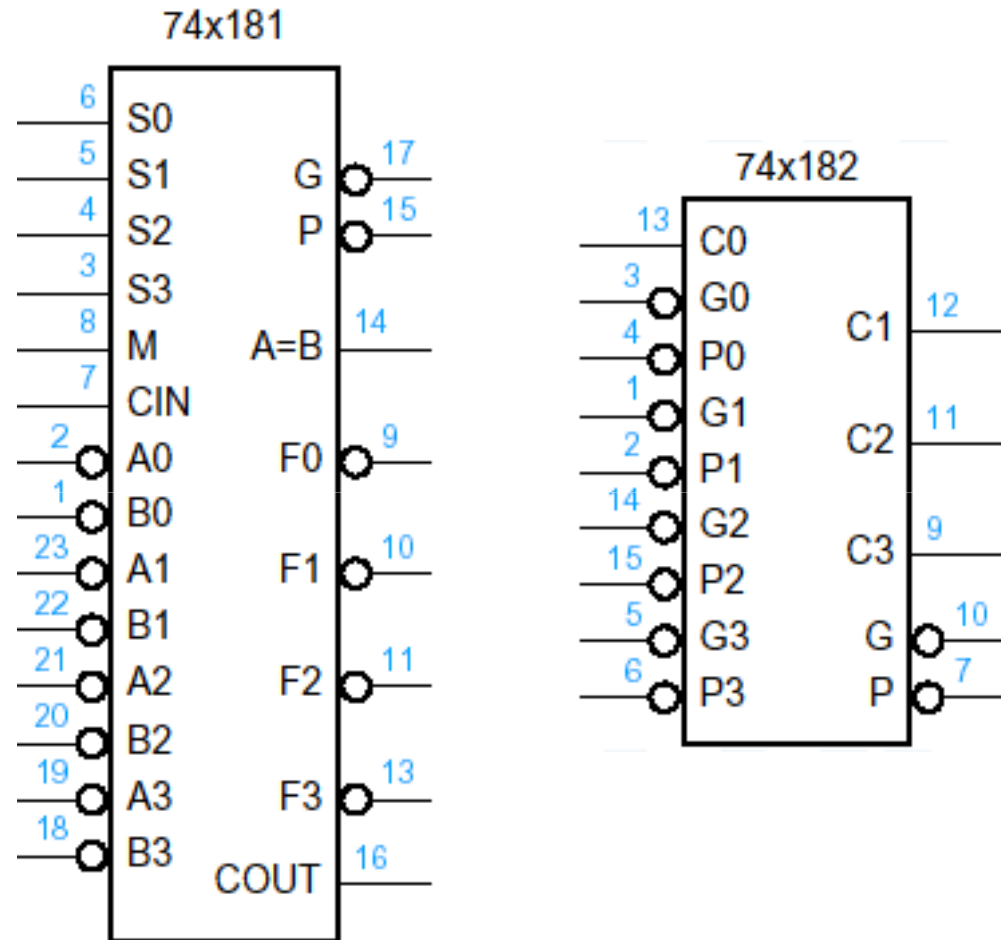

 
# 16-bit ALU with Carry Lookahead Unit

CLA unit speeds up calculations of multi-chip ALU



# 74x381 and 74x382 ALUs

Inputs			Function
S2	S1	S0	
0	0	0	$F = 0000$
0	0	1	$F = B \text{ minus } A \text{ minus } 1 \text{ plus } \text{CIN}$
0	1	0	$F = A \text{ minus } B \text{ minus } 1 \text{ plus } \text{CIN}$
0	1	1	$F = A \text{ plus } B \text{ plus } \text{CIN}$
1	0	0	$F = A \oplus B$
1	0	1	$F = A + B$
1	1	0	$F = A \cdot B$
1	1	1	$F = 1111$

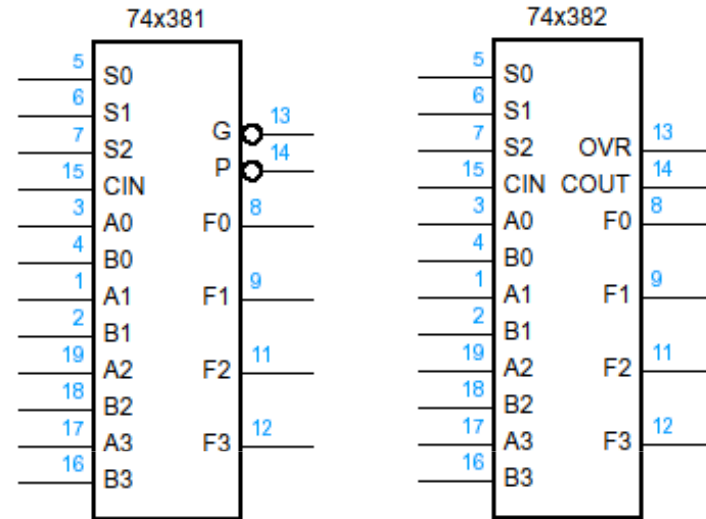

- Compared to 74x181, these ALUs encode their select inputs more compactly, and provide only eight different but useful functions
- The difference?
  - 74x381 provides **group carry lookahead** outputs
  - 74x382 provides **ripple carry-out** and **overflow** outputs

# Combinational Multiplier

- Product of 2 4-bit numbers is an 8-bit number
- Product of m-bit x n-bit numbers is an (m+n)-bit number

				$A_3$	$A_2$	$A_1$	$A_0$
				$B_3$	$B_2$	$B_1$	$B_0$
				$A_3B_0$	$A_2B_0$	$A_1B_0$	$A_0B_0$
			$A_3B_1$	$A_2B_1$	$A_1B_1$	$A_0B_1$	
		$A_3B_2$	$A_2B_2$	$A_1B_2$	$A_0B_2$		
	$A_3B_3$	$A_2B_3$	$A_1B_3$	$A_0B_3$			
$S_7$	$S_6$	$S_5$	$S_4$	$S_3$	$S_2$	$S_1$	$S_0$

Partial products

				1	1	0	1	(13) multiplicand
			X	1	0	1	1	(11) multiplier
				1	1	0		
			1	1	0	1		
		0	0	0	0			
	1	1	0	1				
1	0	0	0	1	1	1	1	(143) product



# Combinational Multiplier

		$B_1$	$B_0$
	$A_1$	$A_0 B_1$	$A_0 B_0$
	$A_1 B_1$	$A_1 B_0$	
$C_3$	$C_2$	$C_1$	$C_0$



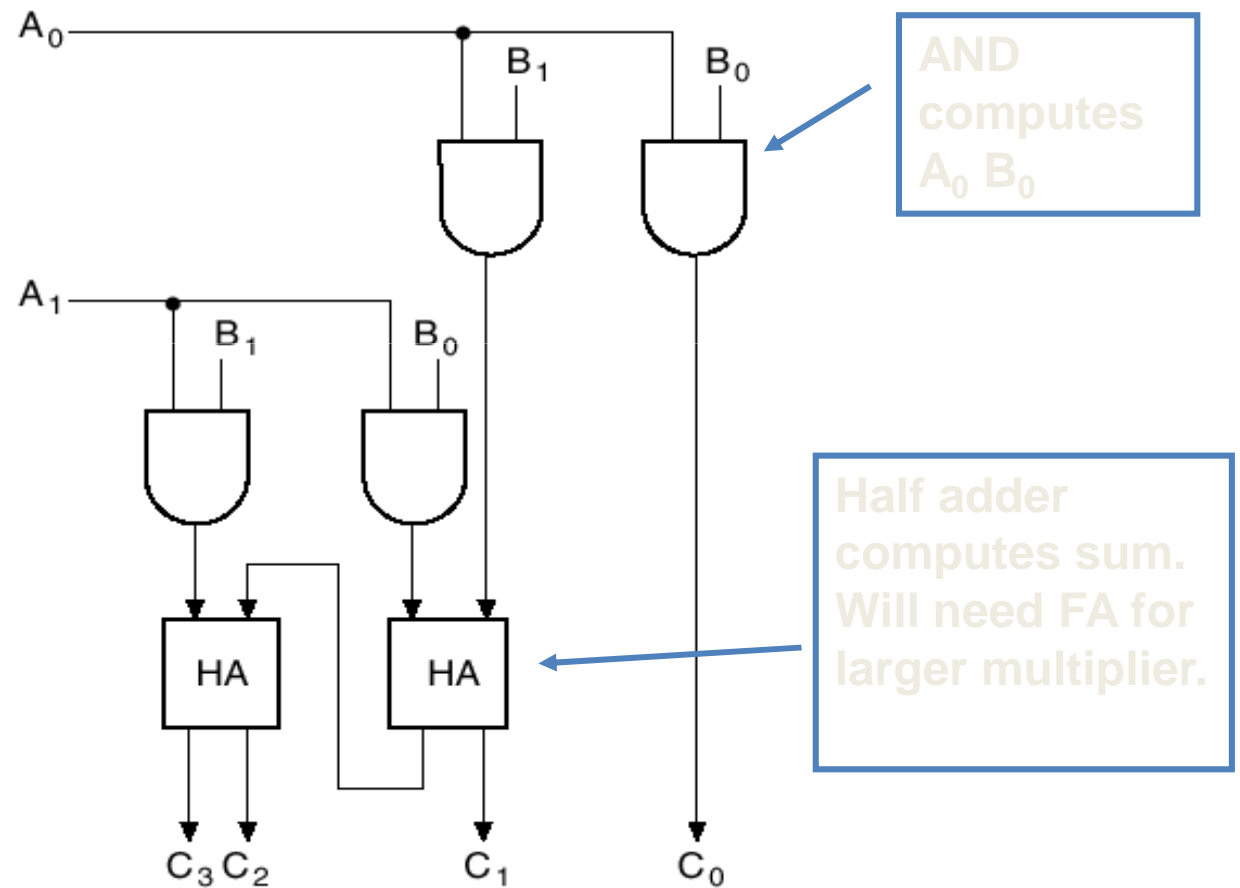


Fig. 3-33 A 2-Bit by 2-Bit Binary Multiplier

# Basic Idea of A Larger Multiplier

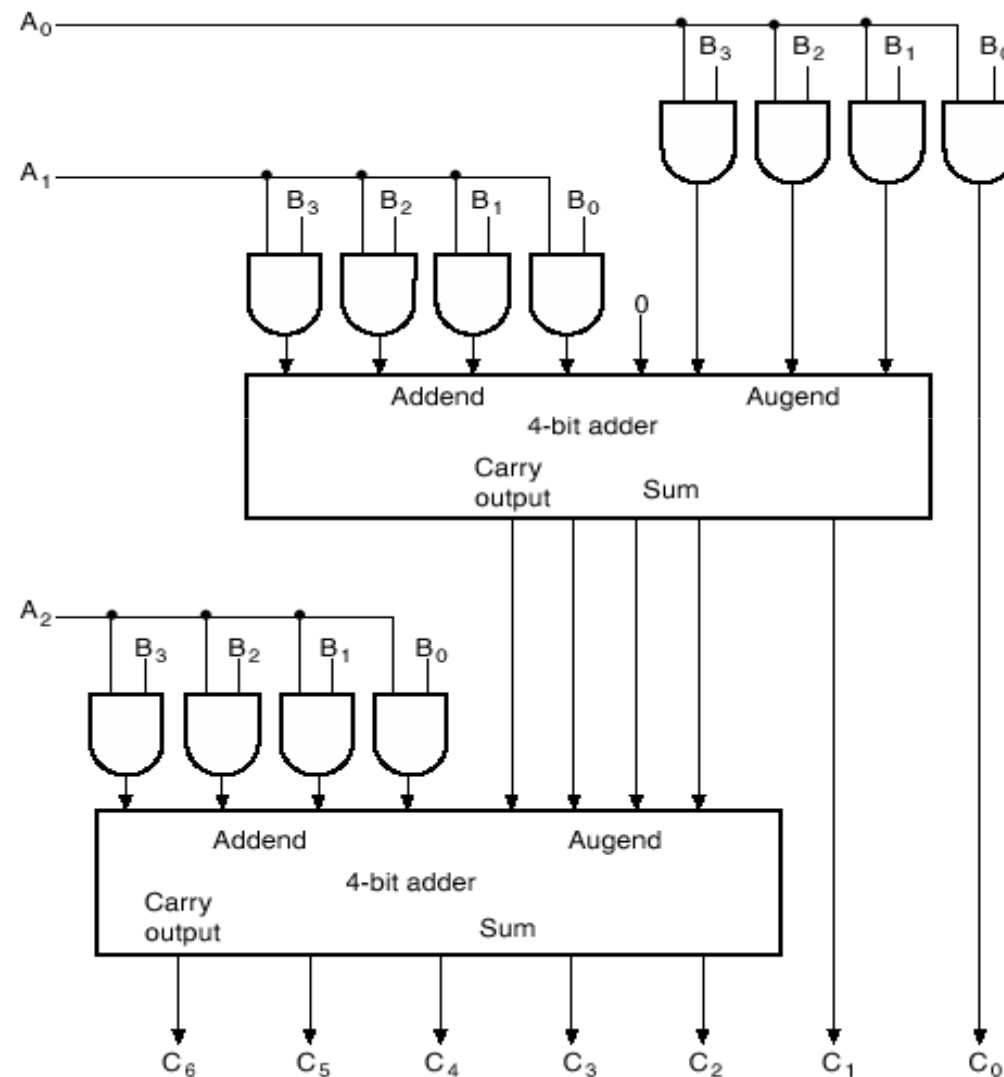

# 4x4 Combinational Multiplier

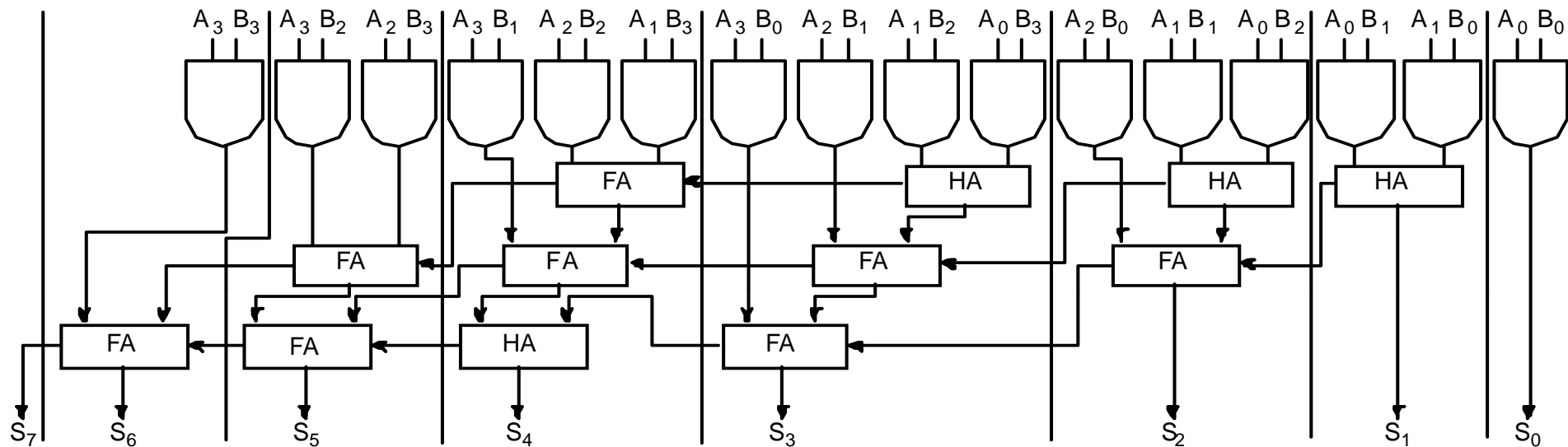

Note use of parallel carry-outs to form higher order sums


12 Adders, if full adders, this is 6 gates each = 72 gates

16 gates form the partial products


total = 88 gates!

# Combinational Multiplier

*Another Representation of the Circuit*

 

Building block: full adder + and

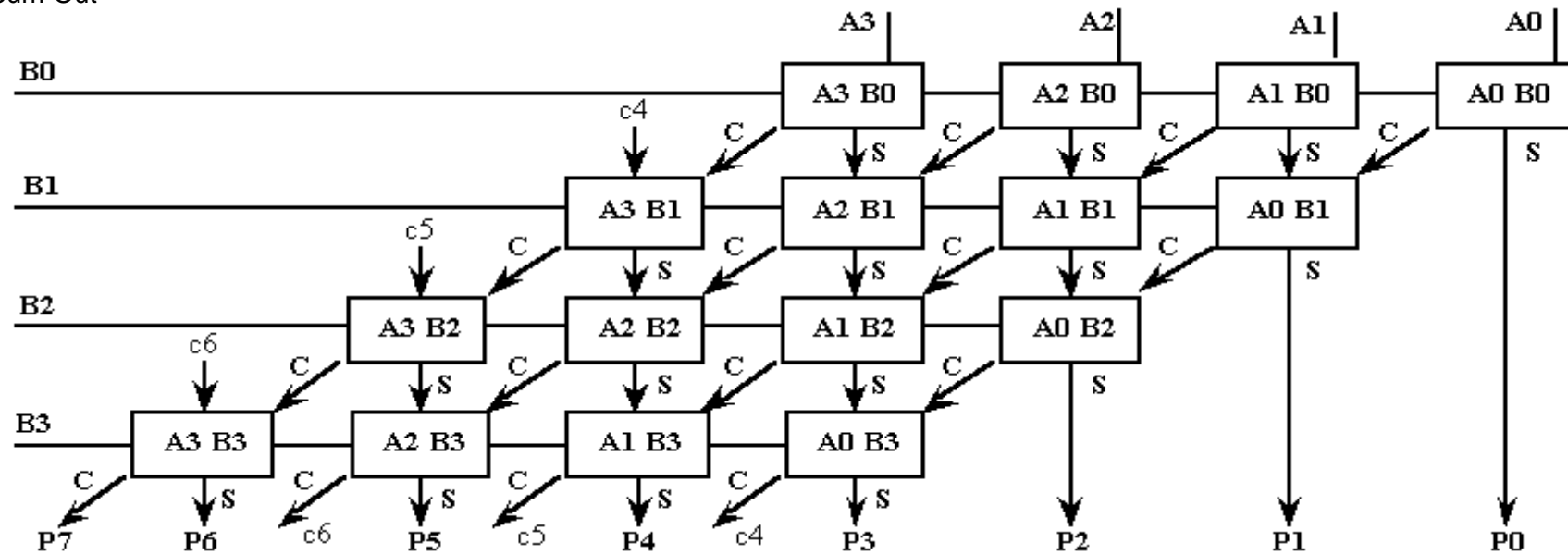

4 x 4 array of building blocks