

INDUSTRIAL ELECTRONICS

DDPE 3103


TOPIC 1

SWITCHING CIRCUITS

PROF MADYA DR MORINA ABDULLAH | ENCIK KAMARUDDIN TAWI
UTM KUALA LUMPUR CAMPUS

Mechanical Switches

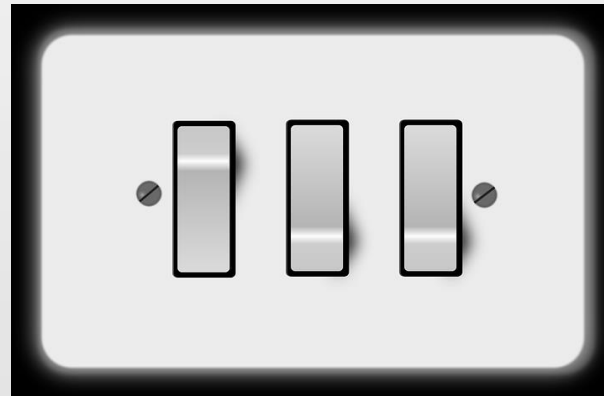- **Mechanical Switches are devices that turn ON and OFF the current flowing along a conductor or a circuit.**




Mechanical switches come in two basic types depending on the switching action.

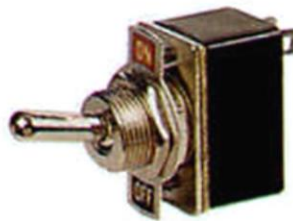- i. Permanent
- ii. Momentary

Permanent Switch

- Permanent type switch changes from 'On' to 'OFF' or 'OFF' to 'ON' and remains at the 'On' or 'OFF' position.
- Example of these switches are Toggle, Rocker, Slide, Rotary and Key switches.



Toggle Switch



Rocker Switch



Key switch

Momentary Switch

- The momentary switch need to apply a force to change the switch from 'ON' to 'OFF' or 'OFF' to 'ON'.
- When the force is removed, the switch immediately returns to its original position.
- Example are : Push, Reed and Micro switches



Push Switch



Reed Switch
 frm Wikimedia



Micro Switches
 frm Wikimedia

RELAY

- **Relays** act as remote switches that open and close circuits electromechanically or electronically.
- The relay control one **electrical** circuit by opening and closing contacts in another circuit.
- When a **relay** contact is closed the relay is said to be energized.

Types of Relay


1. Mechanical relay

Mechanical relays operate by applying a current through a coil magnet which then pull a flexible, spring-loaded conductive plate from one switch contact to another.



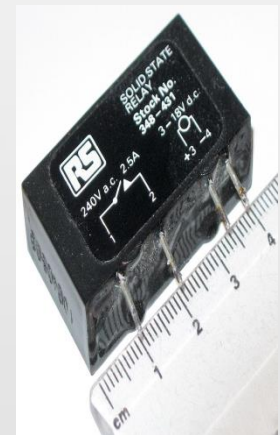2. Electronic relay (Solid – State Relay)

A **solid-state relay (SSR)** is an electronic switching device that contains no moving parts and switches on or off when a small external voltage is applied across its control terminals. In an SSR a small control signal controls a larger load current or voltage



Poles and Throws

1. **Poles** are considered as the input terminals of a switch and these define how many separate circuits the switch can control.

- A **single-pole** switch controls just one circuit.
- A **double-pole** switch controls two separate circuits.

2. **Throws** are considered as the output terminal of a switch and these define how many separate output circuits each of the switch's poles can be connected to

- A single-throw can connect to one output circuit
- A double-throw can connect to one of the two output circuits.

Arrangement of Relay

1. Single Pole Single Throw (SPST)
2. Single Pole Double Throw (SPDT)
3. Double Pole Single Throw (DPST)
4. Double Pole Double Throw (DPDT)




SPST



SPDT



DPST

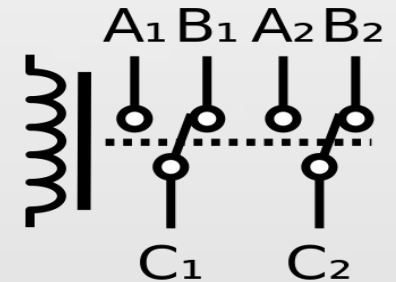

DPDT

References

1. Motor Control Fundamental, by Steve Senty, Cengage Learning, 2012, ISBN 1133709176, 9781133709176, 288 pages
2. National Instruments , 2016
 - Electric Relays: Principles and Applications (Electrical and Computer Engineering) by Vladimir I. Gurevich, 1st Edition , ISBN-13: 978-0849341885 , ISBN-10: 0849341884 , 704 pages
3. This Automotive Series , UNDERSTANDING RELAYS has been developed by Kevin R. Sullivan